
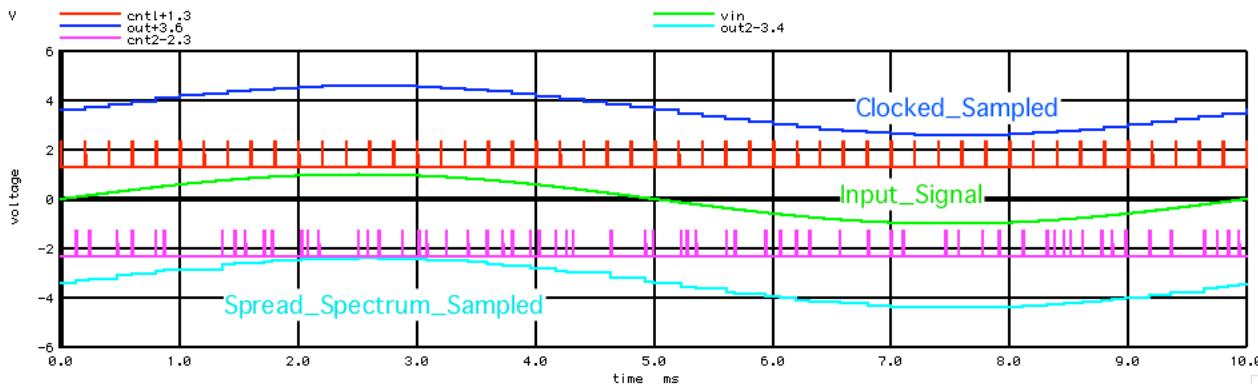


=====Spread_Spectrum_Sampling=====

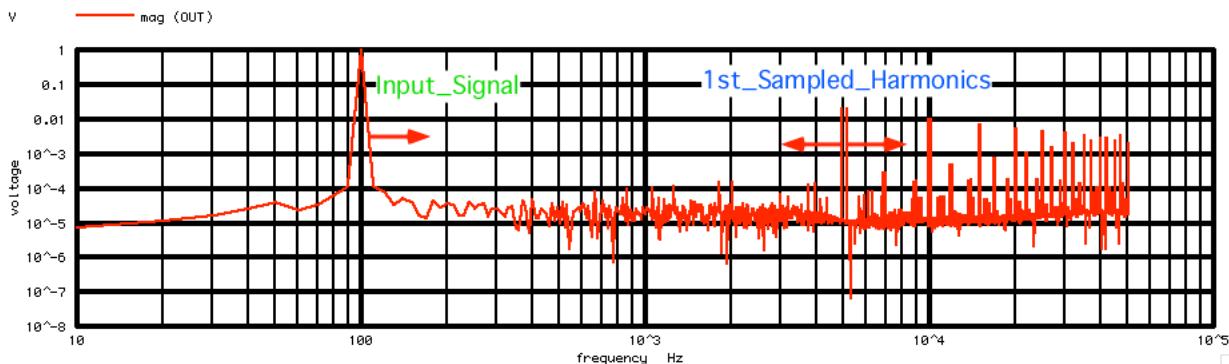
- 1) For **Clocked ADC**, the vin signal generates harmonics above and below multiples of the sample frequency.
 - 2) Adding around $\pm 1\text{ rms}$ radian of Phase Modulation to the clock appears to completely spread these harmonics out over the entire spectrum.
 - 3) A [paper](#) on Spread Spectrum Sampling is included below.



A sub Nyquist frequencies, the clocked and spread spectrum samples look about the same.



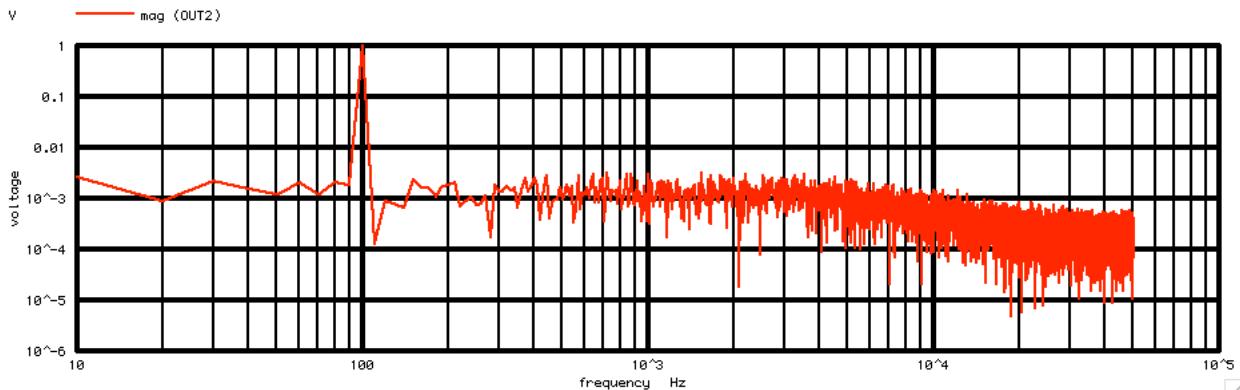
The sampling is at 5Khz. So a clock sampling produces harmonics at 5Khz +/- 100Hz, and 10Khz +/- 100Hz, and 15Khz +/- 100Hz , etc.



What the spread spectrum sampling does it that it spreads all the harmonic evenly around the whole spectrum.

-----MacSpiceCode-----

Spread_Spectrum_Sampling

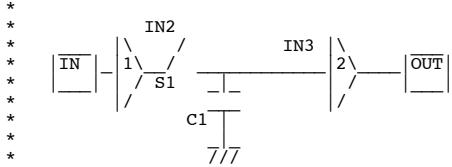

*=====Need_voltage_Sources_to_alter_with_PWL_Data=====

```

VT Vtime 0 - dc 0 PWL( 0 0 1 1 ) -
B0 SAW 0 V = atan(tan(3.141592653589793*500*v(Vtime)))
V1 V1 0 dc 0
*VSIN NODE_P NODE_N DC VALUE SIN( V_DC AC_MAG FREQ DELAY FDAMP)
VIN VIN 0 dc 0 SIN( 0 1 100 )
BVref Vref 0 V = u(sin(6.2831*5000*v(Vtime)))
BVjtit Vjtit 0 V = u(sin(6.28*5000*v(Vtime)+v(V1)))

```

```

XPE1 Vref CNTL POS_E
XPE2 V jit CNT2 POS_E
XS_H1 VIN CNTL OUT SH
XS_H2 VIN CNT2 OUT2 SH

.control
set pensize = 2
=====Want_1000_.1ms_steps=====
let n = 1000
let Nlev = 127
let tstep = .1ms
let Nrnd = 8
let Nbins = Nlev*Nrnd
echo "random levels 0-> $&Nlev"
echo "Numb rnd waveforms $&Nrnd"
echo =====Create_PhaseNoise_array=====
let PNoise = vector($&n)
let IntPNoise = vector($&n)
let ii = vector($&n)
let index = 0
repeat
let PNoise[index] = 3.14*(rnd(127)+rnd(127)+rnd(127)+rnd(127)+rnd(127)+rnd(127)+rnd(127)-507.5)/102.879
let index = index + 1
end
let averVal = mean(PNoise)
let noisAC = PNoise - averVal
let RmsVal = sqrt(mean(noisAC*noisAC))
echo "Average level $&averVal"
echo "RMS level $&RmsVal"
echo =====Create_PWL_arrays=====
let pwl_1 = vector(2*n)*.5*tstep
echo =====Create_Integrated_PhaseNoise_array=====
let n2 =
let index =
repeat
let pwl_1[2*index+1] = PNoise[index]
let index = index + 1
end
echo
alter @v1[pwl] = pwl_1
echo =====Run_and_Plot=====
10u 100m 0 10u
cntl+1.3 vin out+3.6 out2-3.4 cnt2-2.3 xlimit 0 10ms
echo =====FFT_and_Plot_OUT=====
linearize
let FFT_BandWidth_Hz = 50K
let FFT_resolution_Hz = 10
echo "FFT_BandWidth_Hz= $&FFT_BandWidth_Hz"
echo "FFT_resolution_Hz= $&FFT_resolution_Hz"
set specwindow = "rectangular"
specplot mag (OUT) loglog
echo =====FFT_and_Plot_OUT2=====
destroy
let FFT_BandWidth_Hz = 50K
let FFT_resolution_Hz = 10
echo "FFT_BandWidth_Hz= $&FFT_BandWidth_Hz"
echo "FFT_resolution_Hz= $&FFT_resolution_Hz"
set specwindow = "rectangular"
specplot mag (OUT2) loglog
echo =====Done=====

.endc

=====Sample_Hold=====
*
*          IN2
*          | \ / /
*          | 1 \ / S1
*          /   IN3
*          | \ / /
*          | 2 \ / | OUT
*          /   |
*          C1
*          |||/
*.SUBCKT SH IN CNTL OUT
B1 IN2 0 V = v(IN ) 0 SW
S1 IN2 IN3 CNTL 0
C1 IN3 0 .1u
R1 IN3 0 10Meg
B2 OUT 0 V = v(IN3 )
.ENDS

=====POS_Edge=====
*
*          VBF
*          | \ / /
*          | 3 \ / VLP [ PE ] -| OUT | | IN | -| PE | -| OUT |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*          | \ / \ / \ / | RLP | -| / | | / | | / | | / |
*.SUBCKT POS_E IN OUT
BBUF VBF 0 V = u( v(IN )-.5 )
RLP VBF VLP 10k

```

```
CLP      VLP      0      1n      IC=0
BAND    OUT      0      V =      u( u(v(VBF )-.5)*u(.5 -v(VLP )) -.1)
.ENDS  POS_E
```

```
.MODEL SW      SW(      VT=.5 VH=.1 RON=1 ROFF=100MEG)
```

```
.end
```

4.4.11_12.22PM
dsauersanjose@aol.com
Don Sauer