 


*-----CLASS_D_OPAMP-----

Suppose one wants to take the concept of a Class D amplifier to make an Op Amp. There are some important Gain bandwidth considerations if one wants to make this Op Amp unity gain stable.

CLASS_D_OpAmP_AC



In this simulation, the Op Amp is being modeled as an input transconductance stage which has its open loop gain defined by the input transconductance and R_B , and its bandwidth is defined by the input transconductance and C_{Comp} .

The output stage is being modeled as feeding the Op Amp's signal into one side of a voltage comparator which is seeing a triangle wave. The duty cycle output is fed into a Class D output stage.

* * * * *

VIN

VCC

VP

MP1

1000p

100u

Freq = 9 K

Z=5.80ohms

RFB

OUT

R1 = 5

Vhalf

VN

PWM

VG

RN

MN1

VOUT

INP

INN

VIN

* * * * *

```

.OPTIONS GMIN=1p          METHOD=trap      ABSTOL=1u      TEMP=27      srcsteps = 1      gminsteps = 1
.OPTIONS RELTOL=.001       ABSTOL=1n        VNTOL=1u      ITL4=500      ITL1=400
*=====Create_Signal=====
VT      VT      0      DC      0      PWL( 0      0      1      1)
Vfreq   Vfreq   0      DC      100k
B_TRI   TRI     0      V      =      acos( cos(6.283185*V(VFREQ)*V(VT)) )/3.141592
B_OTA   VD      0      I      =      -.3u*tanh((tanh(V(INP)-V(INN))*5)*1)
RB      VD      0      50meg
CCOMP   VD      0      50p
B_VD2   VD2    0      V      =      .5*tanh(v(VD) )+.5

```

```

BVG      VG      0      V =      5*u( v(TRI) -v(VD2))
VCC      VCC      0      DC      5
RPP      VCC      VP      1u
RN       VN       0      1u
MN1      VOUT     VG      VN      0      NMOSC    W=90000u    L=1u
MP1      VOUT     VG      VP      VCC    PMOSC    W=90000u    L=1u
L1       VOUT     OUT     100u
C1       OUT      0      3u
Rout     OUT      Vhalf   5
Vhalf    Vhalf   0      2.5
RFB      OUT      INN    1K
RIN      VIN      INP    1K
ccc      out      vout   1000p
VIN      VIN      0      DC      0      SIN( 2.5 2.4 100 )

```

*=====The_CMOS_Model_Files=====

```


.model  NMOSC      NMOS(Level= 1 Cbs=2f Cbd=2f)
.model  PMOSC      PMOS(Level= 1 Cbs=2f Cbd=2f)
.model  DD          D( IS=3.15e-18 )

.control
*TRAN  TSTEP  TSTOP  TSTART TMAX  ?UIC?
tran   .1u   20m    0      .1u
plot   out   vin
.endc

.end


```

 This simulation is showing a unity gain Op Amp configuration connected as a buffer to a 100Hz sine wave. But the Open loop gain of this "Op Amp" is only 150. This is for stability purposes.




What is making stability challenging is the fact that L1 at 100uH and C1 at 3uF are in the loop, and they provide two poles at 9kHz. The 5 Ohm value of RL is making those pole more real. But anyone who has designed Op Amps knows how adding open loop gain can make poles go complex

and migrate toward the right half plane.

 

The root locus of a more common Op Amp is shown below.
Adding open loop gain causes the two left most poles
to come together, split into complex poles, and then
migrate to the right side.

Units o : IPlot


 


A Root locus simulation has been done in MacSpice. It is online at the following site.

<http://www.idea2ic.com/PlayWithSpice/pdf/RootLocusPlot.pdf>

=====Full_Netlist_For_Copy_Paste=====

CLASS_D_OpAmp_AC

  

.OPTIONS GMIN=1p METHOD=trap ABSTOL=1u TEMP=27 srcsteps = 1 gminsteps = 1
.OPTIONS RELTOL=.001 ABSTOL=1n VNTOL=1u ITL4=500 ITL1=400

=====Create_Signal=====

VT	VT	0	DC	0	PWL(0	0	1	1)
Vfreq	Vfreq	0	DC	100k					
B_TRI	TRI	0	V	=	acos(cos(6.283185*V(VFreq)*V(VT)))	/3.141592	
B OTA	VD	0	I	=	-.3u*tanh((tanh(V(INP)-V(INN))*5)*1)				
RB	VD	0	50meg						
CCOMP	VD	0	50p						
B_VD2	VD2	0	V	=	.5*tanh(v(VD))	+.5			
BVG	VG	0	V	=	5*u(v(TRI) -v(VD2))			
VCC	VCC	0	DC	5					
RPP	VCC	VP	1u						
RN	VN	0	1u						
MN1	VOUT	VG	VN	0	NMOSC	W=90000u	L=1u		
MP1	VOUT	VG	VP	VCC	PMOSC	W=90000u	L=1u		
L1	VOUT	OUT	100u						
C1	OUT	0	3u						
Rout	OUT	Vhalf	5						
Vhalf	Vhalf	0	2.5						
RFB	OUT	INN	1K						
RIN	VIN	INP	1K						
ccc	out	vout	1000p						
VIN	VIN	0	DC	0	SIN(2.5	2.4	100)

=====The_CMOS_Model_Files=====

```
.model NMOSC                    NMOS(Level= 1 Cbs=2f Cbd=2f)
.model PMOSC                    PMOS(Level= 1 Cbs=2f Cbd=2f)
.model DD                        D( IS=3.15e-18 )
```

```
.control
*TRAN TSTEP TSTOP TSTART TMAX ?UIC?
```

```
tran      .1u    20m      0      .1u
plot      out    vin
.endc
.end
```

9.16.10_1.23PM
dsauersanjose@aol.com
Don Sauer