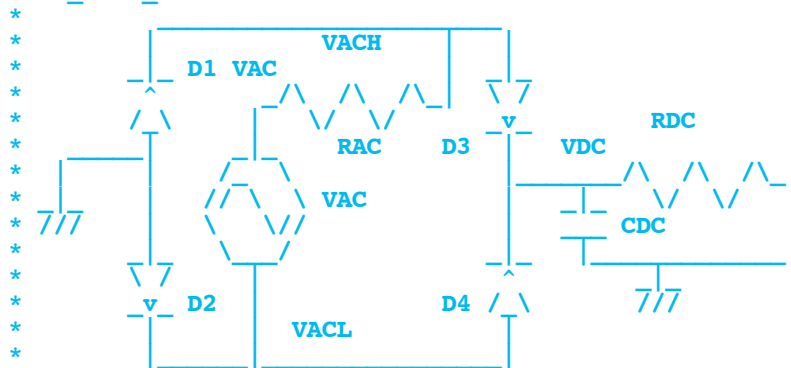


***=====FULL_WAVE_RECTIFIER_POWER=====**

How energy efficient are full wave rectifiers?

FULL_WAVE_RECTIFIER



```
.OPTIONS GMIN=1p METHOD=trap ABSTOL=1u TEMP=27 srcsteps = 1 gminsteps = 1
.OPTIONS RELTOL=.001 ABSTOL=1n VNTOL=1u ITL4=500 ITL1=400
```

```
*=====Create_Signal=====
VAC VAC VACL DC 0 SIN( 0 24 60 )
```


```
D1 0 VACH DD
D2 0 VACL DD
D3 VACH VDC DD
D4 VACL VDC DD
RAC VACH VAC 1m
RDC VDC 0 10k
CDC VDC 0 30u
```

```
*=====The_Model_Files=====
.model DD D( IS=3.15e-18 rs = 1m)
```

```
.control
*TRAN TSTEP TSTOP TSTART TMAX ?UIC?
tran .1m 120m 20m .1m
```


Create a 60Hz sine wave with a 24V peak magnitude and here are the following output waves.
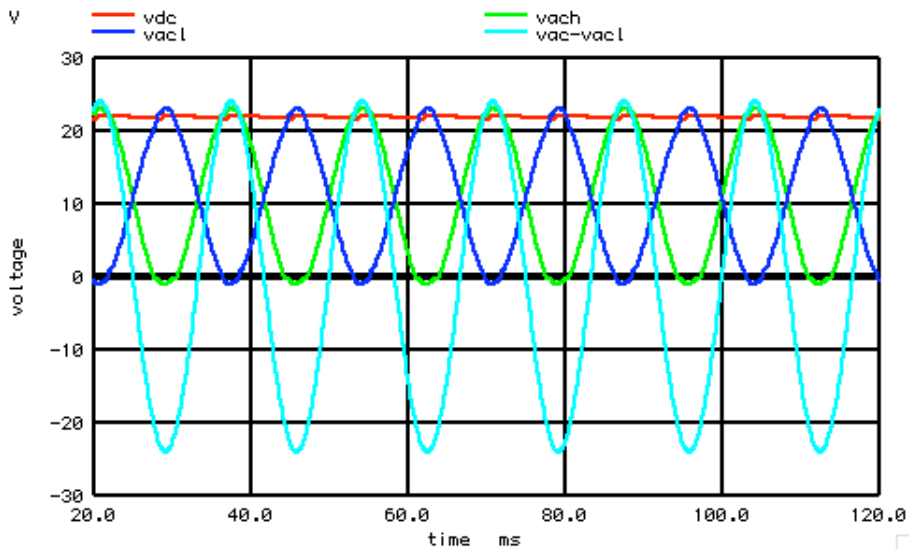
```
set pensize = 2
plot vdc vach vacl vac-vacl
```



Now look at power over time.
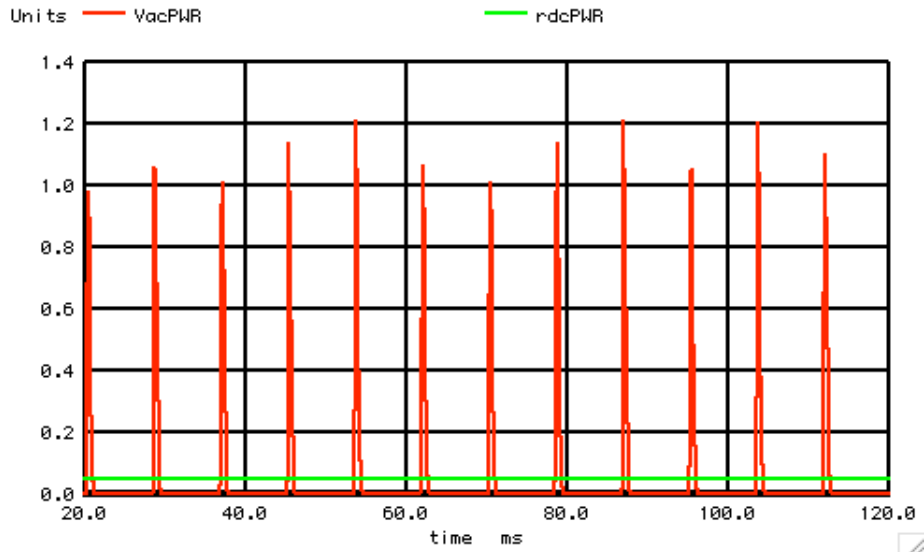
```
let vaci = (vac-vach)/lm
let VacPWR= vaci*(vac-vac1)
let rdcPWR=vdc*vdc/10k
plot VacPWR rdcPWR
```



Now use some vector processing to **find efficiency**.
Predict efficiency by subtracting two diodes from the
24volt peak AC waveform.


```
let VacPWRave = mean(VacPWR )
let rdcPWRave = mean( rdcPWR)
let lossPWR = VacPWRave -rdcPWRave
let EffPWR = rdcPWRave/VacPWRave
let DlossRatio = (24-1.6)/24
echo "VacPWRave =$&VacPWRave rdcPWRave =$&rdcPWRave lossPWR =$&lossPWR "
echo "EffPWR =$&EffPWR DlossRatio =$&DlossRatio
```

```
VacPWRave =0.0513707 rdcPWRave =0.0479852 lossPWR =0.00338558
EffPWR =0.934095 DlossRatio =0.933333
```

The predicted efficiency comes close to the actual efficiency.

=====**Full_Netlist_For_Copy_Paste**=====

FULL_WAVE_RECTIFIER

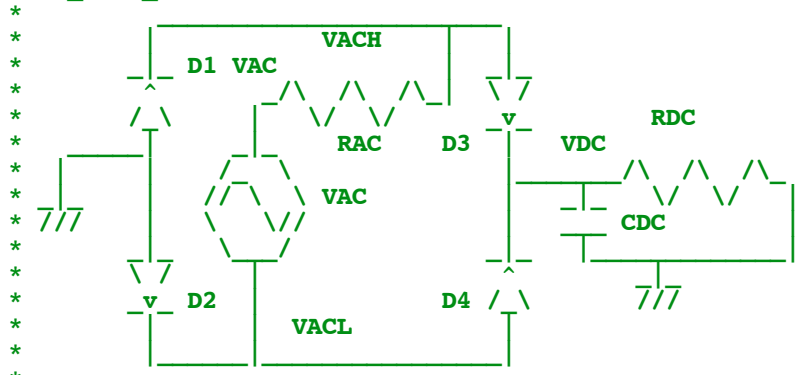

```
**
.OPTIONS GMIN=1p METHOD=trap ABSTOL=1u TEMP=27 srcsteps = 1 gminsteps = 1
.OPTIONS RELTOL=.001 ABSTOL=1n VNTOL=1u ITL4=500 ITL1=400
```

```
*=====Create_Signal=====
VAC VAC VACL DC 0 SIN( 0 24 60 )
D1 0 VACH DD
D2 0 VACL DD
D3 VACH VDC DD
D4 VACL VDC DD
RAC VACH VAC 1m
RDC VDC 0 10k
CDC VDC 0 30u
```

```
*=====The_Model_Files=====
.model DD D( IS=3.15e-18 rs = 1m)
```

```
.control
*TRAN TSTEP TSTOP TSTART TMAX ?UIC?
tran .1m 120m 20m .1m
set pensize = 2
plot vdc vach vacl vac-vacl

let vaci = (vac-vach)/1m
let VacPWR= vaci*(vac-vacl)
let rdcPWR=vdc*vdc/10k
plot VacPWR rdcPWR

let VacPWRave = mean(VacPWR )
let rdcPWRave = mean( rdcPWR)
let lossPWR = VacPWRave -rdcPWRave
let EffPWR= rdcPWRave/VacPWRave
let DlossRatio = (24-1.6)/24
echo "VacPWRave =$&VacPWRave rdcPWRave =$&rdcPWRave lossPWR =$&lossPWR "
echo "EffPWR =$&EffPWR DlossRatio =$&DlossRatio "
.endc
.end
```

9.16.10_12.48PM
dsauersanjose@aol.com
Don Sauer