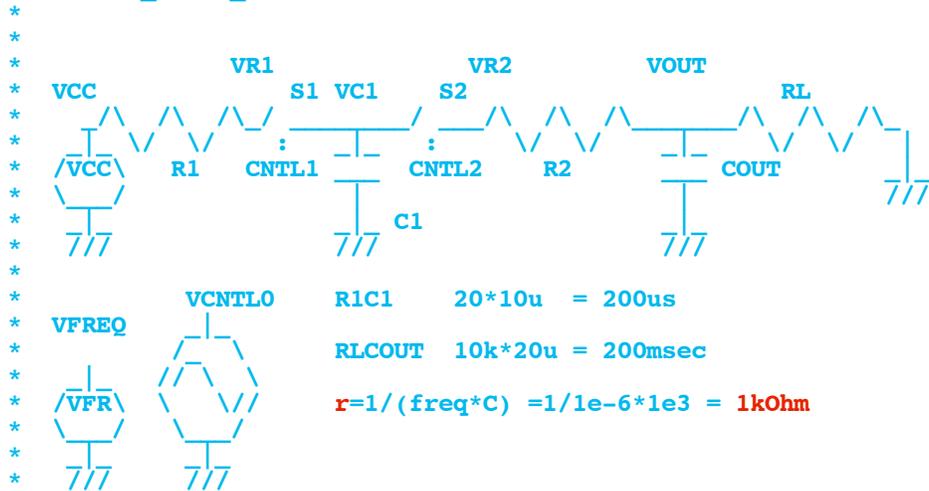


**\*=====SWITCH\_CAPACITOR\_POWER=====**

**How energy efficient are switched capacitors?**

**SWITCHING\_POWER\_LOSS**



$R1C1 = 20 \times 10\mu = 200\mu s$   
 $RLCOUT = 10k \times 20\mu = 200msec$   
 $r = 1 / (freq * C) = 1 / (1e-6 * 1e3) = 1k\Omega$

```


.OPTIONS GMIN=1f METHOD=trap ABSTOL=1u TEMP=27 srcsteps = 1 gminsteps = 1
.OPTIONS RELTOL=.001 ABSTOL=1n VNTOL=1u ITL4=500 ITL1=400

```

```

=====Create_Signal=====
VTime VTime 0 DC 0 PWL( 0 0 1 1)
Vfreq Vfreq 0 DC 1k
BVCNTL0 VCNTL0 0 V = sin( 6.283185*V(VFreq)*V(VTime))
BVCNTL1 VCNTL1 0 V = u( v(VCNTL0) -.3)
BVCNTL2 VCNTL2 0 V = u( -1*v(VCNTL0) -.3)
VCC VCC 0 DC 1
R1 VCC VR1 10
S1 VR1 VC1 VCNTL1 0 SWP
C1 VC1 0 1u
S2 VC1 VR2 VCNTL2 0 SWP
R2 VR2 VOUT 10
COUT VOUT 0 20u
RL VOUT 0 10K
.MODEL SWP SW( VT=.5 VH=.2 RON=1m ROFF=100MEG)
.control
*TRAN TSTEP TSTOP TSTART TMAX ?UIC?
tran 10u 100m 0 10u
set pensize = 2
plot vout

```

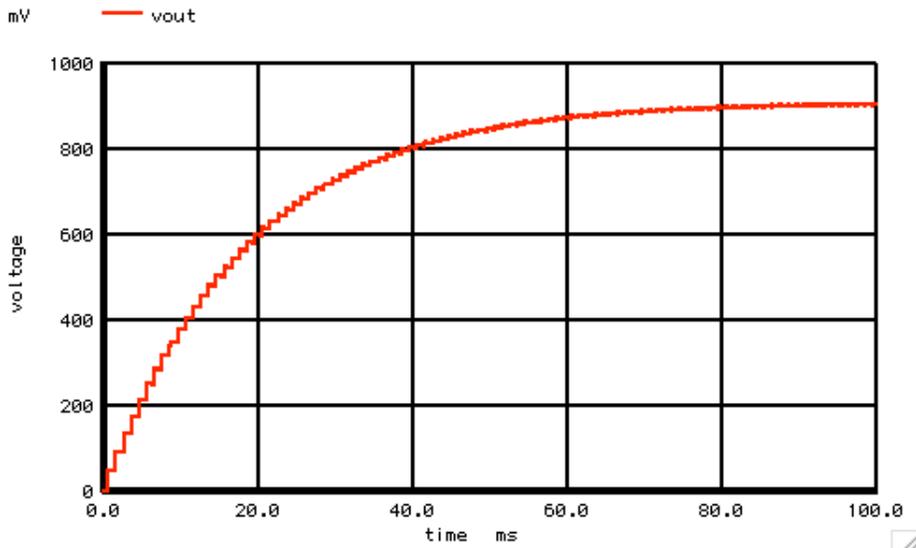


The switch capacitor should appear as a 1k Ohm resistor.

$$r_{out} = 1/(freq * C) = 1/1e-6 * 1e3 = 1k\Omega$$

With 20uF at the output, the RC should be 20msec.  
So start the simulation after 200msec.
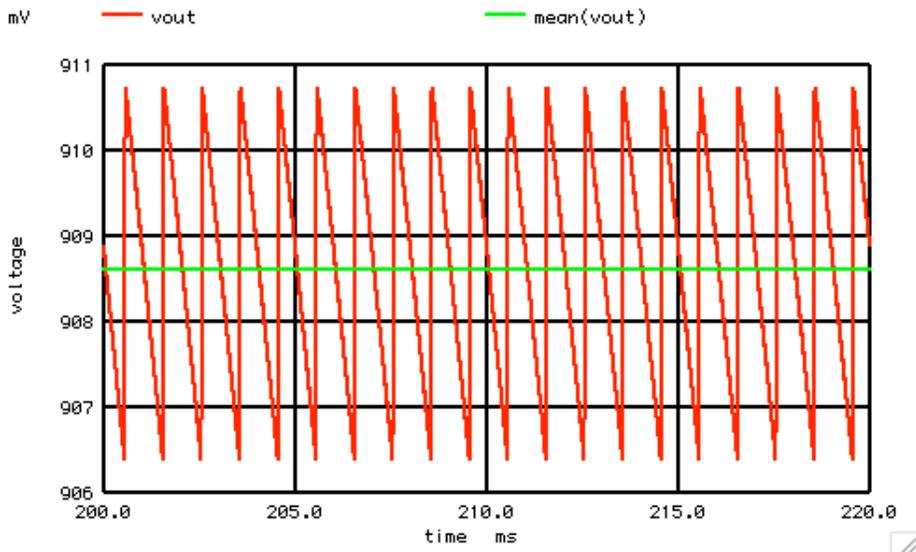
```
tran      3u      220m      200m      3u
plot      vout    mean(vout)
```



Calculating power loss from DC values is easy.

```
let      iout      = mean(vout)/10K
let      pwr      = 1*iout
let      pwrout   = mean(vout)*iout
let      pwrloss  = pwr - pwrout
echo     "iout=$iout pwr=$pwr pwrout=$pwrout pwrloss=$pwrloss "
```





```

let      irr2 = (vr2-vout)/10
let      irr2rms = sqrt(mean(irr2*irr2))
let      pwrr2 = irr2rms*irr2rms*10
let      pwrr1r2= pwrr1+ pwrr2
print

plot      vr2-vout pointplot xlimit 200m 201m
plot      vr2-vout          xlimit 200m 201m

```

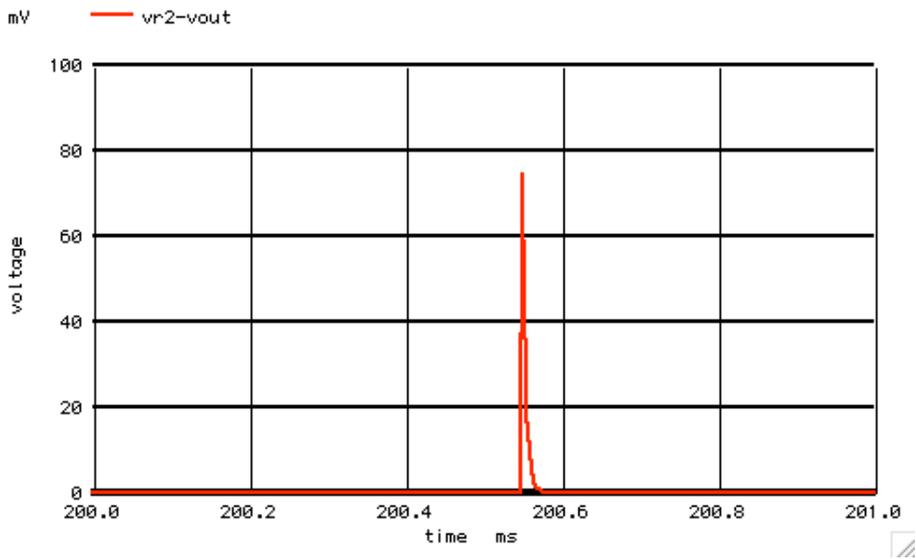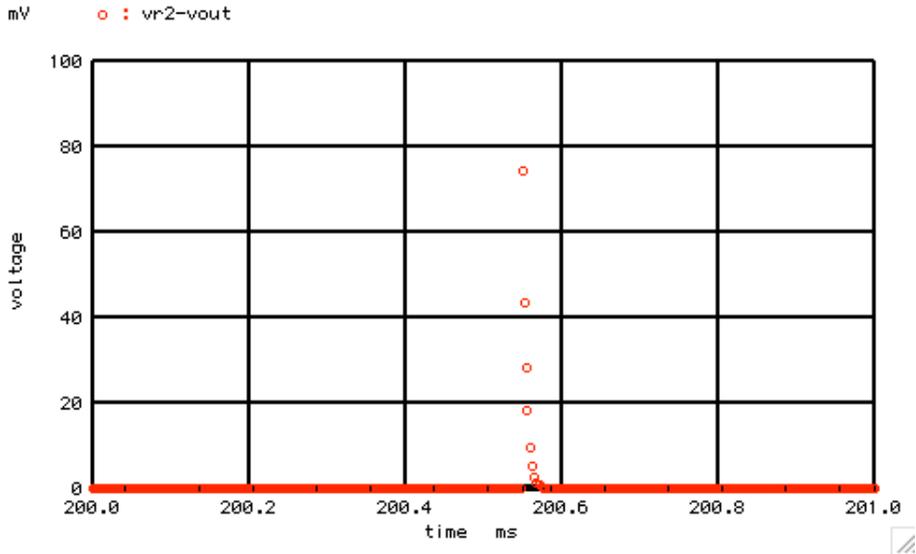

**pwrloss = 8.3035E-06**

**pwrr1r2 = 1.35964e-05**

=====  
The non uniform timing of data points gives a calculated power in the switch resistors to be a factor of two too high.

Linearizing the time points will make things worse.

One solution is to scale each measurement by the difference

in time between all the points.


```
=====
set      numb      = length(vout)
let     numb2     = length(vout)-1
print   numb
let     dtscale   = vector($&numb)

let     indx      = 1
repeat  $&numb2
let     dtscale[indx] = ($&numb)*(time[indx] -time[indx-1])/(time[$&numb2]-time[0])
let     indx      = indx +1
end

let     dtscale[0] = dtscale[1]
let     irr1rms   = sqrt(mean(irr1*irr1*dtscale))
let     pwrr1    = irr1rms*irr1rms*vres[0]
let     irr2rms   = sqrt(mean(irr2*irr2*dtscale))
let     pwrr2    = irr2rms*irr2rms*vres[0]
let     pwrr1r2  = pwrr1+ pwrr2

print   pwrr1r2
print   vres[0]

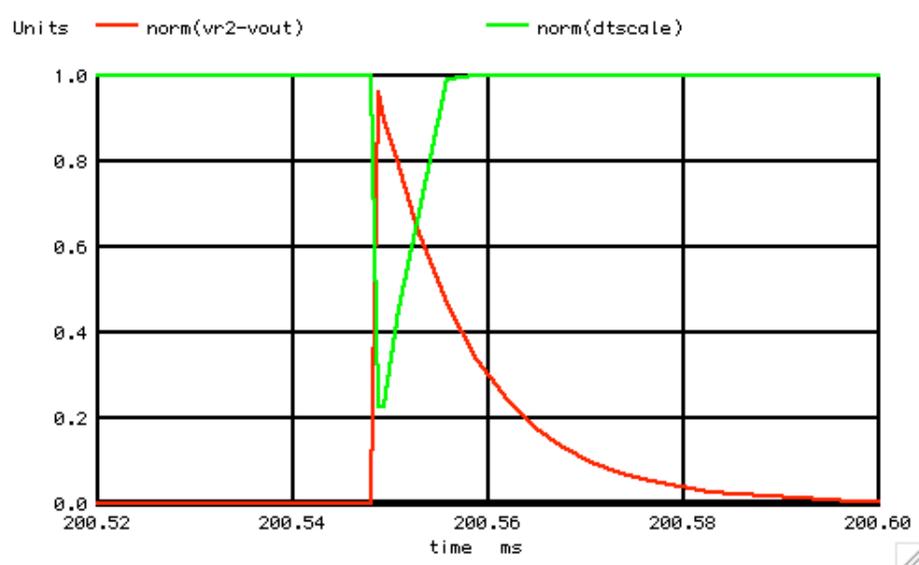plot    norm(vr2-vout) norm(dtscale) xlimit 200.52m 200.60m
```



```
numb      = 6.81100e+03
pwrr1r2   = 7.03901e-06
pwrloss   = 8.30716E-06
```

Now the power in the switch resistors come within 85% of the value calculated from the DC values.

A resistive voltage divider consisting of a 1K Ohm and a 10K Ohm resistor should produce a .9090V output with a 1 volt input. The simulated value is 99.946% of that. So powers loss is all due to the fact that the switch capacitor is looking like a simple 1K Ohm resistor.

$$\text{rout} = 1/(\text{freq} * C) = 1/1e-6 * 1e3 = 1k\text{Ohm}$$



```

S1      VR1      VC1      VCNTL1  0      SWP
C1      VC1      0        1u
S2      VC1      VR2      VCNTL2  0      SWP
R2      VR2      VOUT     10
COUT    VOUT     0        20u
RL      VOUT     0        10K
.MODEL  SWP      SW(      VT=.5    VH=.2    RON=1m  ROFF=100MEG)

.control
*TRAN   TSTEP   TSTOP   TSTART  TMAX   ?UIC?
tran    10u    100m   0       10u
set     pensize = 2
plot    vout

tran    3u    220m   200m   3u
plot    vout mean(vout)

let     iout = mean(vout)/10K
let     pwrt = 1*iout
let     pwrou = mean(vout)*iout
let     pwrloss = pwrt- pwrou
echo    "iout=$&iout pwrt = $&pwrt pwrou=$&pwrou pwrloss = $&pwrloss "
plot    vr2-vout

*linearize
let     numb = length(vout)
let     numb2 = length(vout)-1
let     irr1 = (vcc-vr1)/10
let     irr1rms = sqrt(mean(irr1*irr1))
let     pwrr1 = irr1rms*irr1rms*10
let     irr2 = (vr2-vout)/10
let     irr2rms = sqrt(mean(irr2*irr2))
let     pwrr2 = irr2rms*irr2rms*10
let     pwrr1r2= pwrr1+ pwrr2
print   pwrr1r2

plot    vr2-vout pointplot xlimit 200m 201m
plot    vr2-vout xlimit 200m 201m
plot    vr2-vout

let     numb = length(vout)
let     numb2 = length(vout)-1
print   numb
let     dtscale = vector($&numb)
let     indx = 1
repeat  $&numb2
let     dtscale[indx] = ($&numb)*(time[indx] -time[indx-1])/(time[$&numb2]-time[0])
let     indx = indx +1
end
let     dtscale[0]= dtscale[1]

let     irr1rms = sqrt(mean(irr1*irr1*dtscale))
let     pwrr1 = irr1rms*irr1rms*10
let     irr2rms = sqrt(mean(irr2*irr2*dtscale))
let     pwrr2 = irr2rms*irr2rms*10
let     pwrr1r2= pwrr1+ pwrr2
print   pwrr1r2

plot    norm(vr2-vout) norm(dtscale) xlimit 200.52m 200.60m

.endc

.end

```

```

9.16.10_12.57PM
dsauersanjose@aol.com
Don Sauer

```