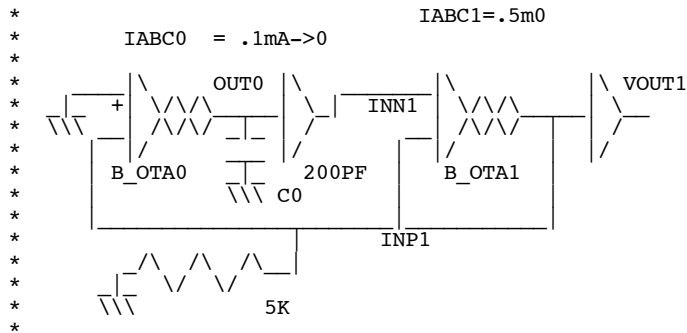


OTA\_TRI\_SQUAR  
 \* dsauersanjose@aol.com 10/07/08  
 \* www.idea2ic.com




```
.OPTIONS GMIN=1e-18 METHOD=trap srcsteps = 1 gminsteps = 1 trtol=1 VNTOL=1m
V_Iabc0 VIABC0 0 PWL ( 0 .1m 1m 0 )
B_OTAO OUT0 0 I = -1*(v(VIABC0)+v(VHI))*tanh( v(INP1)/.052)
C0 OUT0 0 2000p IC=1
B_BUF0 INN1 0 V = v(OUT0)
V_Iabc1 VIABC1 0 DC .5m
B_OTA1 INP1 0 I = -1*v(VIABC1)*tanh( (v(INP1)-v(INN1)) /.052)
R1 INP1 0 5k
B_BUF1 VOUT1 0 V = v(INP1)
Cstray INP1 0 15p
B_U VHI 0 V = u(V(INP1))*1m
.tran .1u 1m 0 .1u UIC

.control
run
set pensize = 2
plot v(inp1) v(out0)
.endc

.end
```

=====END\_OF\_SPICE=====

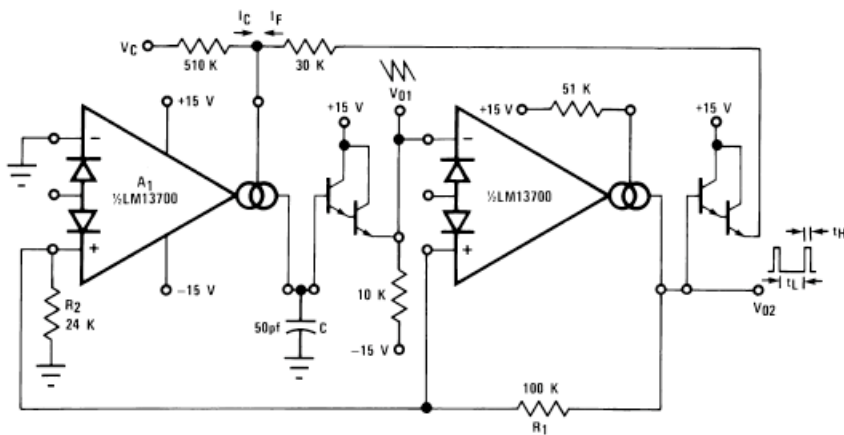To Covert PDF to plain text click below  
<http://www.fileformat.info/convert/doc/pdf2txt.htm>  
 This code works with winspice.



00798123

$$V_{PK} = \frac{(V^+ \pm 0.8V) R_2}{R_1 + R_2}$$

$$t_H \approx \frac{2V_{PK}C}{I_F}$$

$$t_L = \frac{2V_{PK}C}{I_C}$$

$$f_0 \approx \frac{I_C}{2V_{PK}C} \text{ for } I_C \ll I_F$$

FIGURE 16. Ramp/Pulse VCO

