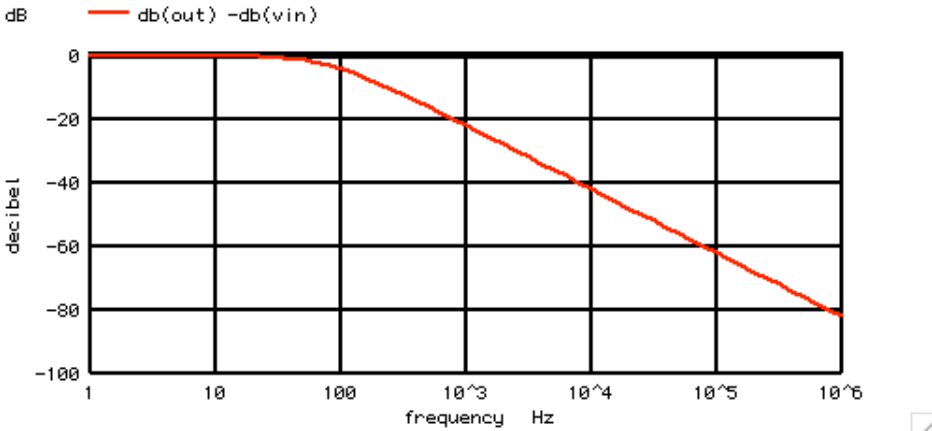






Graph 27 - ac33: Gain2OUT@IABC10uA



At 1000uA, the 3dB bandwidth has increased to 1530Hz. So the 0.22uF is effectively reduced by a factor of 20.

Graph 17 - ac20: Gain2OUT@IABC1000uA

