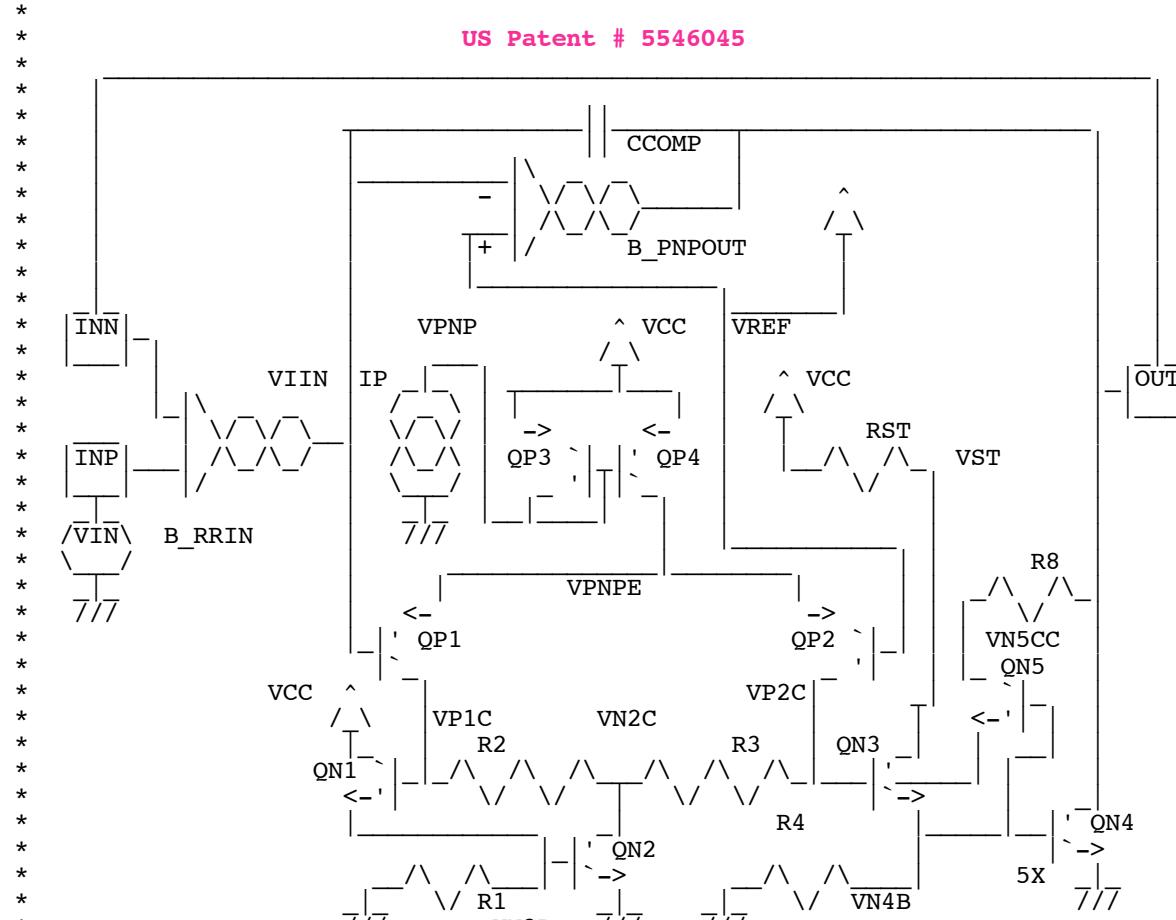


OUTPUT_CLAMP_REQUIREMENTS

* dsauersanjose@aol.com 12/17/08

* www.idea2ic.com



.OPTIONS method=trap

VIN	INP	0	SIN(6	6.1	1K)	AC 1m
VREF	VREF	0	DC	6		
VCC	VCC	0		12		

```

IP      VPPNP    0      40u
B_RRIN  VRRIN    0      I = ( V(INP) - V(OUT) )/5000
CBYP    VRRIN    VIIN   1k

QP1      VP1C     VIIN   VPPNP    PNPV    1
QP2      VP2C     VREF    VPPNP    PNPV    1
QP3      VPPNP    VPNP    VCC     PNPV    1
QP4      VPPNP    VPNP    VCC     PNPV    1

QN1      VCC      VP1C    VN2B    NPNV    1
QN2      VN2C    VN2B    0       NPNV    1
QN3      VST      VP2C    VN4B    NPNV    1
QN4      OUT      VN4B    0       NPNV    10
R1       VN2B    0       20K
R2       VP1C     VN2C    5K
R3       VP2C     VN2C    5K
R4       VN4B    0       10K

RST      VCC      VST    1
R8       OUT      VN5CC   300k
QN5      VN5CC   VN4B    VP2C    NPNV    1

CCOMP    OUT      VIIN   10p
BOTA    OUT      0       I = -200u

CBYP    VRRIN   VP2C    4p

.tran    1u      2m      0      1u
.model   NPNV    npn     BF=150  BR=5
.model   PNPV    pnp     BF=60   BR=5

.control
run
let Vshootthru =( V(vcc)-V(vst))*1e3
plot   V(Vshootthru) V(out) title WithShootThur

alter R8 resistance = 300
run
let Vshootthru =( V(vcc)-V(vst))*1e3
plot   V(Vshootthru) V(out) title WithoutShootThur


.endc
.end

```

* ======END=====


To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

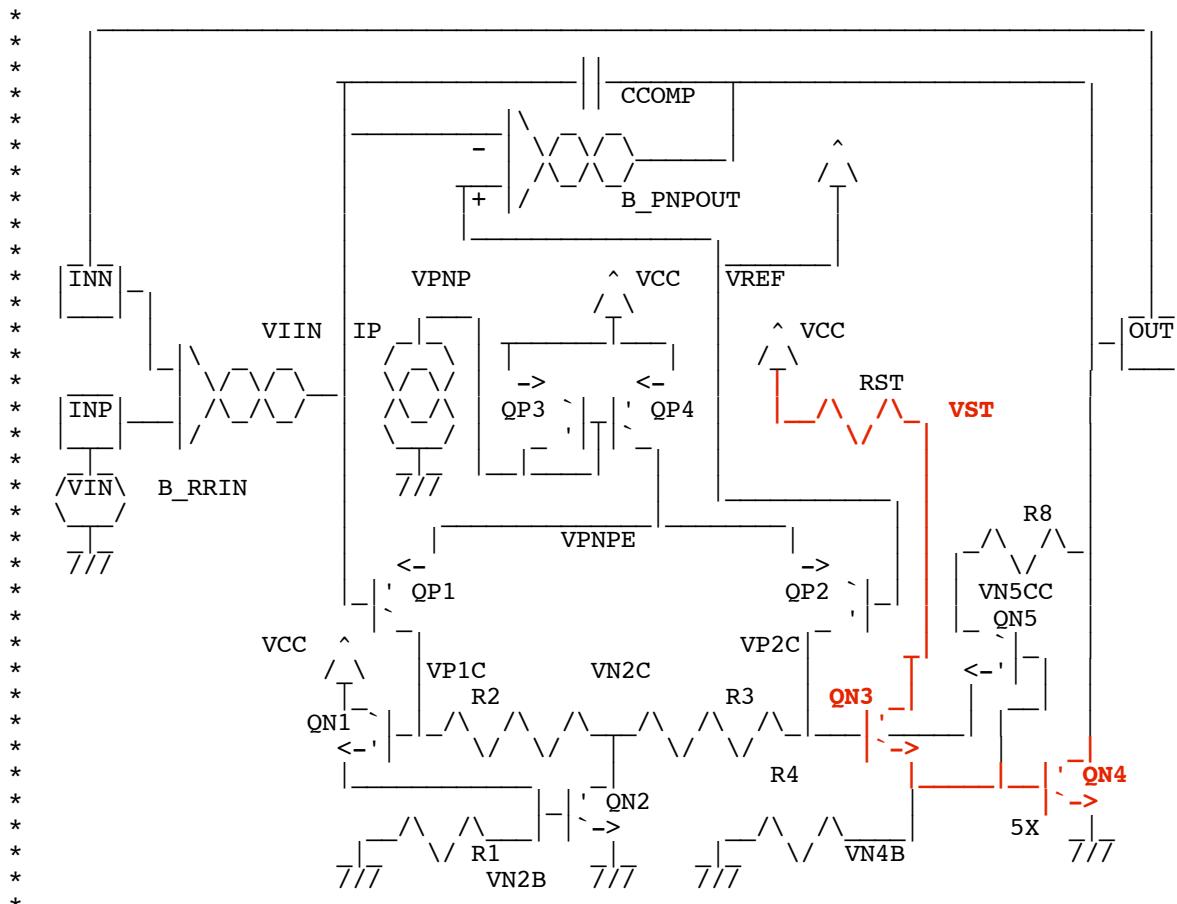There are often hidden features inside an Op Amp design such as having an input that can exceed the supplies without phase reversal and having graceful death at low supply voltage. Another hidden feature has to do with addressing a supply current shoot thru problem.




When an output transistor like QN4 saturates, the transistor

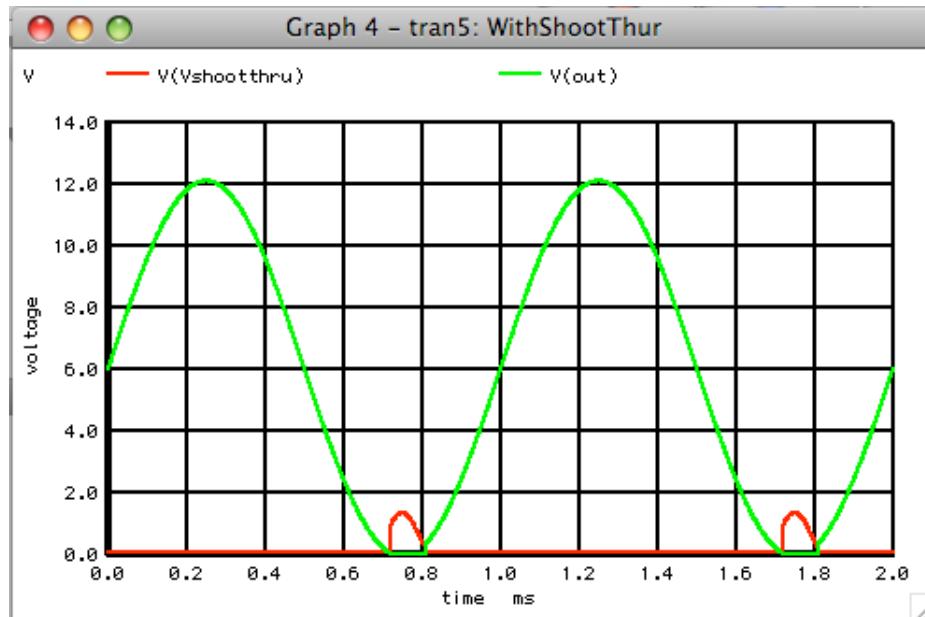
driving the output transistor will try to dump a lot of current into the base of the output transistor. This has two negative effects. First, there will be a lot of charge in the base which will take some effort to remove in order for the output transistor to come out of sat. Second, the collector current of transistors like QN3 which are driving the output transistor will greatly increase.



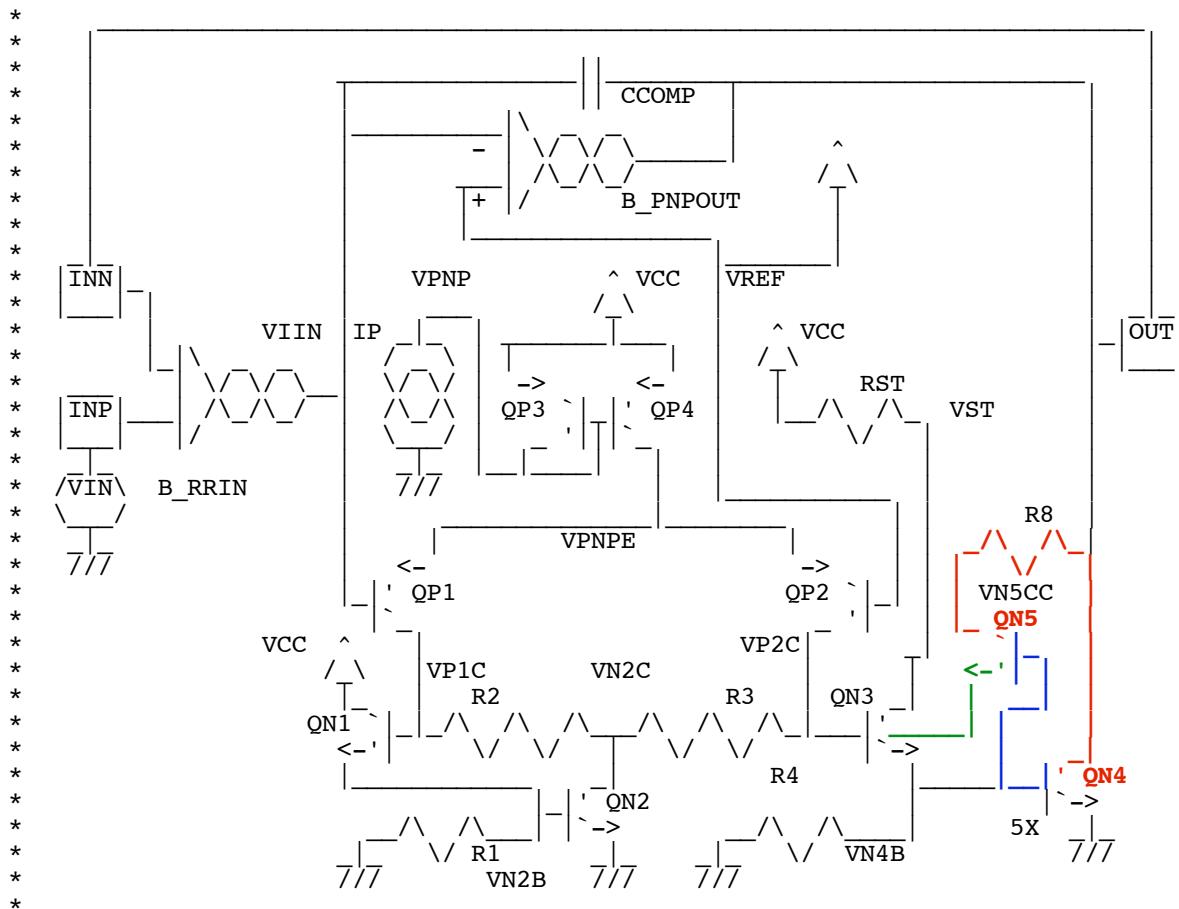This means every time the output hits one of the rails, an supply current spike will happen which is referred to a a shoot thru current.



This problem can be handle by building an output transistor saturation current limit. Transistor QN5 is a reverse connected transistor which is using the collector junction as an emitter and the emitter is being used as a collector. The performance of such a transistor is not great. But since QN6 and QN4 are both npns, the "emitter base" of QN5 will turn on exactly when the collector base of QN4 turns on. Some adjustments like R8 are sometimes needed to optimize this type of current limit.

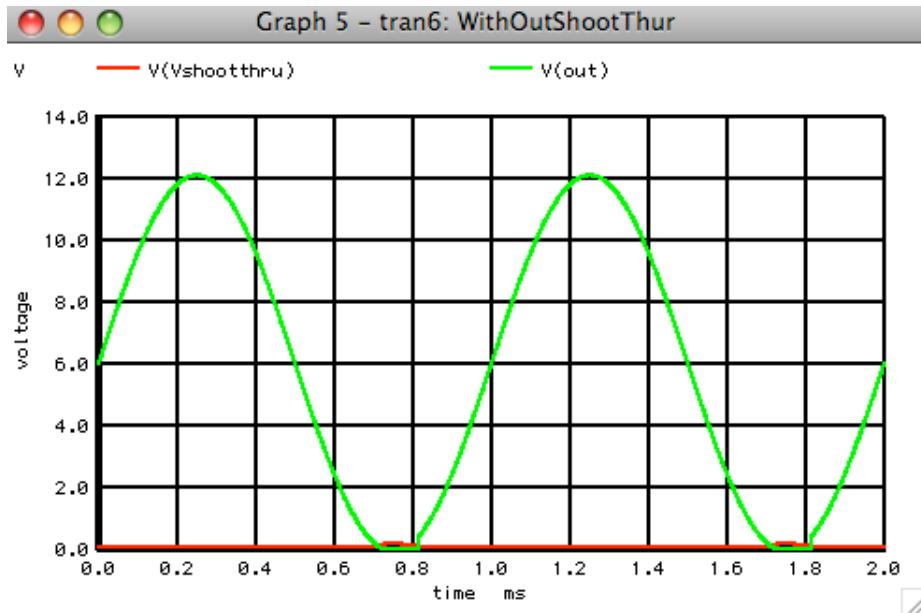

Both the supply current shoot thru problem and the recovery from output saturation problem are improved. Features like this are not listed in the spec itself. But customers expect them anyway.