 


OUTPUT_REQUIREMENTS

* dsauersanjose@aol.com 12/17/08

* www.idea2ic.com

* US Patent # 5546045



.OPTIONS method=gear GMIN=1e-18

VIN INP 0 SIN(6 3 1K)

VCC VCC 0 12
IP VPNP 0 40u

B_RRIN VIIN 0 I = (V(INP) - V(OUT))/5000

QP1	VP1C	VIIN	VPNPE	PNPV	1
QP2	VP2C	VREF	VPNPE	PNPV	1
QP3	VPNPE	VPNP	VCC	PNPV	1
QP4	VPNP	VPNP	VCC	PNPV	1
QP5	VP5C	VPNP	VCC	PNPV	4
QN1	VCC	VP1C	VN2B	NPNV	1
QN2	VN2C	VN2B	0	NPNV	1
QN3	VCC	VP2C	VN4B	NPNV	1
QN4	OUT	VN4B	0	NPNV	10
QN5	VREF	VREF2	0	NPNV	1
R5	VREF2	0	6K		
R6	VREF	VREF2	12K		
R7	VP5C	VREF	18K		
R1	VN2B	0	20K		
R2	VP1C	VN2C	5K		
R3	VP2C	VN2C	5K		
R4	VN4B	0	10K		
CCOMP	OUT	VIIN	10p		
BOTA	OUT	0	I = -200u		

.tran 1u 2m 0 1u

.model NPNV npn BF=150
 .model PNPV pnp BF=60

.control
 run
 set pensize = 2
 plot v(inp) v(out)


dc vCC 1 12 100m
 plot v(vref) v(vp5c)
 .endc
 .end

* ======END=====

To Covert PDF to plain text click below

<http://www.fileformat.info/convert/doc/pdf2txt.htm>

The output stage introduces a number of requirements.
First off, the actual outputs are collectors of transistor.
Then there is a need to have a lot of input to output
current gain. Then there is this need to work down to the
same voltage requirements as the input stage. That is to
work down to a supply voltage of 2 diodes and two sats.
Then there is the low supply current requirement. Then there
is high bandwidth requirement. Then there is the unity gain
stability with a 200pF cap load requirement.

 


*
The bottom NPN half of the output stage is shown above. The top PNP half is an exact mirror image of the NPN half and is represented by B_PNPOUT. The current gain supplied by QN4, QN3, and QP1. If VREF is at half supply, then QP3, QP2, QN3 and QN4 can work down to two diodes and two sats.


For supply rejection reasons, it is not desirable that VREF should be modulated by VCC. The circuit above shows a simplified version used in the LM6142.

There is an unwritten spec that an Op Amp should have a "graceful death" when the supply voltage is lowered. Ideally what this means is the the Op Amps should still function but progressively degrade in performance as the supply voltage is lowered. Having an Op Amp go crazy at low voltages does not go unfixed.

 The LM6142 was originally designed for the 5V and 12V market. Below 5 volts, it was OK to start graceful death at the output stage. While the circuit below is not exact, it shows the details under consideration.



 Above 5 volts a current source biases up a diode multiplier to provide a stable VREF. The plot of VP5C and Vref versus VCC shown below somewhat resembles the LM6142. Transistor QP5 is set up to saturate such that a 2.4V supply voltage generates a VREF which is at 1.2V.



This feature worked so well that it was found that the part was solid at both 2.4Volts and 24volts. So the data sheet specs were extended to those supply specs as well.