 


## Rrio\_Clamp\_requirements

\* dsauersanJose@aol.com 12/17/08

\* www.idea2ic.com



.OPTIONS method=trap

VIN	INP	0	PULSE( 1 9 1n 1n 1n 10u 20u )		
RS1	INP	INP2	7000		
QP5	OUT	OUT	INP2	PNPV	1
QN5	OUT	OUT	INP2	NPNV	1
QP1	VP1	INP2	VPNP	PNPV	1
QP2	VP2	OUT	VPNP	PNPV	1
QP3	VPNP	VP	VCC	PNPV	1
QP4	VP	VP	VCC	PNPV	1
RP1	VP1	0	5K		
RP2	VP2	0	5K		
QN1	VN1	INP2	VNPN	NPNV	1
QN2	VN2	OUT	VNPN	NPNV	1

```

QN3      VNPN  VN      0      NPNV    1
QN4      VN      VN      0      NPNV    1
RN1      VCC    VN1     5K
RN2      VCC    VN2     5K

VCC      VCC    0      12
VREF     VREF    0      6
IPNP     VP      0      20u
INPN     VCC    VN     20u

BDITA    VIOUT  0      I = ( V(VP2) - V(VP1) + V(VN2) - V(VN1) )/5000
BOTA     OUT     0      I = -1*( V(VIOUT) - V(VREF) )/50
CCOMP    OUT     VIOUT 20p

.tran    100n   50u    0      100n

.model   NPNV npn BF=150
.model   PNPV pnp BF=150


.control
run
set      pensize = 2
plot    v(out) v(inp)
.endc
.end

```

\* ======END=====

To Convert PDF to plain text click below  
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

 
The development of vertical pnps was a natural for RRIO Op Amp Design. The vertical pnps are about a thousand times faster and have at least ten times better beta than lateral pnps.



For the LM6142, the tail currents IPNP of the input stages was chosen by weighing an input bias current spec against a process beta spec. That chosen, the desired GainBandWidth for the Op Amp defines the magnitude of the compensation capacitor CCOMP used. This in turn

defines the slew of the Op amp which is simply +/- full tail current into the compensation capacitor CCOMP.

 Connecting the Op Amp up as a simple voltage follower demonstrates why the input clamp diodes are needed. Both vertical npns and pnps will be destroyed with reverse emitter base voltages above a few volts. Just supplying a square wave to a voltage follower application will do that because the output of the Op Amp may not be able to slew as fast as the input signal.



In the case of this simulation, current limiting resistor RS1 and clamp diodes QN5 and QP5 keep the voltages across the input transistors to within reason during the slewing period.