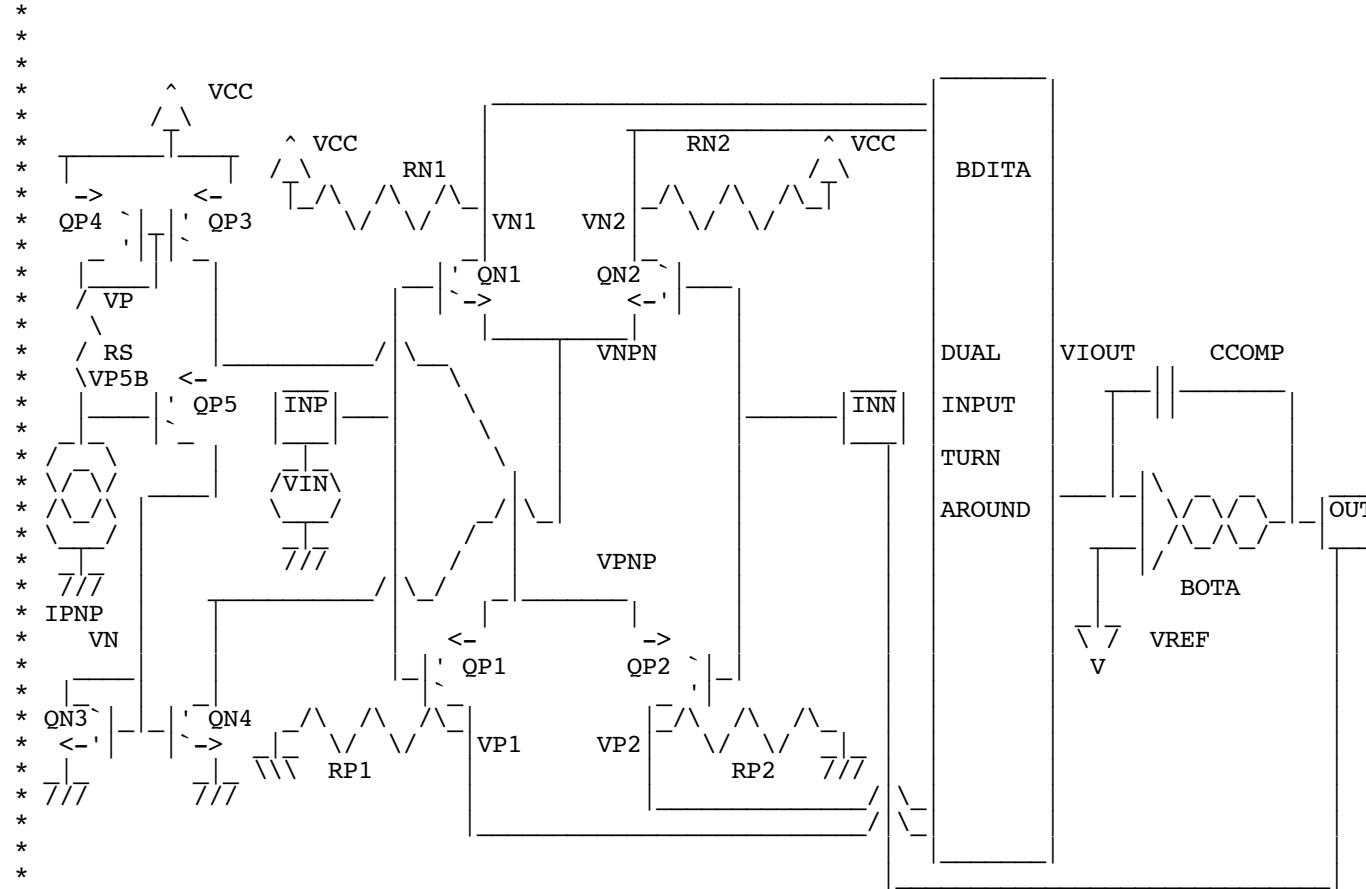


RRI_Preferred_steering

* dsauersanjose@aol.com 12/17/08

* www.idea2ic.com



.OPTIONS method=gear GMIN=1e-18

VIN	INP	0	SIN(6	6	1K)
QP1	VP1	INP	VPNP	PNPV	1.04
QP2	VP2	OUT	VPNP	PNPV	1
QP3	VPNP	VP	VCC	PNPV	1
QP4	VP	VP	VCC	PNPV	1
RP1	VP1	0	5K		
RP2	VP2	0	5K		
QN1	VN1	INP	VNP	NPNV	1.02
QN2	VN2	OUT	VNP	NPNV	1
QN3	VNP	VN	0	NPNV	1

```

QN4      VN     VN      0      NPNV    1
RN1      VCC    VN1     5K
RN2      VCC    VN2     5K

VCC      VCC    0      12
VREF     VREF    0      6
IPNP     VP5B   0      20u
RS       VP     VP5B   10k
QP5      VN     VP5B   VPPNP   PNPV    1

BDITA    VIOUT  0      I = ( V(VP2) - V(VP1) + V(VN2) - V(VN1) )/5000
BOTA     OUT    0      I = -1*( V(VIOUT) - V(VREF) )/5000
CCOMP    OUT    VIOUT  3p

.model    NPNV npn BF=150
.model    PNPV pnp BF=150
.model    PNPL pnp BF=5


.control
run
set      pensize = 2
dc       vin 0 12 100m
plot    v(out)-v(inp) title OffsetVoltageVsCommonMode
plot    v(vp1)  v(vp2) v(vcc)-v(vn1) v(vcc)-v(vn2) title TailCurrentsVsCommonMode
plot    v(vppn)-v(vp5b) title PnpEmitterBase
.endc
.end

* =====END=====


```

To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

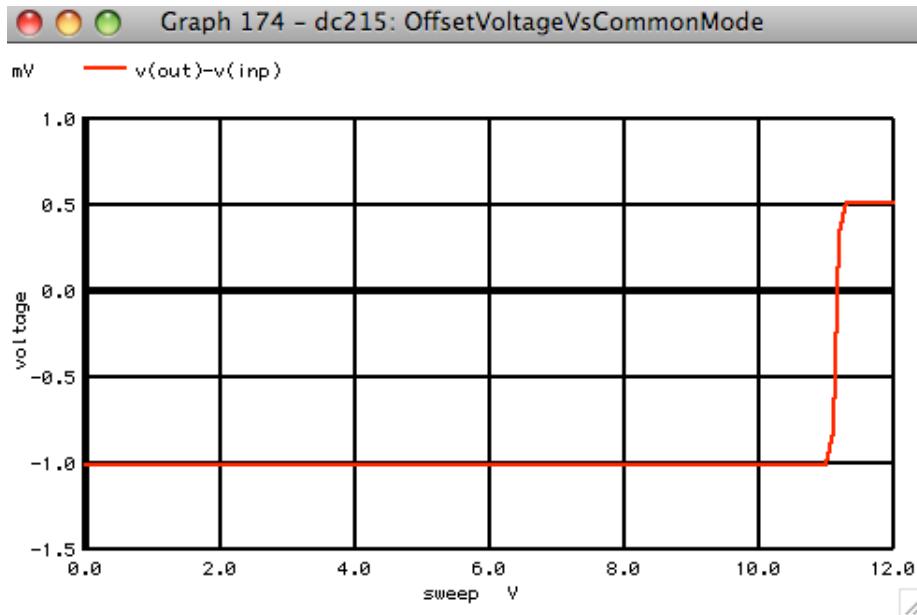
The preferred input stage is just a LM324 input stage that can swing to the positive rail. Most customers are going to be using a RRIO like a LM324, but they like the extra common mode range.



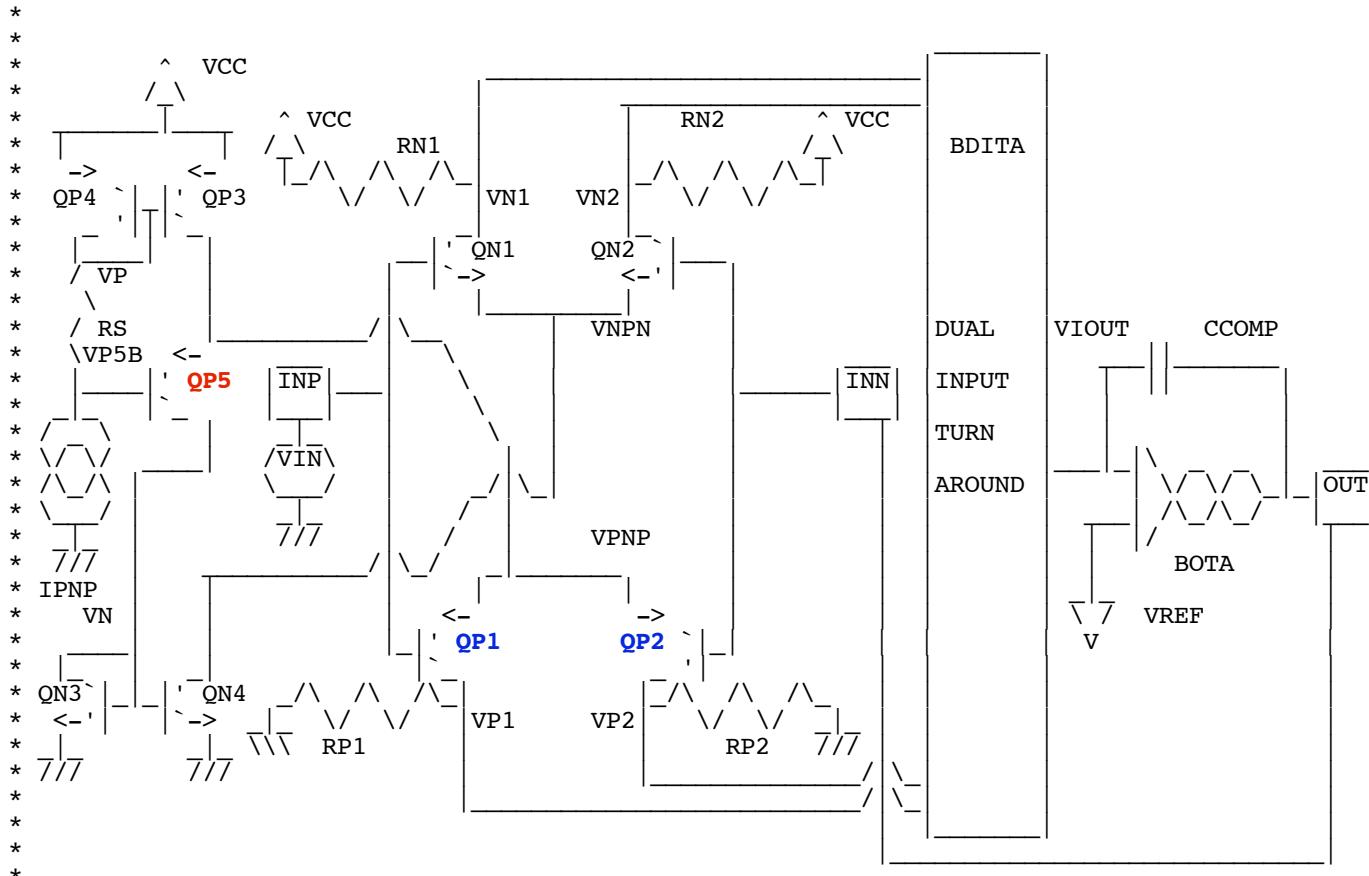
This means that there will only be one transition point where the offset voltage of the pnp's gets replaced by that of the npn's. This means some kind of current steering circuit needs to be build.



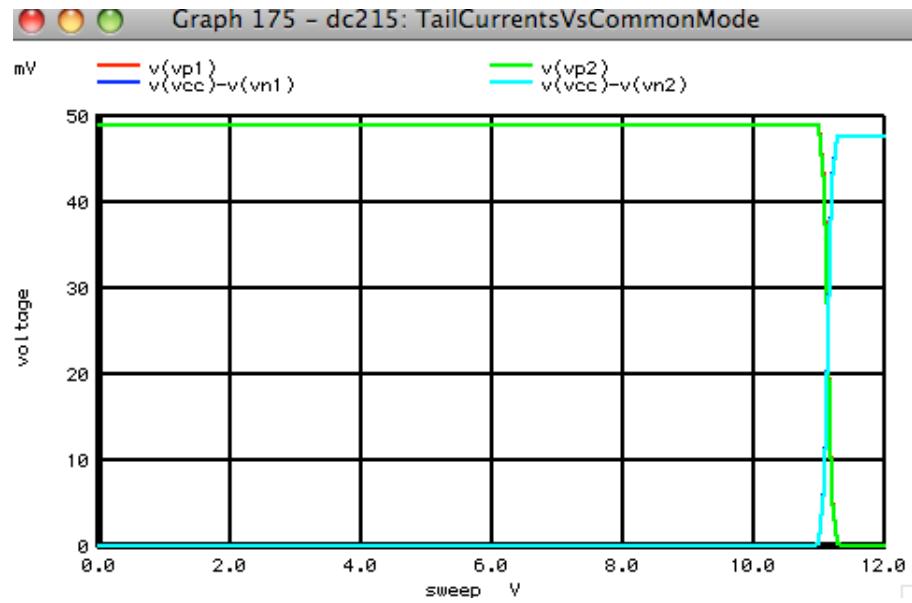Transistor QP5 can do the job all by itself. When QP1 and QP2 are low, QP5 and QN1->QN4 are all off and all current flow in QP1 and QP2. At high supply the exact opposite is true.



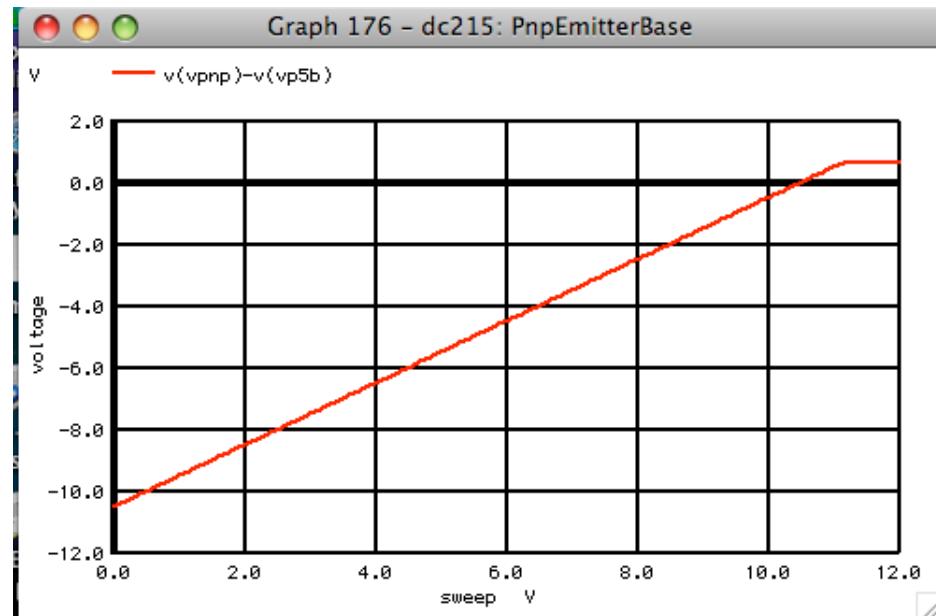The only problem is the emitter base voltage of QP5 which can get close to full supply.



That is not a problem if lateral pnps are used. The problem with that is that lateral pnps have at least a factor of ten less beta and are close to a thousand times slower than vertical pnps.

If vertical pnps are used, their emitter base voltages need to be protected. Applying a reverse voltage greater than a few volts is destructive.