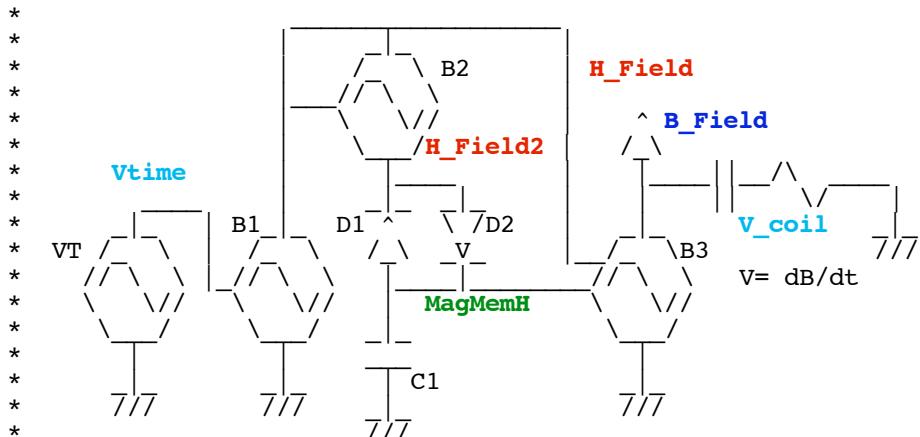


BH Almost

- * dsauersanjose@aol.com 5/07/08
- * www.idea2ic.com



```


VTime      0          PWL ( 0 0 1 1 )
B1 H_Field  0          V = v(VTime)*30*( 2*acos(cos(3.142*200*v(VTime)))-3.145)
B2 H_Field H_Field2   V = .7*v(H_Field)
D1 H_Field2 MagMemH   DD
D2 MagMemH  H_Field2 DD
C1 MagMemH  0          1p
B3 B_Field   0          V = tanh(V(H_Field)+2*V(MagMemH))
C2 B_Field   V_coil    1u
R2 V_coil   0          1
.tran .1m     .1        0        .1m
.control
run
set pensize = 1
plot v(h_field) v(magmemh) v(b_field) v(v_coil)*1000
plot v(b_field) vs v(h_field)
.endc
.model DD D(IS=3.15e-18)
.end

```

=====**END OF SPICE**=====


To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

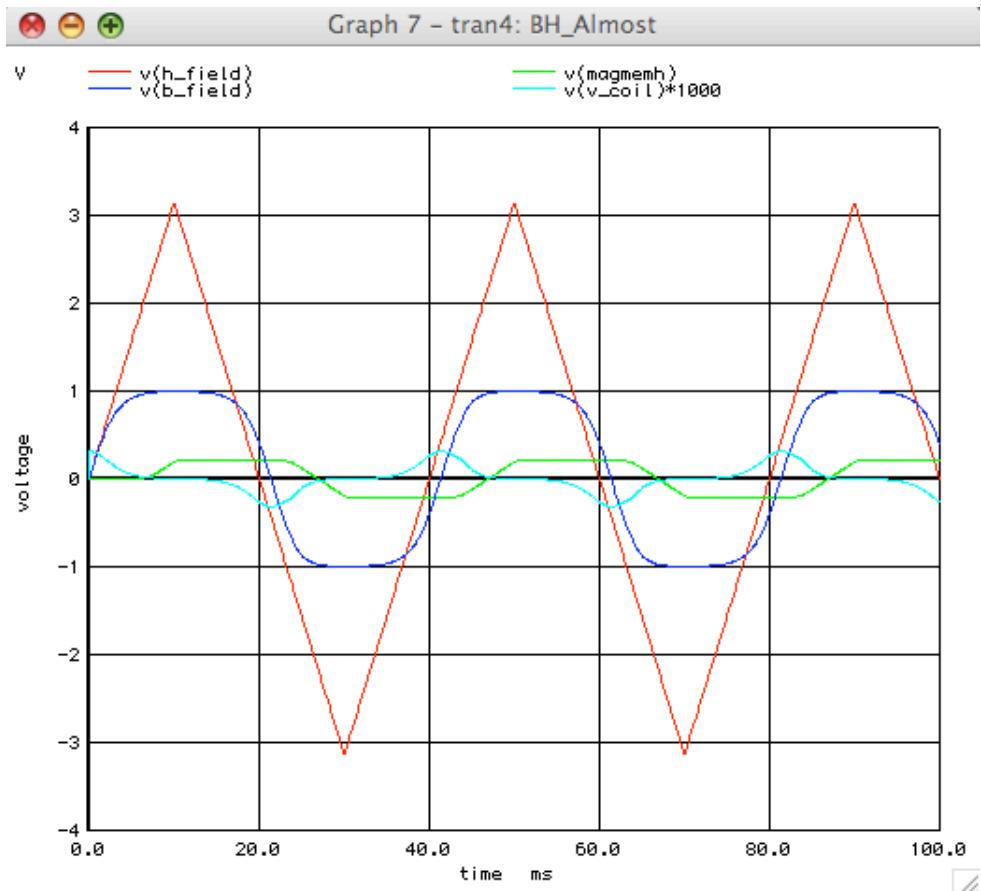The need is to somehow store what happens in the past which in this case the magnetic memory.




The store magnetic memory is used to offset the applied H_field.

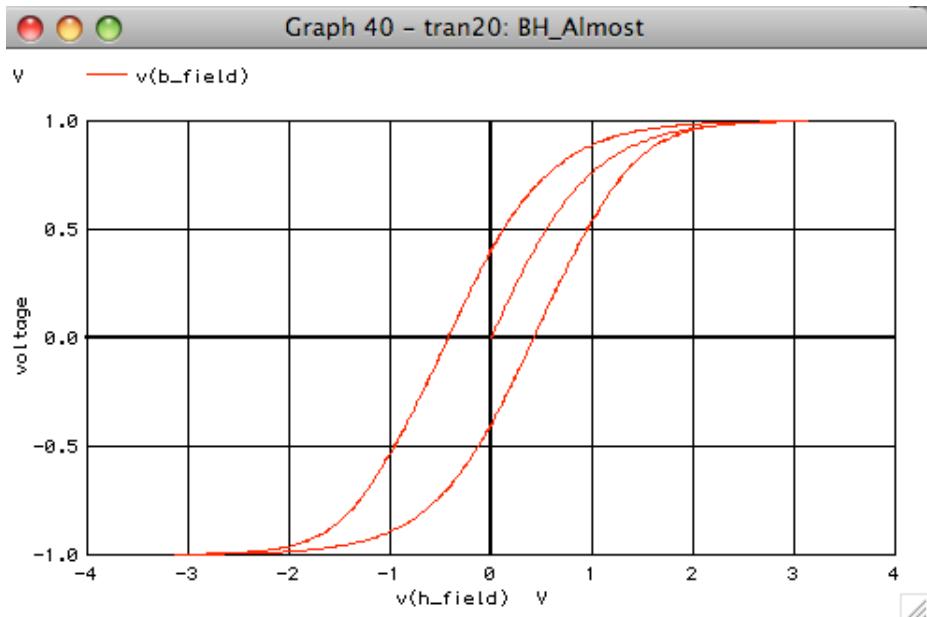The offsetted H_Field can then be put into some nonlinear function. (tanh in this case)



Using diodes and a capacitor with a variable

offset may still needs some tweeking.

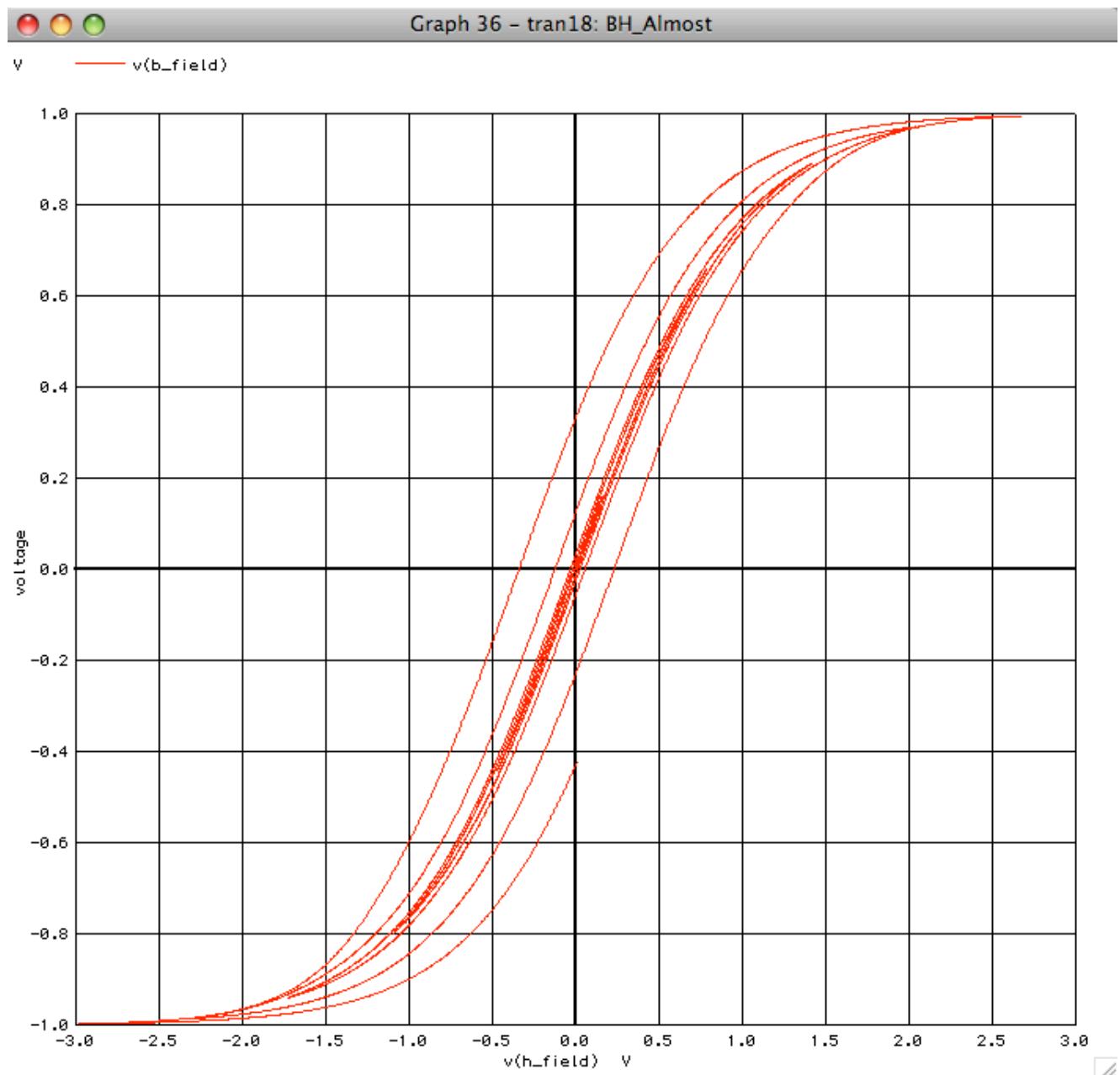

But it is not obvious why enough circuitry couldn't be added to achieve the needed correlation to a real BH curve.

*#1=====WinSpiceVersion=====

```

BH_Almost
* dsauersanjose@aol.com 5/07/08
* www.idea2ic.com
*
*
*
*
*
*
*
Vtime
*
*
*
*
*
*
VT
B1
D1
D2
MagMemH
C1
B2
H_Field2
H_Field
B3
V_coil
v= dB/dt
^ B_Field

PWL ( 0 0 1 1 )
V = 2* v(Vtime )*asin(sin(3.142*10*v(Vtime)))
V = 2* asin(sin(3.142*50*v(Vtime)))
V = .8*v(H_Field)
DD
DD
1p
V = tanh(V(H_Field)+2*V(MagMemH))
1u
1
.1m
0
.1m
.control
run
set pensize = 1
plot v(h_field) v(magmemh) v(b_field) v(v_coil)*1000
plot v(b_field) vs v(h_field)
.endc
.model DD D(IS=3.15e-18)
.end

```