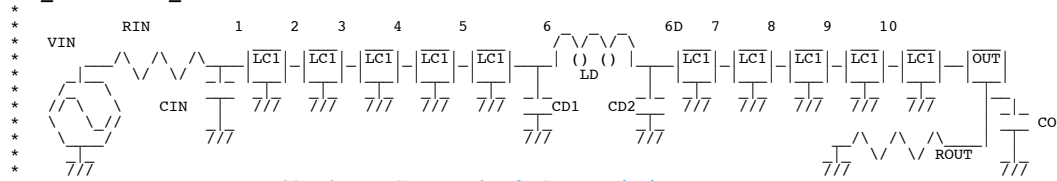


LC_transLine_Tweek



www.idea2ic.com dsauersanjose@aol.com 4/15/08

```

.OPTIONS GMIN=1e-18 METHOD=euler ABSTOL=1e-18 TEMP=27 srcsteps = 1 gminsteps = 1
VIN VIN 0 PWL( 0 0 2n 0 3.0n 1 18n 1 19.0n 0)
RIN VIN 1 50
C1 VIN 0 1.6p
XLC1 1 2 LC1
XLC2 2 3 LC1
XLC3 3 4 LC1
XLC4 4 5 LC1
XLC5 5 6 LC1
CD1 6 0 3f
LD 6 6D 16n
CD2 6D 0 3f
XLC6 6D 7 LC1
XLC7 7 8 LC1
XLC8 8 9 LC1
XLC9 9 10 LC1
XLC10 10 OUT LC1
C2 OUT 0 -1.6p

ROUT OUT 0 50
C3 OUT 0 10f
.tran 0.01n 30n 0 30n

```

***#1===What_To_Do_About_Reflection=====**

.control

***#1==First_The_Addition_Of_16nH_of_Stray_Inductance===**

run

plot v(1) v(6) out title **L_16n_1f_1f**

***#2===Then_Capacitance_Is_Added_to_tweek_It_Out==**

alter CD1 capacitance = **1.6p**

alter CD2 capacitance = **4.8p**

run

plot v(1) v(6) out title **L_16n_1.6p_4.8p**

***#3===Try_Other_Capacitance_Ratios=====**

alter CD1 capacitance = **1.8p**

alter CD2 capacitance = **5.4p**

run

plot v(1) v(6) out title **L_16n_1.8p_5.4p**

***#4===Try_Other_Capacitance_Ratios=====**

alter CD1 capacitance = **1.8p**

alter CD2 capacitance = **5.0p**

run

plot v(1) v(6) out title **L_16n_1.8p_5p**

***#5===What_Happens_With_Balanced_Capacitance_?===**

alter CD1 capacitance = **3.2p**

alter CD2 capacitance = **3.2p**

run

plot v(1) v(6) out title **L_16n_3.2p_3.2p**

.endc

.SUBCKT LC1 IN OUT

L1 IN OUT 8n

C1 OUT 0 3.2p

.ENDS LC1


But stray capacitors CD1 and CD2 are next added to get all nodes to resonate at 50 Ohms.

```
*#2===Then_Capacitance_Is_Added_to_tweek_It_Out==
```

```
alter CD1      capacitance = 1.6p
alter CD2      capacitance = 4.8p
```

```
run
```
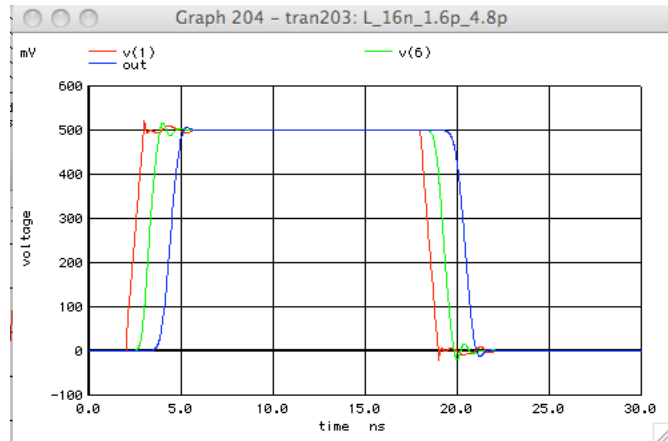
```
plot v(1) v(6) out title L_16n_1.6p_4.8p
```




```
*#3===Try_Other_Capacitance_Ratios=====
```

```
alter CD1      capacitance = 1.8p
alter CD2      capacitance = 5.4p
```

```
run
```
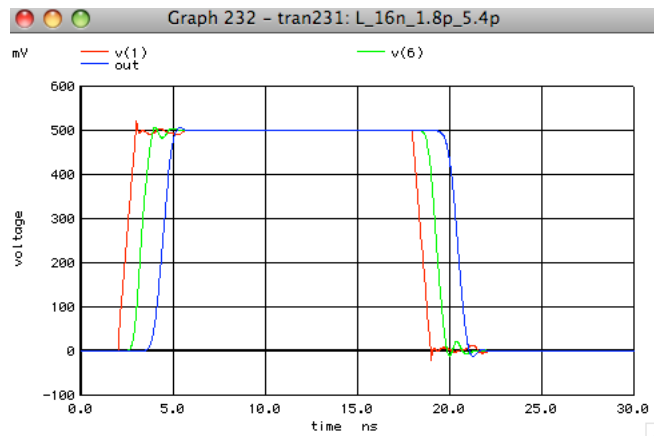
```
plot v(1) v(6) out title L_16n_1.8p_5.4p
```



```
*#4===Try_Other_Capacitance_Ratios=====
```

```
alter CD1      capacitance = 1.8p
alter CD2      capacitance = 5.0p
```

```
run
```

```
plot v(1) v(6) out title L_16n_1.8p_5p
```

```
*#5===What_Happens_With_Balanced_Capacitance_?===  
alter CD1 capacitance = 3.2p  
alter CD2 capacitance = 3.2p  
run  
plot v(1) v(6) out title L_16n_3.2p_3.2p
```

Having CD1 = CD2 does not appear to be optimum.

