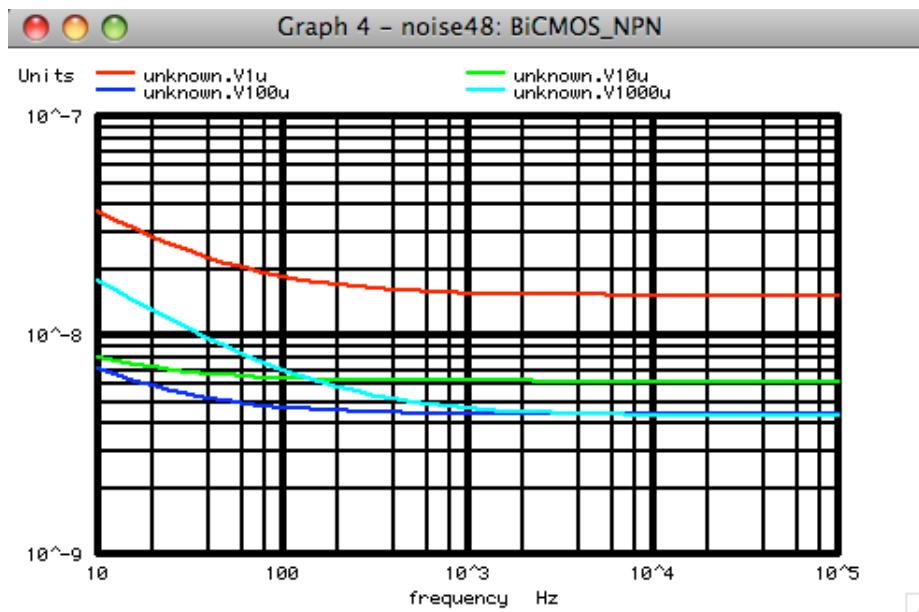


BiCMOS BJT Noise Voltage Test

=====END=====

```
.model BiCMOS_NPN npn kf=.3e-16 af=.75 bf=200 rb=1000
```

In this case the BiCmos NPN Model is showing what to expect in a BiCMOS world. The base resistance has been set to 1kOhms such that at currents above 30uA, the flat band noise should be the same as a 1KOhm resistor (4nV_per_rt_Hz). At the higher currents, the 1/f noise corner should be expected to increase in frequency.



Spice likes to think in terms of power. Therefore a square root function needs to be applied to the output noise. In the output noise is onoise_spectrum. The referred to input noise is the should equal the output noise divided by the gain.