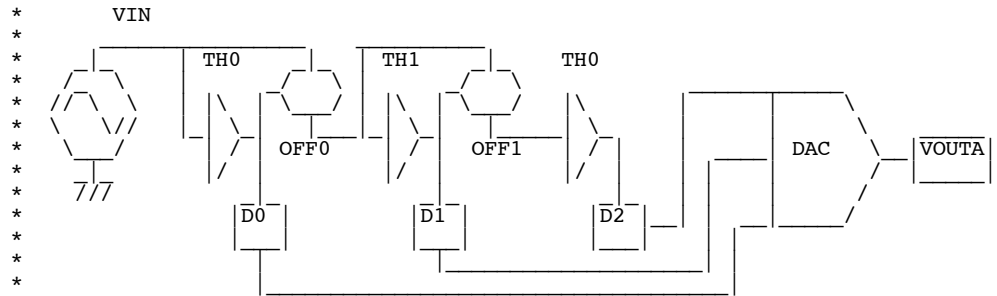


How Does OverSampling work?




Make a simple ideal non-clocked 3bit ADC/DAC.

It only takes six lines of spice code.


It will quantize signal in terms of voltage levels, but not in time.

```

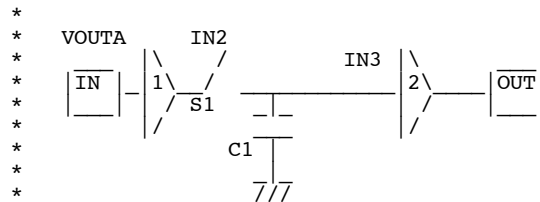
BTH0      D0      0      V =   u(V(VIN)  -1/2)
BOFF0     VIN     OFF0   V =   V(D0)/2
BTH1      D1      0      V =   u(V(OFF0) -1/4)
BOFF1     OFF0   OFF1   V =   V(D1)/4
BTH2      D2      0      V =   u(V(OFF1) -1/8)
BDAC      VOUTA  0      V =   (V(D0)/2+V(D1)/4+V(D2)/8)
    
```



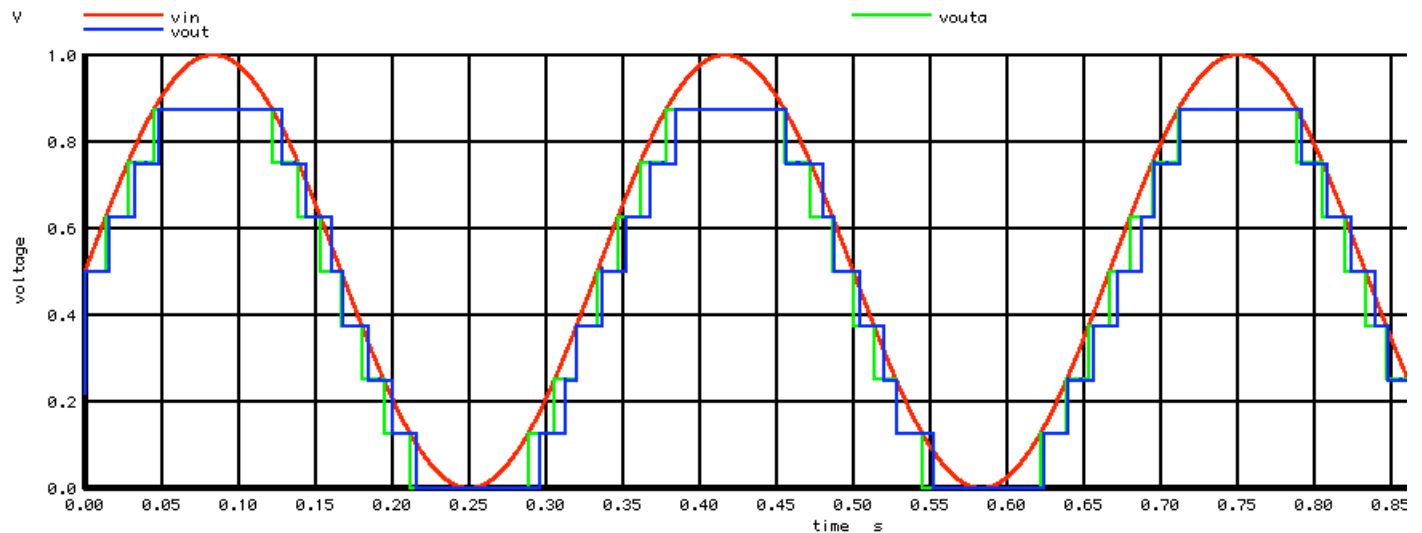Now add a sample and hold to quantize the output now in both voltage and time.
In this case, sample period is set to a 8msec rate.



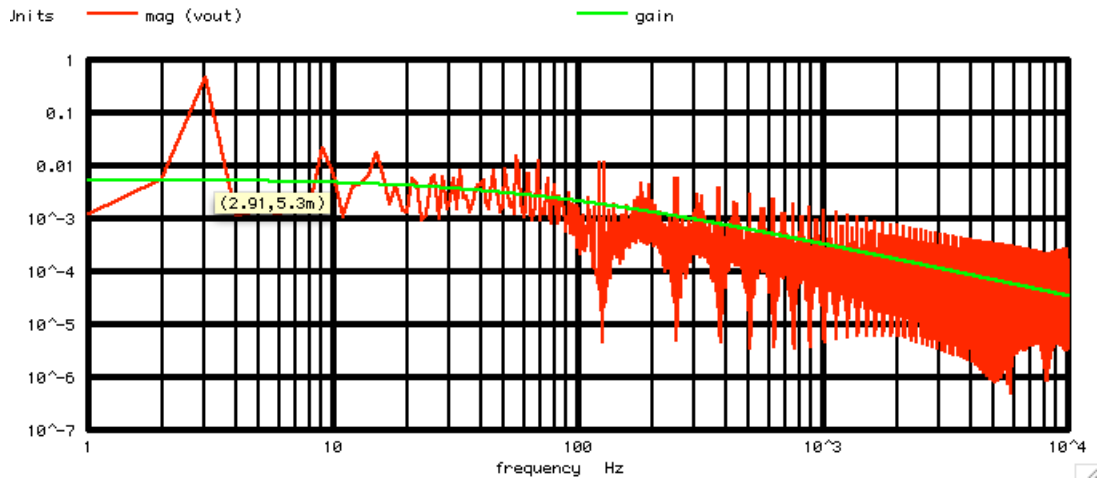
The sampling rate is low enough such that the difference between the clocked and clock-less output values are visible.



The spectrum of the quantization error is defined as per bandwidth and power. The bandwidth is defined by the nyquist of the **8msec sample rate**. The total quantization noise is set by the number of bits. The typical formula is given below.

$$\text{Signal_2_Noise_Max_db} = 6.02 * \text{Numb_Bits} + 1.76$$

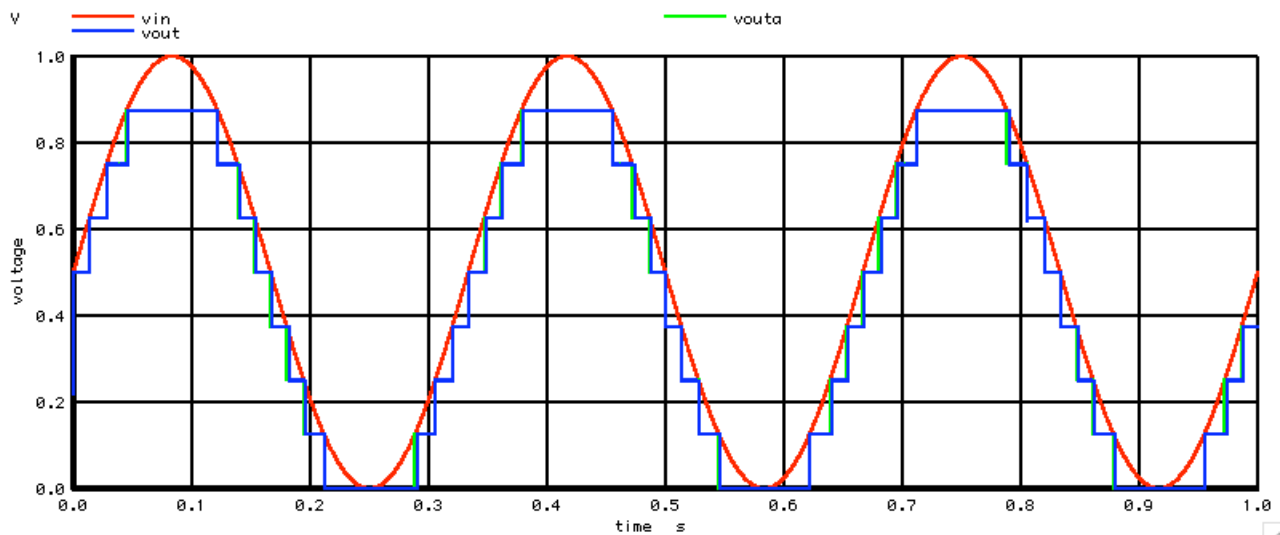This **5.3m quantization noise level** will be spread out over the full bandwidth. Since its noise, its average level drops by the square root of the bandwidth. The spectrum shows expected quantization noise level with expected bandwidth.



Now increase the sample rate by a factor of four to **2msec**.


```

BTH2      D2      0      V =      u( V(OFF1) -1/8)
BOFF2     OFF1    OFF2    V =      V(D2)/8
BTH3      D3      0      V =      u( V(OFF2) -1/16)
BOFF3     OFF2    OFF3    V =      V(D3)/16
BTH4      D4      0      V =      u( V(OFF3) -1/32)
BDAC      VOUTA  0      V =      (V(D0)/2+V(D1)/4+V(D2)/8)

.control
*TRAN      TSTEP  TSTOP  TSTART TMAX  ?UIC?
tran       .05m   1      0      .05m
set        pensize = 2
plot       vin vouta vout

*plot      vin -vout xlimit 1m 1

echo "=====FFT_and_Plot=====
linearize

let        FFT_BandWidth_Hz = 10k
let        FFT_resolution_Hz = 1
echo       "FFT_BandWidth_Hz= $&FFT_BandWidth_Hz"
echo       "FFT_resolution_Hz= $&FFT_resolution_Hz"
set        specwindow = "rectangular"
spec       $&FFT_resolution_Hz $&FFT_BandWidth_Hz $&FFT_resolution_Hz v(vout)
let        BW = 1/2m
let        gain = 1/(1 + frequency/(0.5*BW))
let        gain = gain*((.5/8)/sqrt(BW))
plot       mag (vout) gain loglog
echo "=====Done=====

.endc

*=====Sample_Hold=====
*
*
*          IN2
*          IN3
*  IN ---| 1 |--- S1 ---| 2 |--- OUT
*          |
*          C1
*          |
*          777
*
.SUBCKT    SH      IN      CNTL      OUT
B1         IN2     0          V =      v( IN )
S1         IN2     IN3       CNTL     0      SW
C1         IN3     0          .1u
R1         IN3     0          100Meg
B2         OUT     0          V =      v( IN3 )
.ENDS

*=====POS_Edge=====
*
*
*          IN
*          VBF
*          VLP
*          PE
*  IN ---| 3 |---|--- VLP ---| PE --- OUT
*          | \ \ \ \ \ \ /
*          RLP
*          CLP
*          |
*          777
*
.SUBCKT    POS_E  IN      OUT
BBUF       VBF     0          V =      u( v( IN )-.5 )
RLP        VBF     VLP       10k
CLP        VLP     0          1n      IC=0
BAND       OUT     0          V =      u( u(v(VBF) -.5)*u(.5 -v(VLP) ) ) -.1)
.ENDS

.MODEL     SW      SW(      VT=.5 VH=.1 RON=1 ROFF=100MEG)

.end

```