

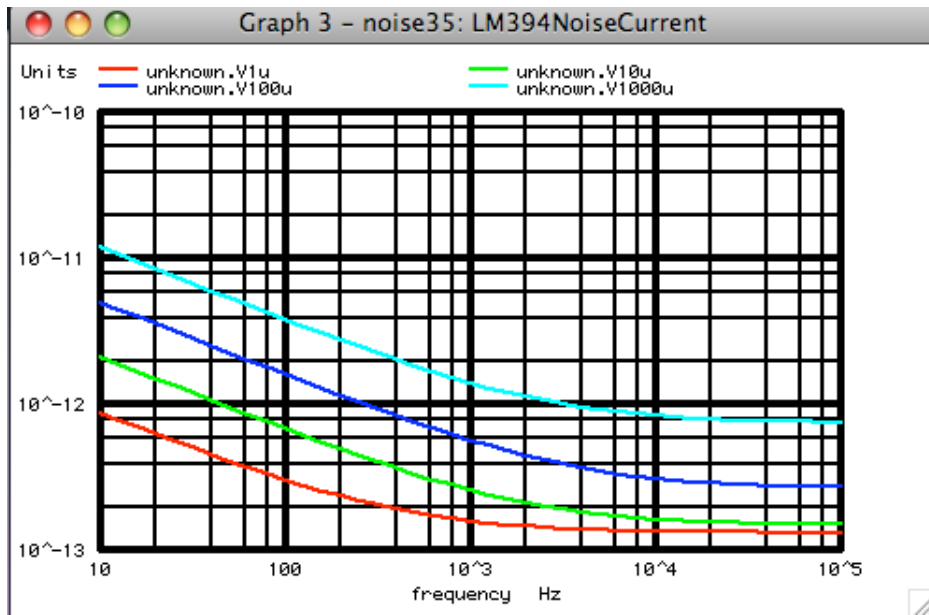

```

op
noise          v(vc) vin dec 10 10 100k 1
destroy
let            unknown.V100u = sqrt(v(onoise_spectrum))*1u
alter         I1      dc = 1000u
op
noise          v(vc) vin dec 10 10 100k 1
destroy
let            unknown.V1000u = sqrt(v(onoise_spectrum))*1u
set pensize = 2
plot unknown.V1u unknown.V10u unknown.V100u unknown.V1000u vs frequency loglog title
LM394NoiseCurrent
echo          "    ... done."
.endcontrol
.end

```


=====END=====

Noise current is measured by adding a 1MegOhm resistor in the base such that the base current noise dominates.



Spice likes to think in terms of power. Therefore a square root function needs to be applied to the output noise. In the output noise is onoise_spectrum. The referred to input noise is the should equal the output noise divided by the gain.

Base Current Noise vs Frequency

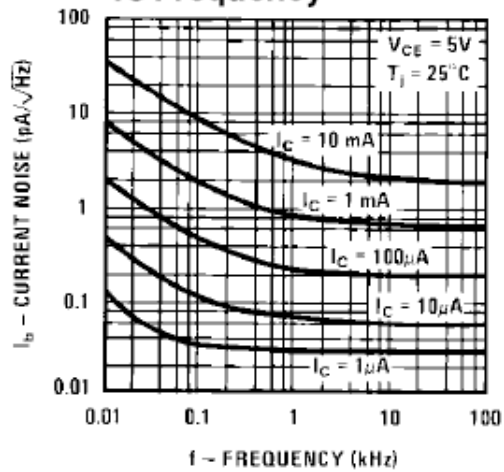

Getting the simulated base noise to track silicon is becoming difficult here. Changes in AF or KF affect each other. So there may be a trade off between the two.