
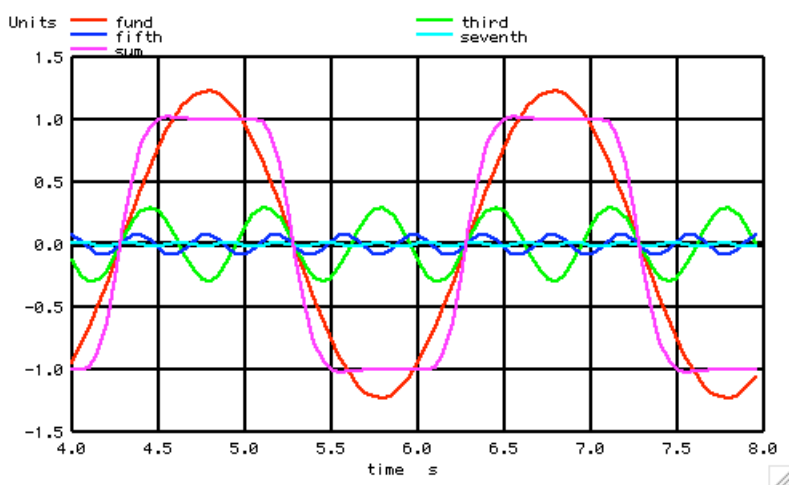


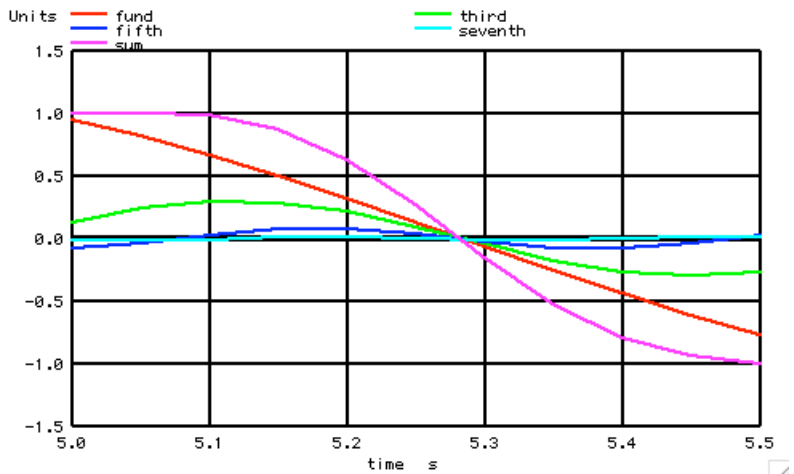The Bessel is not as good as a Butterworth in terms of magnitude.



But a Bessel does not distort the output like a Butterworth. In this case harmonics below the seventh have gotten through.




Plotting all the harmonics on the same plot shows that everything has the exact same time delay. This allows the Bessel to do a better job of rounding off the edges of a square wave without changing its shape.

So building an ideal filter involves not only ideal magnitude response, but also ideal timing or phase response.

=====**Full_Netlist_For_Copy_Paste**=====

Better_Butterworth_6P_State_Variable

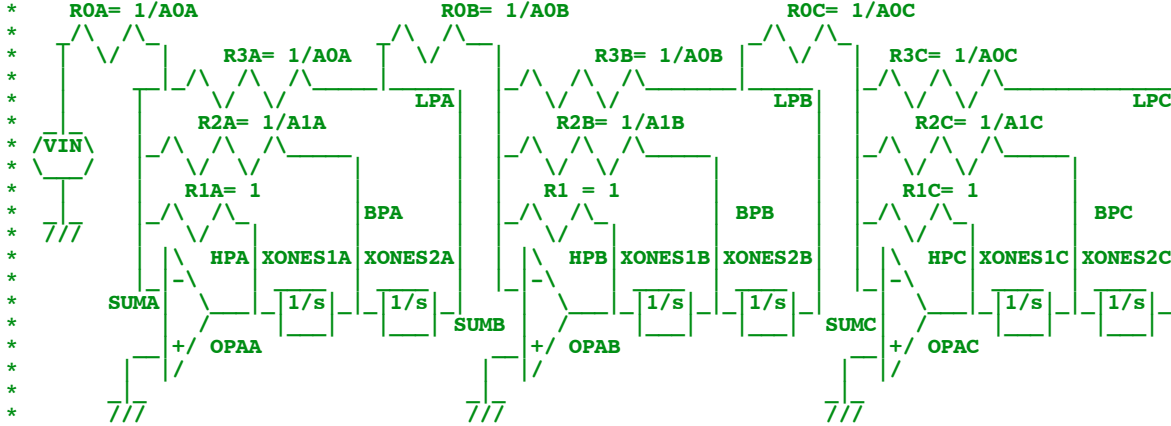* dsauersanjose@aol.com
 * www.idea2ic.com
 * 8.13.10_10.02AM




Butterworth terms

(s^2 + 0.5176s + 1)(s^2 + 1.4142s + 1)(s^2 + 1.9319s + 1)
 .OPTIONS GMIN=1e-18 METHOD=euler srcsteps = 1 gminsteps = 1

*V_PULSE#	NODE_P	NODE_N	DC	VALUE	PULSE (VINIT	VPULSE	TDELAY	TRISE	TFALL	PWIDTH	PERIOD)
V_IN	VIN	0	DC	0	PULSE (-1	1	100u	100u	100u	1	2) AC = 1
R0A	VIN	SUMA	1									
R1A	SUMA	HPA	1									
R2A	SUMA	BPA	1.9319									
R3A	SUMA	LPA	1									
BOPA1A	HPA	0	V =	5*tanh(tanh((-v(SUMA))*100)*100)								
XONES1A	HPA	BPA	ONE_S									
XONES2A	BPA	LPA	ONE_S									
R0B	LPA	SUMB	1									
R1B	SUMB	HPB	1									
R2B	SUMB	BPB	.707									
R3B	SUMB	LPB	1									
BOPA1B	HPB	0	V =	5*tanh(tanh((-v(SUMB))*100)*100)								
XONES1B	HPB	BPB	ONE_S									
XONES2B	BPB	LPB	ONE_S									
R0C	LPB	SUMC	1									
R1C	SUMC	HPC	1									
R2C	SUMC	BPC	.5176									
R3C	SUMC	LPC	1									
BOPA1C	HPC	0	V =	5*tanh(tanh((-v(SUMC))*100)*100)								
XONES1C	HPC	BPC	ONE_S									
XONES2C	BPC	LPC	ONE_S									
BinV	LPD	0	V =	-V(LPC)								

=====**Integrator_Cell**=====

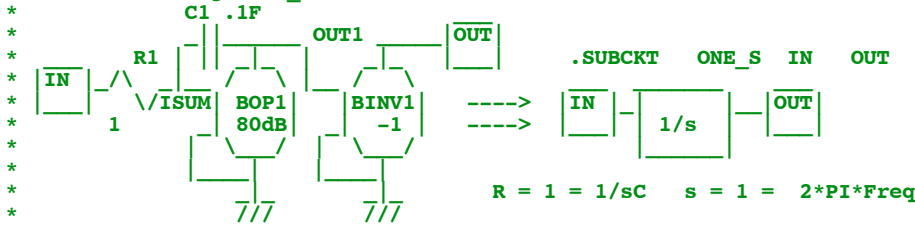

.SUBCKT	ONE_S	IN	OUT
R1	IN	ISUM	1
C1	ISUM	OUT1	.1
BOP1	OUT1	0	V = 5*tanh(tanh((-v(ISUM))*100)*100)
BINV1	OUT	0	V = -v(OUT1)

.ends

=====**A_Bessel_is_Best_for_Low_Phase_Distortion**=====


.control
 ac dec 500 .01 100
 plot db(lpc)
 *TRAN TSTEP TSTOP TSTART TMAX
 tran 50m 7.95 4 50m


```

XONES2B  BPB  LPB  ONE_S
R0C      LPB  SUMC  .389
R1C      SUMC  HPC  1
R2C      SUMC  BPC  .318
R3C      SUMC  LPC  .389
BOPA1C   HPC  0    V = 5*tanh(tanh((-v(SUMC))*100)*100)
XONES1C   HPC  BPC  ONE_S
XONES2C   BPC  LPC  ONE_S
BinV     LPD  0    V = -V(LPC)

```

=====Integrator_Cell=====

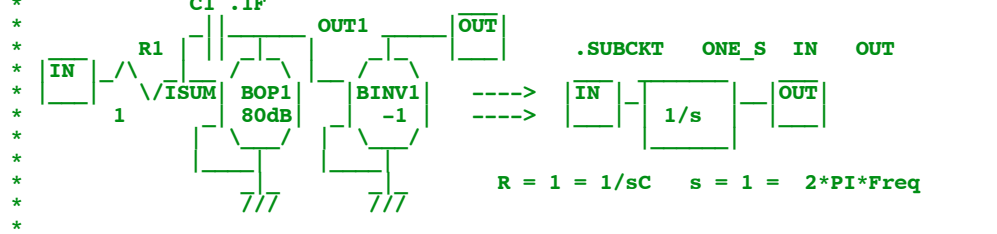

```

.SUBCKT  ONE_S  IN  OUT
R1      IN      ISUM  1
C1      ISUM    OUT1  .1
BOP1    OUT1    0      V = 5*tanh(tanh((-v(ISUM))*100)*100)
BINV1   OUT     0      V = -v(OUT1)
.ends

```

=====A_Bessel_is_Best_for_Low_Phase_Distortion=====

```

.control
ac      dec 500 .01 100
plot   db(lpc)
*TRAN  TSTEP TSTOP TSTART TMAX
tran   50m 7.95 4 50m

```

```

linearize
plot   vin lpd
let   numb2 = length(vin)
print numb2
let   t_indx2 = vector($&numb2)

let   ac = lpd +j(0)
let   ac_fft=fft(ac)
plot  real(ac_fft) imag(ac_fft) vs t_indx2

let   funbin = 2
let   unvect          = univect($&numb2)
let   fundspec        = unvect*0 +j(0)
let   fundspec[2]     = real(ac_fft[2])      +j(imag(ac_fft[2] ))
let   fundspec[numb2-2] = real(ac_fft[numb2-2]) +j(imag(ac_fft[numb2-2] ))
let   fund            = ifft(fundspec)
let   thirdspec       = unvect*0 +j(0)
let   thirdspec[6]    = real(ac_fft[6])      +j(imag(ac_fft[6] ))
let   thirdspec[numb2-6] = real(ac_fft[numb2-6]) +j(imag(ac_fft[numb2-6] ))
let   third           = ifft(thirdspec)
let   fifthspec       = unvect*0 +j(0)
let   fifthspec[10]   = real(ac_fft[10])     +j(imag(ac_fft[10] ))
let   fifthspec[numb2-10] = real(ac_fft[numb2-10]) +j(imag(ac_fft[numb2-10] ))
let   fifth           = ifft(fifthspec)
let   seventhspec     = unvect*0 +j(0)
let   seventhspec[14] = real(ac_fft[14])     +j(imag(ac_fft[14] ))
let   seventhspec[numb2-14] = real(ac_fft[numb2-14]) +j(imag(ac_fft[numb2-14] ))
let   seventh         = ifft(seventhspec)
let   sum = fund + third + fifth + seventh
set   scale time
plot  fund third fifth seventh sum

plot  fund third fifth seventh sum xlimit 5 5.5
.endc

```

.end