
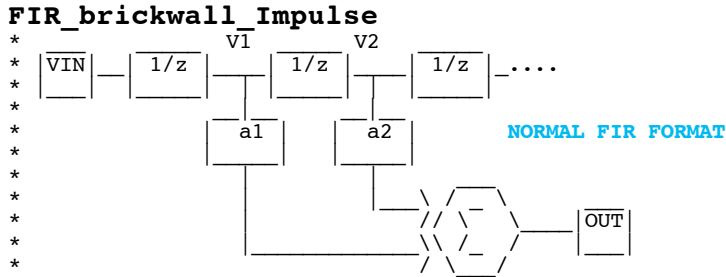


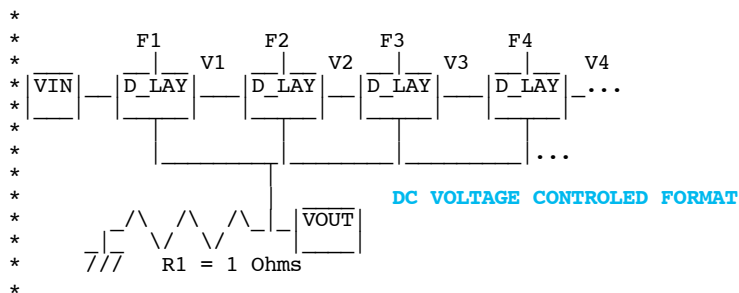
====FIR_brickwall_Impulse_DC_Controlled====



A digital filter can approximate the impulse response of a brickwall filter by putting the signal through a series of time delays and feeding a scaled version from each delay point to a common summing point.




 This spice simulation will be using delay blocks which receives an external DC scale voltage to scale an output current. This method makes it easy to connect and scale a large number of delay points.



This simulation will use 31 amplitude scaled delay blocks to match a sinc response. The delay point at the 16th stage is simply the input signal with 16 clock delays. While it is not possible to have a impulse response happen before the impulse arrives, the output will look that ways from 16th's stage point of view.

=====SCALED_DELAY=====

 

```
.SUBCKT S_DLAY VIN VOUT IOUT CLK F1
XZ_DLAY VIN VOUT CLK Z_DLAY
BOUT IOUT 0 I = -V(VOUT)*V(F1)
.ENDS S_DLAY
```

The delay block (**Z_DLAY**) just delays its input to its output by one clock cycle (**CLK**). Making the output be a current which scales the delayed output to a DC input (**F1**) makes constructing the array much easier.

=====Input_Signals=====


```
*V_PULSE NODE_P NODE_N DC VALUE PULSE( VINIT VPULSE TDELAY TRISE TFALL PWIDTH PERIOD )
VIN VIN 0 DC 0 PULSE( 0 1 .1 1u 1u 20m 33 )
VT VT 0 DC 0 PWL( 0 0 100 100)
VFIN FIN 0 DC 1
VFC FC 0 DC 1
VFS FS 0 DC 50
BVCLK CLK 0 V = u(sin(6.283*V(FS)*V(VT)))
BF12 F12A 0 V = 2*sin(3.14*V(FC)/V(FS))
```

The various clock and frequencies can be made DC variable as well.

=====SCALED_DELAY=====

```
XZ_DLAY VIN VINZ CLK Z_DLAY
XS_DLAY1 VINZ V1 VOUT CLK F17 S_DLAY
XS_DLAY2 V1 V2 VOUT CLK F16 S_DLAY
XS_DLAY3 V2 V3 VOUT CLK F15 S_DLAY
XS_DLAY4 V3 V4 VOUT CLK F14 S_DLAY
XS_DLAY5 V4 V5 VOUT CLK F13 S_DLAY
XS_DLAY6 V5 V6 VOUT CLK F12 S_DLAY
XS_DLAY7 V6 V7 VOUT CLK F11 S_DLAY
XS_DLAY8 V7 V8 VOUT CLK F10 S_DLAY
XS_DLAY9 V8 V9 VOUT CLK F9 S_DLAY
XS_DLAY10 V9 V10 VOUT CLK F8 S_DLAY
XS_DLAY11 V10 V11 VOUT CLK F7 S_DLAY
XS_DLAY12 V11 V12 VOUT CLK F6 S_DLAY
XS_DLAY13 V12 V13 VOUT CLK F5 S_DLAY
XS_DLAY14 V13 V14 VOUT CLK F4 S_DLAY
XS_DLAY15 V14 V15 VOUT CLK F3 S_DLAY
XS_DLAY16 V15 V16 VOUT CLK F2 S_DLAY
XS_DLAY17 V16 V17 VOUT CLK F3 S_DLAY
XS_DLAY18 V17 V18 VOUT CLK F4 S_DLAY
XS_DLAY19 V18 V19 VOUT CLK F5 S_DLAY
XS_DLAY20 V19 V20 VOUT CLK F6 S_DLAY
XS_DLAY21 V20 V21 VOUT CLK F7 S_DLAY
XS_DLAY22 V21 V22 VOUT CLK F8 S_DLAY
XS_DLAY23 V22 V23 VOUT CLK F9 S_DLAY
XS_DLAY24 V23 V24 VOUT CLK F10 S_DLAY
XS_DLAY25 V24 V25 VOUT CLK F11 S_DLAY
XS_DLAY26 V25 V26 VOUT CLK F12 S_DLAY
XS_DLAY27 V26 V27 VOUT CLK F13 S_DLAY
XS_DLAY28 V27 V28 VOUT CLK F14 S_DLAY
XS_DLAY29 V28 V29 VOUT CLK F15 S_DLAY
XS_DLAY30 V29 V30 VOUT CLK F16 S_DLAY
XS_DLAY31 V30 V31 VOUT CLK F17 S_DLAY
```

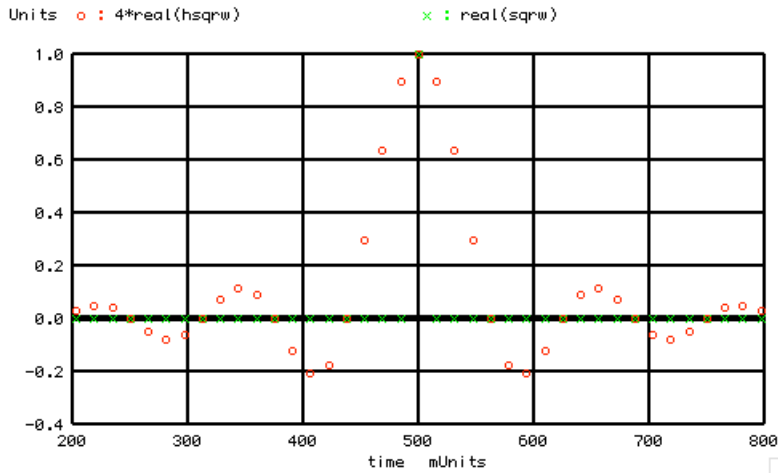The 31 delay blocks are shown above. Since the impulse response is symmetrical over time, only half as many DC voltages (F0->F17) are needed. This is were having a normalize print out of a sinc function comes in handy.




=====SCALED_DELAY=====

VF1	F1	0	DC	0
VF2	F2	0	DC	+1.000
VF3	F3	0	DC	+0.900
VF4	F4	0	DC	+0.640
VF5	F5	0	DC	+0.300
VF6	F6	0	DC	+0.000
VF7	F7	0	DC	-0.175
VF8	F8	0	DC	-0.207
VF9	F9	0	DC	-0.125
VF10	F10	0	DC	+0.000
VF11	F11	0	DC	+0.096
VF12	F12	0	DC	+0.118
VF13	F13	0	DC	+0.075
VF14	F14	0	DC	+0.000
VF15	F15	0	DC	-0.060
VF16	F16	0	DC	-0.080
VF17	F17	0	DC	-0.060

The 17 DC scaling voltages are shown above. In this format, the FIR filter can be changed by simply changing these DC scaling voltages.

=====SCALED_DELAY=====


 
```
*TRAN      TSTEP  TSTOP  TSTART  TMAX   ?UIC?
.tran      30u    1      0       30u   UIC
.control
run
set        pensize = 2
plot      v16  vout
.endc
```



Simulating the sinc impulse response is straight forward.

=====Full_Netlist_For_Copy_Paste=====

FIR_brickwall_Impulse

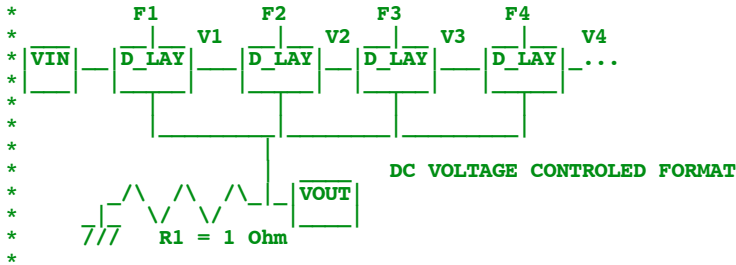 

=====Create_Signal=====

*V_PULSE	NODE_P	NODE_N	DC	VALUE	PULSE(VINIT	VPULSE	TDELAY	TRISE	TFALL	PWIDTH	PERIOD)
VIN	VIN	0	DC	0	PULSE(0	1	.1	1u	1u	20m	33)
VT	VT	0	DC	0	PWL(0	0	100	100)			
VFIN	FIN	0	DC	1							
VFC	FC	0	DC	1							
VFS	FS	0	DC	50							
BVCLK	CLK	0	V	=	u(sin(6.283*V(FS)*V(VT)))						
BF12	F12A	0	V	=	2*sin(3.14*V(FC)/V(FS))						
VF1	F1	0	DC	0							
VF2	F2	0	DC	+1.000							
VF3	F3	0	DC	+0.900							
VF4	F4	0	DC	+0.640							
VF5	F5	0	DC	+0.300							
VF6	F6	0	DC	+0.000							
VF7	F7	0	DC	-0.175							
VF8	F8	0	DC	-0.207							
VF9	F9	0	DC	-0.125							
VF10	F10	0	DC	+0.000							
VF11	F11	0	DC	+0.096							
VF12	F12	0	DC	+0.118							
VF13	F13	0	DC	+0.075							
VF14	F14	0	DC	+0.000							
VF15	F15	0	DC	-0.060							
VF16	F16	0	DC	-0.080							
VF17	F17	0	DC	-0.060							
XZ_DLAY	VIN	VINZ	CLK		Z_DLAY						
XS_DLAY1	VINZ	V1	VOUT	CLK	F17	S_DLAY					
XS_DLAY2	V1	V2	VOUT	CLK	F16	S_DLAY					
XS_DLAY3	V2	V3	VOUT	CLK	F15	S_DLAY					
XS_DLAY4	V3	V4	VOUT	CLK	F14	S_DLAY					
XS_DLAY5	V4	V5	VOUT	CLK	F13	S_DLAY					
XS_DLAY6	V5	V6	VOUT	CLK	F12	S_DLAY					
XS_DLAY7	V6	V7	VOUT	CLK	F11	S_DLAY					
XS_DLAY8	V7	V8	VOUT	CLK	F10	S_DLAY					
XS_DLAY9	V8	V9	VOUT	CLK	F9	S_DLAY					
XS_DLAY10	V9	V10	VOUT	CLK	F8	S_DLAY					
XS_DLAY11	V10	V11	VOUT	CLK	F7	S_DLAY					
XS_DLAY12	V11	V12	VOUT	CLK	F6	S_DLAY					
XS_DLAY13	V12	V13	VOUT	CLK	F5	S_DLAY					
XS_DLAY14	V13	V14	VOUT	CLK	F4	S_DLAY					
XS_DLAY15	V14	V15	VOUT	CLK	F3	S_DLAY					
XS_DLAY16	V15	V16	VOUT	CLK	F2	S_DLAY					
XS_DLAY17	V16	V17	VOUT	CLK	F3	S_DLAY					
XS_DLAY18	V17	V18	VOUT	CLK	F4	S_DLAY					
XS_DLAY19	V18	V19	VOUT	CLK	F5	S_DLAY					
XS_DLAY20	V19	V20	VOUT	CLK	F6	S_DLAY					
XS_DLAY21	V20	V21	VOUT	CLK	F7	S_DLAY					
XS_DLAY22	V21	V22	VOUT	CLK	F8	S_DLAY					
XS_DLAY23	V22	V23	VOUT	CLK	F9	S_DLAY					
XS_DLAY24	V23	V24	VOUT	CLK	F10	S_DLAY					
XS_DLAY25	V24	V25	VOUT	CLK	F11	S_DLAY					

```


XS_DLAY26 V25    V26    VOUT    CLK    F12    S_DLAY
XS_DLAY27 V26    V27    VOUT    CLK    F13    S_DLAY
XS_DLAY28 V27    V28    VOUT    CLK    F14    S_DLAY
XS_DLAY29 V28    V29    VOUT    CLK    F15    S_DLAY
XS_DLAY30 V29    V30    VOUT    CLK    F16    S_DLAY
XS_DLAY31 V30    V31    VOUT    CLK    F17    S_DLAY
R1        VOUT    0      .5
.tran     30u    1      0      30u    UIC
.control
run
*TRAN     TSTEP   TSTOP   TSTART  TMAX   ?UIC?
*tran     10u     2       0       10u
set       pensize = 2
plot     v16 vout

```

```

.endc
=====Switch_Model=====
.MODEL    SW      SW(      VT=.5 VH=.1 RON=100m ROFF=100MEG)
*=====SCALED_DELAY=====
*
*        CLK
*
*

```

 

```



.SUBCKT   S_DLAY VIN    VOUT  IOUT  CLK  F1
XZ_DLAY  VIN    VOUT   CLK  Z_DLAY
BOUNT    IOUT  0      I = -V(VOUT)*V(F1)
.ENDS
S_DLAY

```

```

=====Z_DLAY=====
*
*

```

  

```

.SUBCKT   Z_DLAY VIN    OUT    CLK
B1        VBF    0      V = u( v(CLK )-.5 )
R1        VBF    VLP    10k
CLP       VLP    0      50n    IC=0
BNOR2    NE     0      V = 1-u( u(v(VBF )-.5)+u(.5 -v(VLP ) ) -.1)
BAND3    PE     0      V = u( u(v(VBF )-.5)*u(.5 -v(VLP ) ) -.1)
B4        V1     0      V = V(VIN)
S1        V1     V2     NE     0      SW
R1        V2     0      100Meg
C1        V2     0      1u
B5        V3     0      V = V(V2)
S2        V3     V4     PE     0      SW
R2        V4     0      100Meg
C2        V4     0      100u
B6        OUT    0      V = V(V4)
.ENDS
Z_DLAY

```

```

.end

```

6.7.11_12.09PM
dsauersanjose@aol.com
Don Sauer