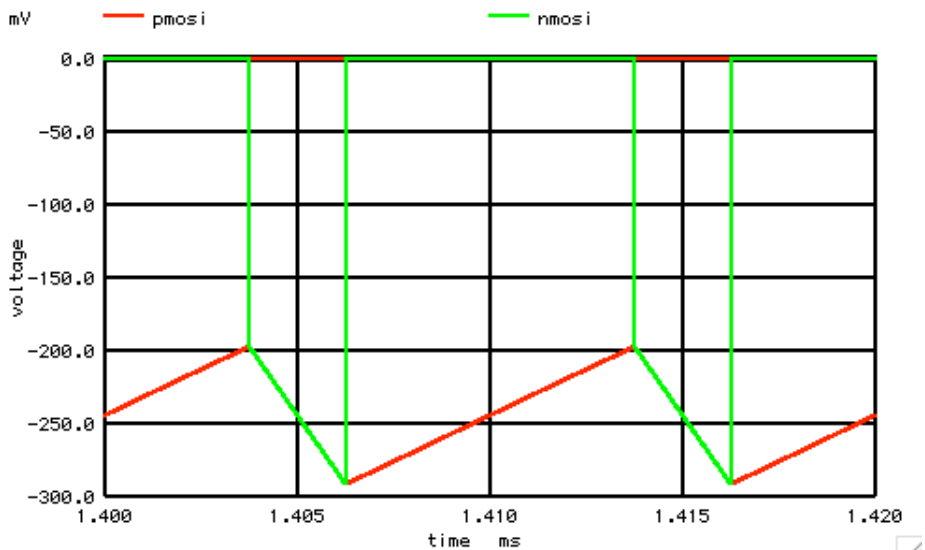


=====
 The currents flowing in VCC and VEE can be found and plotted to show that there is a 75% multiplexing of the 250mA of current flowing in RL. And for VCC, the current coming out is negative polarity. In other words the current is actually going in. In the case of VCC being a battery, VCC is getting charged up.

The current is also flowing into VEE. But since this is the negative node of VEE, VEE is being discharged.

=====

```
let      pmosi = (vcc-vp)*1000k
let      nmosi = (vee-vn)*1000k
let      rout_i = (out-vcn)/vrout[0]
plot    pmosi  nmosi  xlimit 1.4m 1.42m
```



A little math processing comes in handy to show what all is going on.

```

let      pmospwr= pmosi*(vcc-vout)
let      nmospwr= nmosi*(vout-vee)
let      pmospwrdc=mean(pmospwr)
let      nmospwrdc=mean(nmospwr)
echo     "pmospwrdc =${&pmospwrdc}  nmospwrdc =${&nmospwrdc}"

let      outdc=mean(out)
let      vcmdc = vcm[0]
let      routdc =mean(vrout[0])
let      routidc = mean(rout_i)

let      pmosidc = mean(pmosi)
let      nmosidc = mean(nmosi)
let      vccpwr=  mean((pmosi)*vcc[0])
let      veepwr=  mean((nmosi)*vee[0])
let      vcmpwr=  -1*routidc*vcm[0]
let      routpwr  =  routidc*routidc*routdc

let      pwrsupply = vccpwr +veepwr
let      pwrEff    = routpwr/pwrsupply
echo     "pwrsupply =${&pwrsupply}"


echo     "outdc =${&outdc}  rload =${&routdc}  routidc =${&routidc}  pmosidc =${&pmosidc}  nmosidc
=${&nmosidc}  "
echo     "vccpwr =${&vccpwr}  vcmpwr =${&vcmpwr}  veepwr =${&veepwr}  routpwr =${&routpwr}  vcmdc
=${&vcmdc}  "

.endc
.end

```


For the case of VCM = +2.5V and 75% duty cycle.
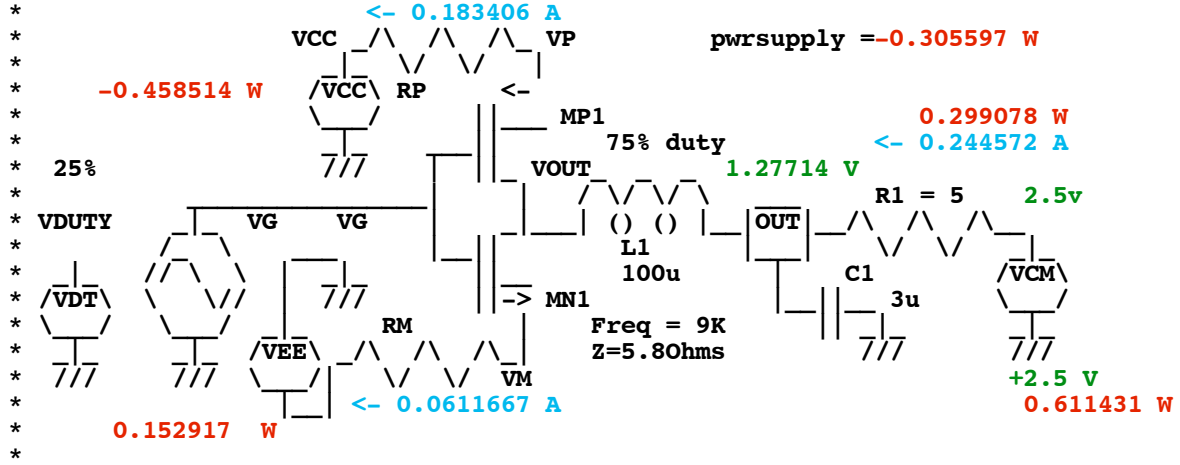
```
Circuit: ClassD_DC_DualSupply
pmspwrdc =0.00441995  nmospwrdc =-0.00229973
pwrsupply =-0.305597
outdc =1.27714  rload =5  routidc =-0.244572  pmosidc =-0.183406  nmosidc =-0.0611667
vccpwr =-0.458514  vcmpwr =0.611431  veepwr =0.152917  routpwr =0.299078  vcmdc =2.5
```



It looks like node OUT is around 1.25V and for a current in of around 250mA. In other words the V to I relationship at the OUT node is that of a 5 Ohm resistor.

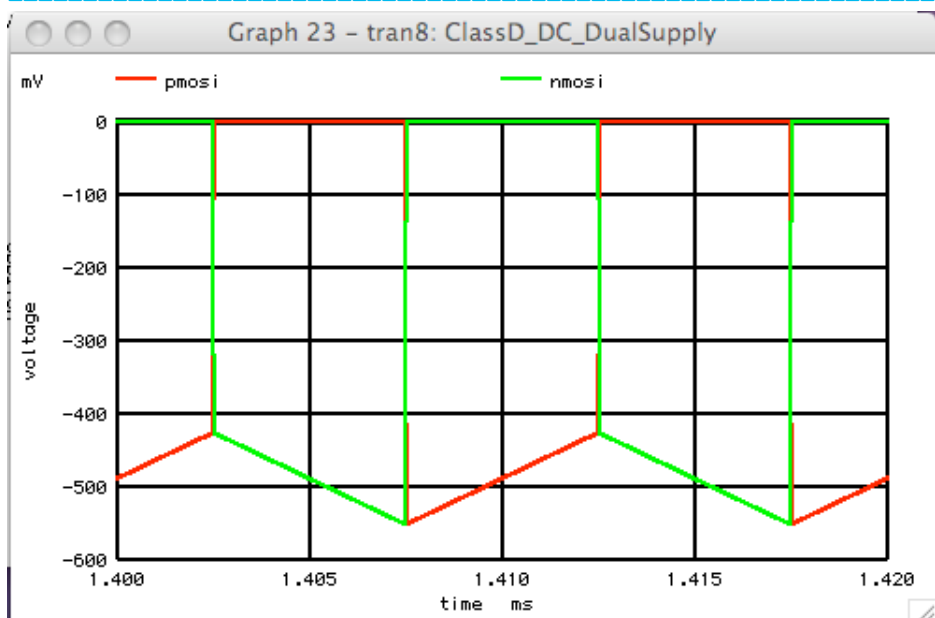Power supply VEE is supplying around 625mW of power, half of which is dissipated by RL. So node OUT is receiving the other half of that power. It looks like VEE is getting charge up and Vee is getting discharge. But it look likes there is a net charging for the two supplies which equal the power that node OUT is absorbing.





For the case of VCM = +2.5V and 50% duty cycle. Now VCM is supplying about 1.25W of power and RL is receiving it all.

Now about **500mA** is flowing into output node OUT. But since it is at zero volts, it is absorbing little power.

Now Vee is still getting discharged and Vcc charges, but both at a equal and opposite value. So there is no net charge to the two supplies, but there is a high efficiency transfer of power between the two supplies.
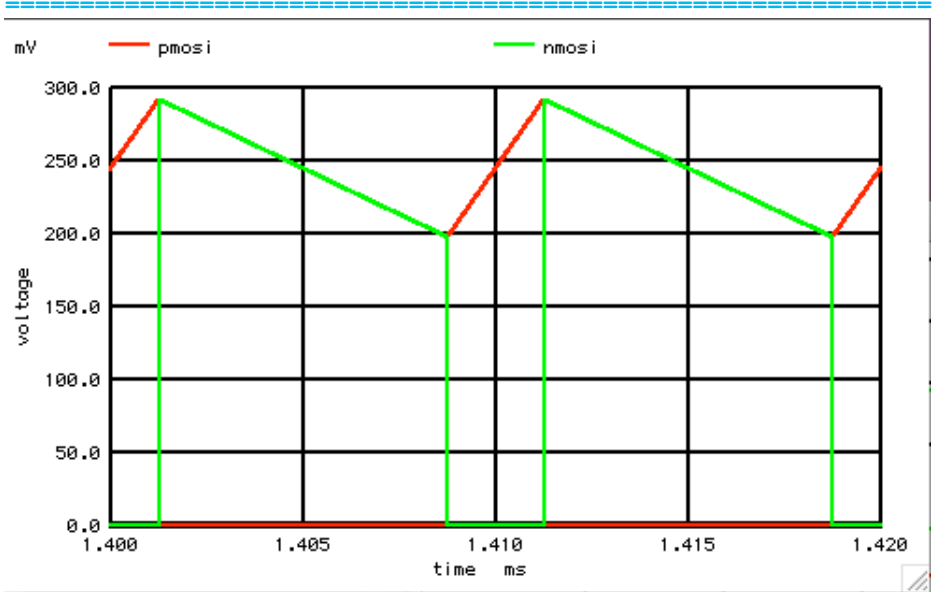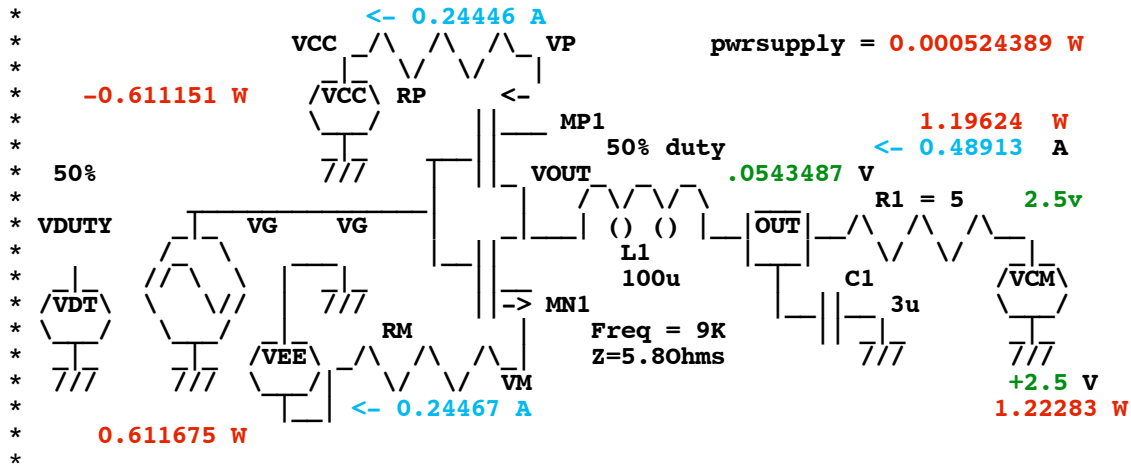
```
pmospwrdc =0.0120588  nmospwrdc =-0.0146741
pwrsupply =0.000524389
outdc =0.0543487  rload =5  routidc =-0.48913  pmosidc =-0.24446  nmosidc =-0.24467
vccpwr =-0.611151  vcmpwr =1.22283  veepwr =0.611675  routpwr =1.19624  vcmdc =2.5
```



For the case of VCM = **-2.5V** and 25% duty cycle. Now VCM is supplying about **625W** of power and RL is receiving half. Now about **250mA** is flowing out of output node OUT. The output Node OUT is again acting like a resistor in terms of voltage, current and power, and the net power is being transferred to the supplies. But in this case Vcc is getting discharged.

```
pmospwrdc =0.00229985  nmospwrdc =-0.00442002
pwrsupply =-0.30559
```



```

*TRAN      TSTEP  TSTOP  TSTART TMAX  ?UIC?
tran      .01u   2m     1m     .01u
linearize
set       pensize = 2
plot     vout out

plot     vcc mean(vp)
plot     vee mean(vn)

let      pmosi = (vcc-vp)*1000k
let      nmosi = (vee-vn)*1000k
let      rout_i = (out-vcm)/vrout[0]
plot     pmosi nmosi xlimit 1.4m 1.42m
let      pmospwr= pmosi*(vcc-vout)
let      nmospwr= nmosi*(vout-vee)
let      pmospwrdc=mean(pmospwr)
let      nmospwrdc=mean(nmospwr)
echo     "pmospwrdc =${&pmospwrdc}  nmospwrdc =${&nmospwrdc}"

let      outdc = mean(out)
let      vcm dc = vcm[0]
let      routdc =mean(vrout[0])
let      routidc = mean(rout_i)
let      pmosidc = mean(pmosi)
let      nmosidc = mean(nmosi)
let      vccpwr= mean((pmosi)*vcc[0])
let      veepwr= mean((nmosi)*vee[0])
let      vcmpwr= -1*routidc*vcm[0]
let      routpwr = routidc*routidc*routdc

let      pwrsupply = vccpwr +veepwr
let      pwrEff = routpwr/pwrsupply
echo     "pwrsupply =${&pwrsupply} "

echo     "outdc =${&outdc}  rload =${&routdc} routidc =${&routidc}  pmosidc =${&pmosidc} nmosidc =
${&nmosidc} "
echo     "vccpwr =${&vccpwr} vcmpwr =${&vcmpwr} veepwr =${&veepwr}  routpwr =${&routpwr} vcm dc =
${&vcm dc} "

*plot     pmosi nmosi pmosidc nmosidc xlimit 1m 1.004m
*plot     vout out xlimit 1m 1.004m
*plot     pmospwr nmospwr pmospwrdc nmospwrdc xlimit 1m 1.004m ylimit -20m 20m

.endc

.end

```

9.16.10_1.59PM
dsauersanjose@aol.com
Don Sauer