
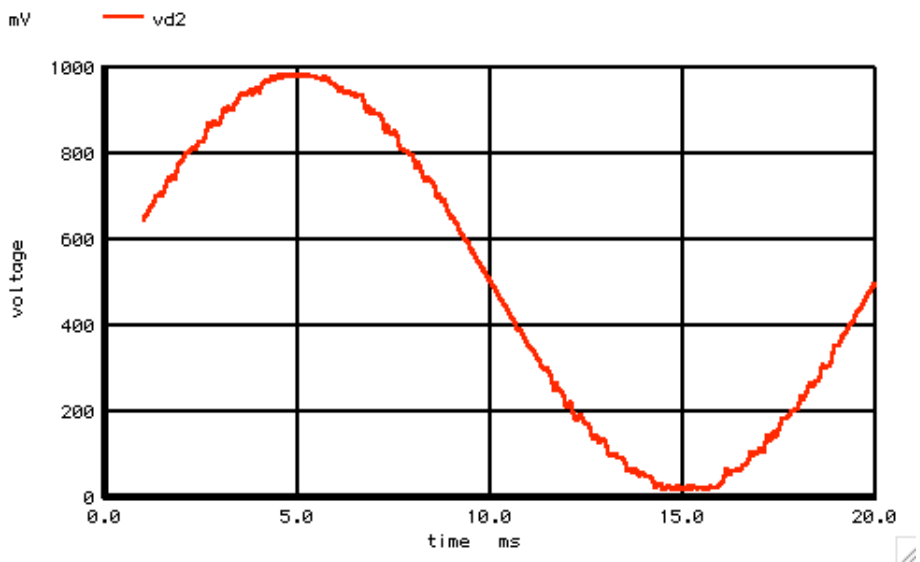



```

L1      VOUT  OUT   100u
C1      OUT  0     3u
RS      OUT  IS    1m
Rout    IS   VCM   .1
Vrout   Vrout 0     DC   .1
VCM     VCM  0     DC   0     SIN( 0 2.5 50 )
*TRAN   TSTEP TSTOP TSTART TMAX ?UIC?
.tran   .1u   20m   1m     .1u   UIC
=====The_CMOS_Model_Files=====
.model  NMOSC          NMOS(Level= 1 Cbs=2f Cbd=2f)
.model  PMOSC          PMOS(Level= 1 Cbs=2f Cbd=2f)
.control
run
linearize
set     pensize = 2
plot   vcm out
plot   vd2


```

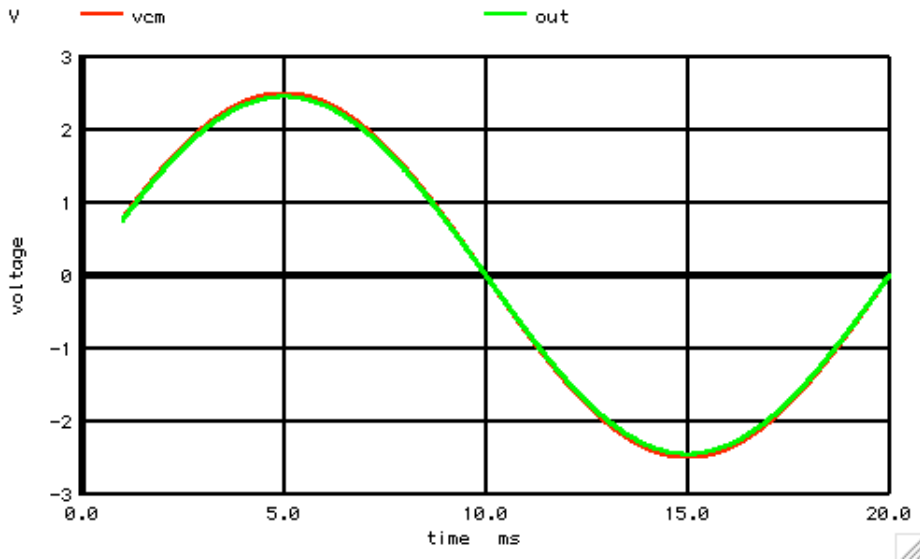Because the LCR tuned circuit at the output has two poles around 9Khz, the "resistor" has a limited bandwidth. But 50Hz is no problem.




And one is going to want to do a V to I curve.
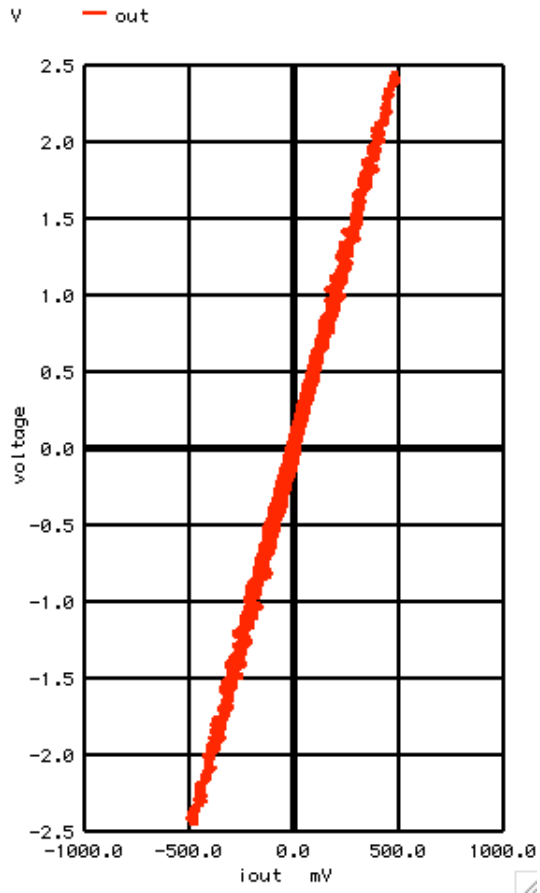
```
let      iout = -(out-vcm)/.1  
plot    out vs iout
```




The current in the CMOS transistors can be observed with a little low pass filtering.

```
plot    vcc vpf mean(vp)
```

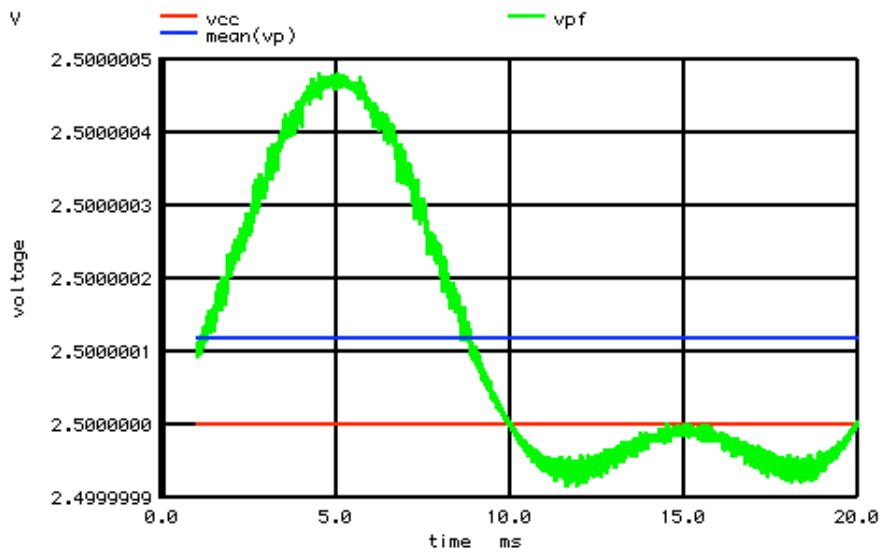


So now power in **VCC**, **VEE**, and **VCM** can be monitored.
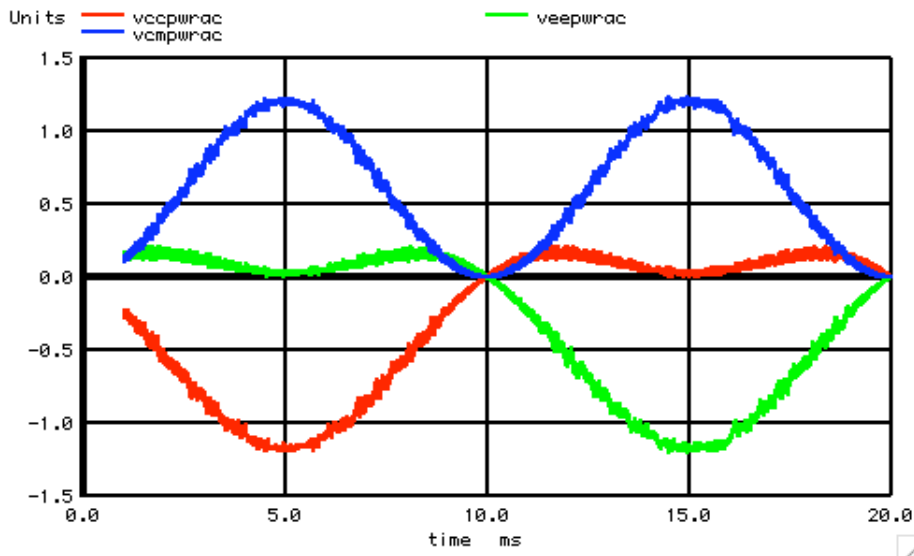
```
let      vccpwrac=vcc*(vcc-vpf)/1u
let      veepwrac=vee*(vee-vnf)/1u
let      vcmpwrac=-vcm*i(vcm)
let      supplypwrac= vccpwrac+ veepwrac
plot     vccpwrac veepwrac vcmpwrac
```




The powers in **VCC** and **VEE** together will match and the power of **VCM** in magnitude, but with opposite polarity.

```
plot     vcmpwrac supplypwrac
```

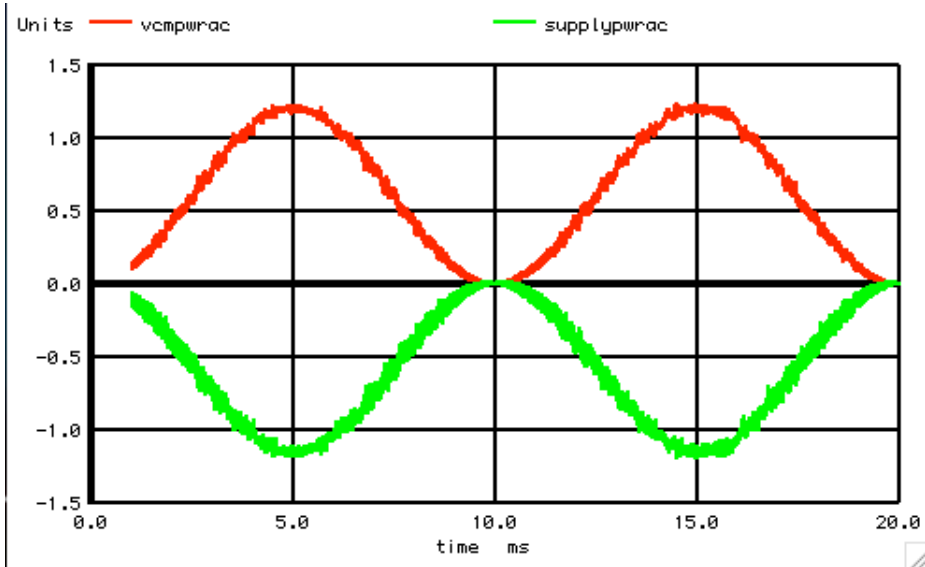

And the power out of VCM is what one would expect from a 5 Ohm resistor.

`plot norm(vcm) norm(vcmpwrac)`

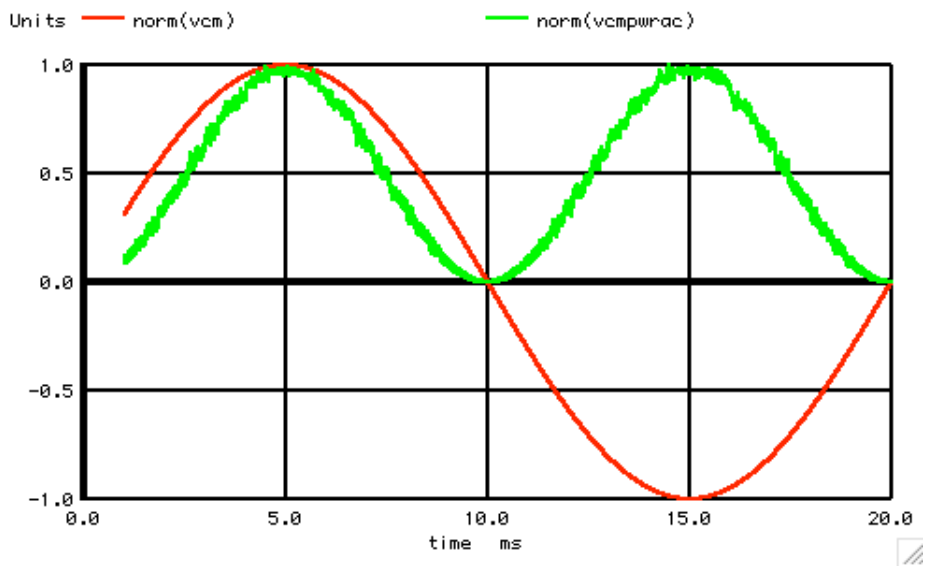


So now AC power can be converged to DC power in a much different way.

====Full_Netlist_For_Copy_Paste====

ClassD_Resistor

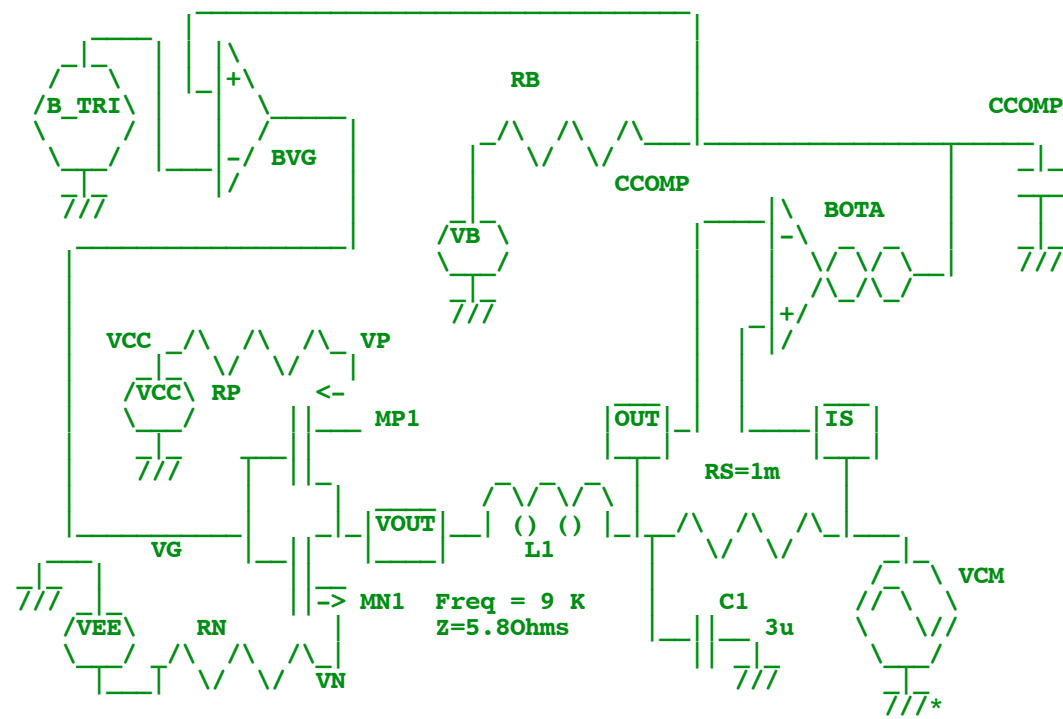*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*



*.OPTIONS GMIN=1f METHOD=trap ABSTOL=1u TEMP=27 srcsteps = 1 gminsteps = 1
*.OPTIONS RELTOL=.001 ABSTOL=1n VNTOL=1u ITL4=500 ITL1=400

====Create_Signal=====

VT	VT	0	DC	0	PWL(0	0	1	1)
Vfreq	Vfreq	0	DC	200k					
VD	VD	0	DC	.5					
RD	VD	VD2	DC	1000k					
CCOMP	VD2	0	50pF	IC=.5					
B OTA	VD2	0	I	= 1m*(v(out)-v(is))					
VPI	VPI	0	DC	3.141592653589793					
B TRI	TRI	0	V =	acos(cos(6.283185*V(VFreq)*V(VT)))/v(VPI)					
BVG	VG	0	V =	5*u(v(TRI) -v(VD2)) -2.5					
VCC	VCC	0	DC	2.5					
VEE	VEE	0	DC	-2.5					
RP	VCC	VP	1u						
RPF	VP	VPF	10K						
CPF	VPF	0	.001u						
RN	VN	VEE	1u						
RNF	VN	VNF	10K						
CNF	VNF	0	.001u						
MN1	VOUT	VG	VN	VEE	NMOSC	W=90000u	L=1u		
MP1	VOUT	VG	VP	VCC	PMOSC	W=90000u	L=1u		
L1	VOUT	OUT	100u						
C1	OUT	0	3u						
RS	OUT	IS	1m						
Rout	IS	VCM	.1						
Vrout	Vrout	0	DC	.1					
VCM	VCM	0	DC	0	SIN(0	2.5	50)

*TRAN TSTEP TSTOP TSTART TMAX ?UIC?
.tran .1u 20m 1m .1u UIC

====The_CMOS_Model_Files=====

```
.model NMOSC NMOS(Level= 1 Cbs=2f Cbd=2f)
.model PMOSC PMOS(Level= 1 Cbs=2f Cbd=2f)
```

```
.control
run
linearize
```

```
set      pensize = 2
plot    vcm out
plot    vd2

let     iout = -(out-vcm)/.1
plot    out vs iout
plot    vcc vpf mean(vp)

let     vccpwrac=vcc*(vcc-vpf)/1u
let     veepwrac=vee*(vee-vnf)/1u
let     vcmpwrac=-vcm*i(vcm)
let     supplypwrac= vccpwrac+ veepwrac

plot    vccpwrac veepwrac vcmpwrac
plot    vcmpwrac supplypwrac
plot    norm(vcm) norm(vcmpwrac)

.endc
.end
```

9.16.10_2.06PM
dsauersanjose@aol.com
Don Sauer