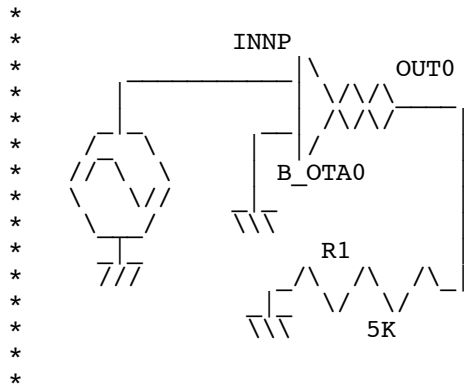


Simple_OTA_LIMITED_SAT

* dsauersanjose@aol.com 10/21/08
 * www.idea2ic.com



```
VIN      VIN      0      DC      0
B_OTA1   OUT0     0      I =     -1*v(VIABC)*tanh(( v(VIN) )/.052)
R1       OUT0     0      2k
B_BUF1   VOUT     0      V =     v(OUT0)
V_Iabc   VIABC    0      DC      1m
```

```
.control
dc      vin      -1V 1V 1m v_iabc .5m 1m .1m
run
set     pensize = 2
plot   v(out0)
.endc

.end
```

=====END_OF_SPICE=====

To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>
 This code works with winspice.

The OTA structure also allows construction of any type of nonlinearities. There are several common System transfer functions which one often will encounter when trying to apply electronics to the real world. A combination of these types of nonlinearities may be needed to closely simulate the actual nonlinearities of real world components.

The LIMIT SATURATION curve is perhaps the most common. It is the type of nonlinearity that OTAs have.



Graph 38 - dc45: OTA_LIMITED_SAT

