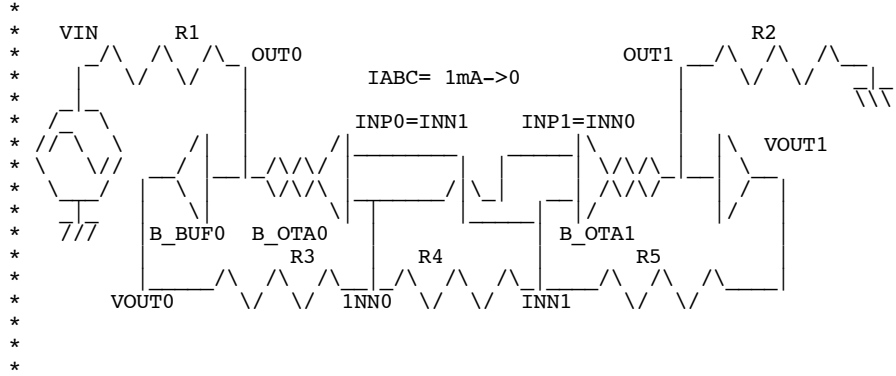


Simple OTA VCR FLOATING

* dsauersanjose@aol.com 10/21/08
 * www.idea2ic.com



```
VIN      VIN      0      SIN( 0 10m 1000 )
R1       VIN      OUT0   10K
R2       OUT1     0      10K
R3       VOUT0    INN0   100K
R4       INN1     INN0   1K
R5       VOUT1    INN1   100K
B_OTAO   OUT0     0      I = -1*v(VIABC)*tanh(( v(INN1) -v(INN0) )/.052)
B_BUF0   VOUT0    0      V = v(OUT0) -1.2
B_OTA1   OUT1     0      I = -1*v(VIABC)*tanh(( v(INN0) -v(INN1) )/.052)
B_BUF1   VOUT1    0      V = v(OUT1) -1.2
V_Iabc   VIABC    0      PWL ( 0 1m 10m 0 )
.tran    1u       10m    0      1u
```

```
.control
run
set pensize = 2
plot v(vin) v(out0) v(out1)
.endc

.end
```

=====END_OF_SPICE=====

To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>
 This code works with winspice.

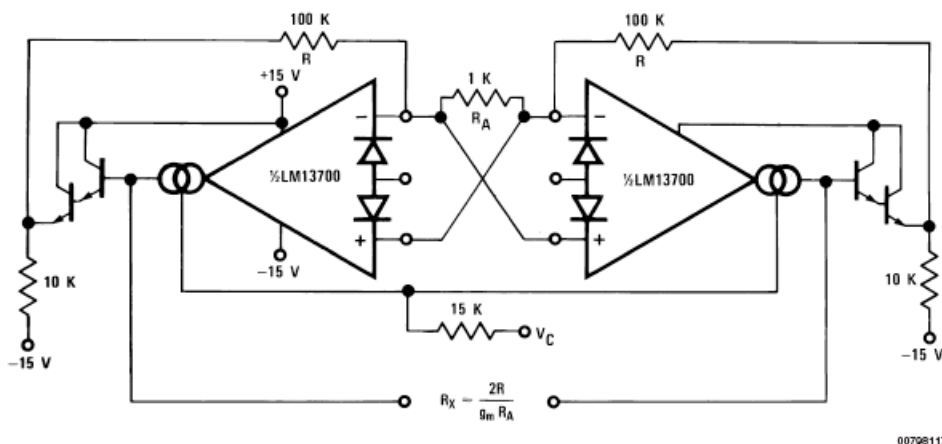


FIGURE 10. Floating Voltage Controlled Resistor

This example shows how the **floating resistor** shown in the data sheet operates. In this case the actual **1.2V offset** of the buffers can be added. All input voltages to the OTAs will float to be 1.2V lower in voltage compared to nodes OUT0 and OUT1.

