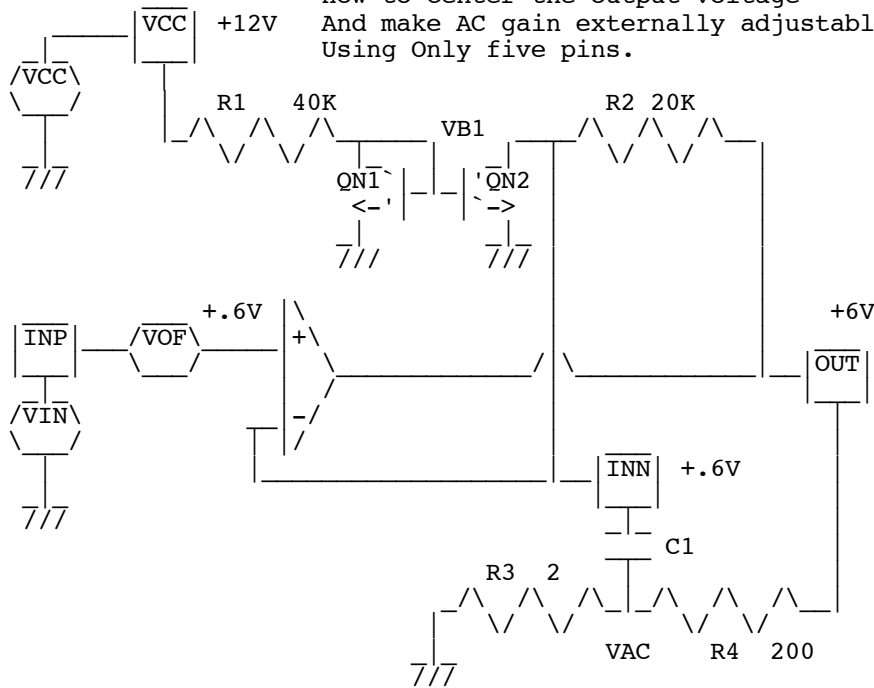


AC_DC_GAINS

* dsauersanjose@aol.com 8/15/08
 * www.idea2ic.com

How to Center the output voltage
 And make AC gain externally adjustable
 Using Only five pins.



```
.option set srcsteps = 1
VCC VC 0 DC 12
VIN IN 0 DC 0 SIN( 0 60m 10k 1n )
VOF INP IN DC .6
R1 VC VB1 40k
R2 INN OUT 20k
X_OPA INN INP OUT OP_AMP
R3 VAC 0 2
R4 OUT VAC 200
CAC INN VAC 100u
QN1 VB1 VB1 0 NPNP
QN2 INN VB1 0 NPNP
.tran 10n .2m 0 10n
```

```
.control
run
set pensize = 2
plot out vc
.endc
```

```
.SUBCKT OP_AMP INN INP OUT
EGBUF VDIFF 0 INN INP 1
RGM1 VDIFF VDIFF2 1k
RGM2 VDIFF2 VGND2 1k
CBW OUT VGND2 4p
CSP VDIFF2 0 4f
EGOUT OUT 0 VGND2 0 -100000000
.ENDS OP_AMP
```

