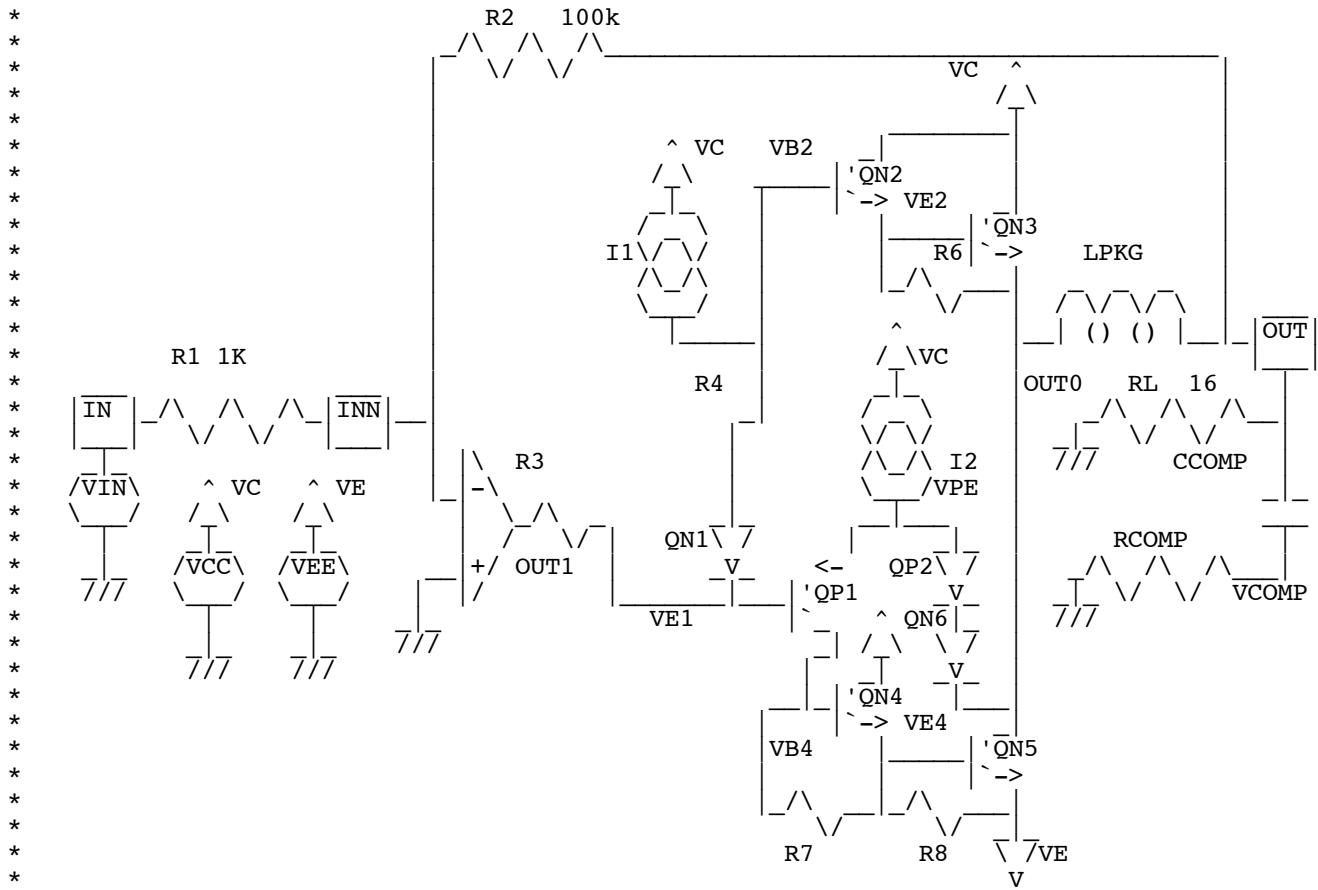


Bottom_Side_Fuzzy

* dsauersanjose@aol.com 8/15/08

* www.idea2ic.com



.OPTIONS GMIN=1e-15 METHOD=gear ABSTOL=1e-15 temp=27

VCC	VC	0	DC	8
VEE	VE	0	DC	-7
VIN	IN	0	DC	0 SIN(0 50m 10k 1n)
R1	IN	INN	1k	
R2	INN	OUT	100k	
X_OPA	INN	0	OUT1	OP_AMP
R3	OUT1	VE1	10	
QN1	VB2	VB2	VE1	NPNP 90
I1	VC	VB2	200u	
QN2	VC	VB2	VE2	NPNP 5
QN3	VC	VE2	OUT0	NPNP 100
R6	VE2	OUT	20k	
I2	VC	VPE	1m	
QP1	VB4	VE1	VPE	PNPP 1
QP2	VPB2	VPB2	VPE	PNPP 10
QN6	VPB2	VPB2	OUT0	NPNP 10
QN4	VC	VB4	VE4	NPNP 10
QN5	OUT0	VE4	VE	NPNP 200
R7	VB4	VE4	100k	
R8	VE4	VE	20k	
LPKG	OUT0	OUT	10n	
RL	OUT	0	16	
CCOMP	OUT	VCOMP	.1u	
RCOMP	VCOMP	0	1	
.tran	10n	.2m	0	10n

.control

run
set pensize = 1
plot out out1 vb4 ve title With_Comp

```

alter CCOMP capacitance = 1p
run
set pensize = 1
plot out out1 vb4 ve title WithOut_Comp

```

.endc

```

.SUBCKT OP_AMP INN INP OUT 1
EGBUF VDIFF 0 INN INP 1
RGM1 VDIFF VDIFF2 1k
RGM2 VDIFF2 VGND2 1k
CBW OUT VGND2 4p
CSP VDIFF2 0 4f
EGOUT OUT 0 VGND2 0 -100000000
.ENDS OP_AMP

```

```

*
*          CBW   _|_
*          | \  / |
*          VDIFF  RGM  VGND  EGOUT  OUT
*          | \  / |
*          | \  / |
*          INN    + EGBUF   GAIN=1  7/7  7/7  GAIN=-1M
*          | \  / |
*          | \  / |
*          INP    7/7    7/7
*          ODB = 20MHz
*
*.SUBCKT OP_AMP INN INP OUT
| \  / |
| \  / |
OPA  OUT
| \  / |
| \  / |
INP

```


```
.model NPNP NPN( BF=210 IS=1e-17 )
```

```
.model PNPP PNP( BF=10 IS=1e-17 IKF=7.6e-06 ITF=1.70E-6
+ CJE= 4e-12 CJC=1.826E-12 CJS=1.826E-12
+ TF=.03e-6 PTF=205 )
```

.end


=====Bottom_Side_Fuzzy=====

Equivalent Schematic

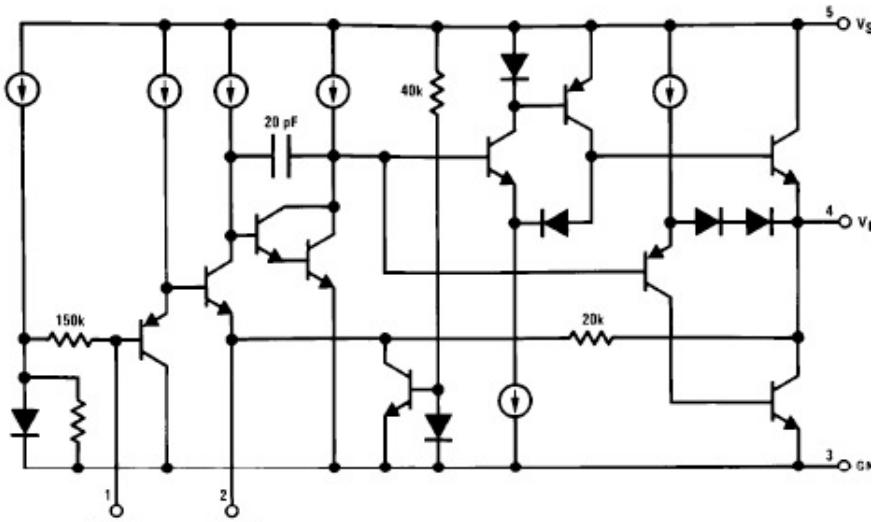


At the time that LM383 was designed, the only available PNPs were lateral and had an ftau

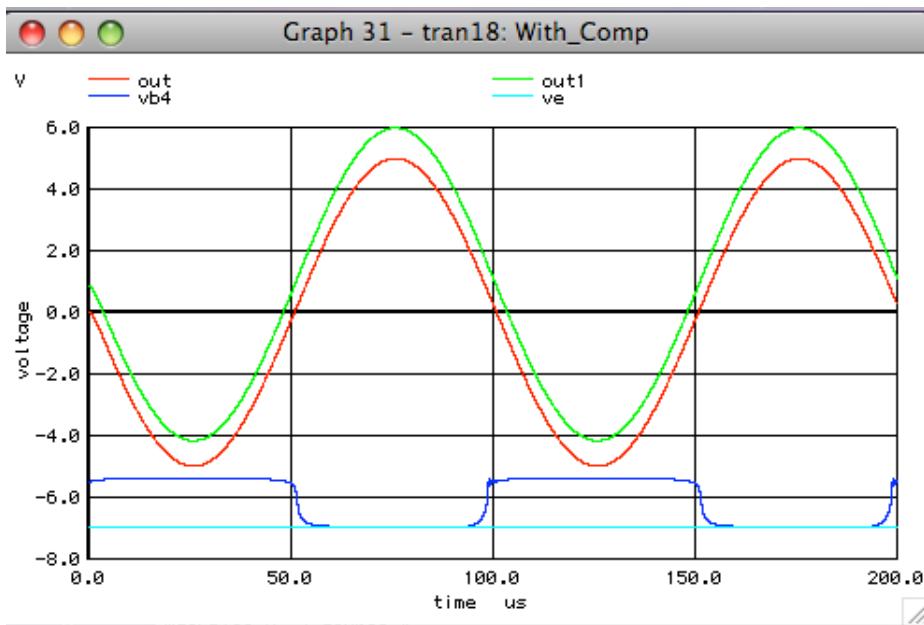around a few MegHz. They also could put out much less current. In order to have an big enough NPN output transistor be able to pull the output almost to ground at 5 amps, one of these lateral PNPs needs to be put in a loop similiar to what is shown in the LM383's equivalent schematic shown above.



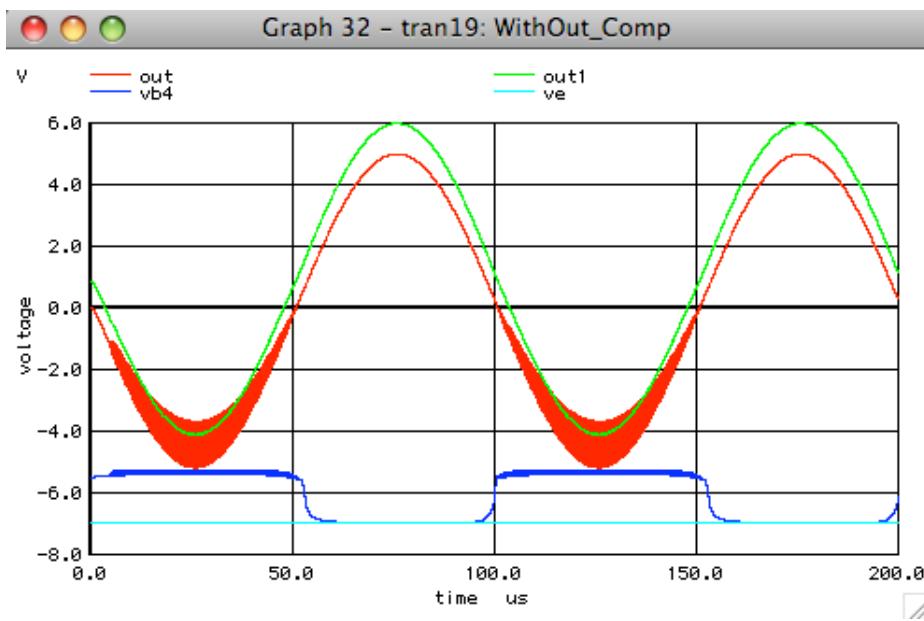It had been common practice to stablize such an output stage by connecting a capacitor and small resistor to from the output to ground. The plot above shows the output with the stability compensation network in place.



For comparison sake, the plot above is without


the stability compensation network. In this simulation, transistors QN2 and QN3 are AB biased with the bottom side pnp composite. The NPN darlington attempts to stabilize the pnp composite but is less and less able to do so as the QN5 is required to produce more output current. The lower the output voltage swings, the more QN5 turns on and QN3 turns off resulting in more instability. This was commonly referred to at that time as "the Bottom Side Fuzzies".

*#1=====WinSpiceVersion=====

Bottom_Side_Fuzzy

* dsauersanjose@aol.com 8/15/08

* www.idea2ic.com

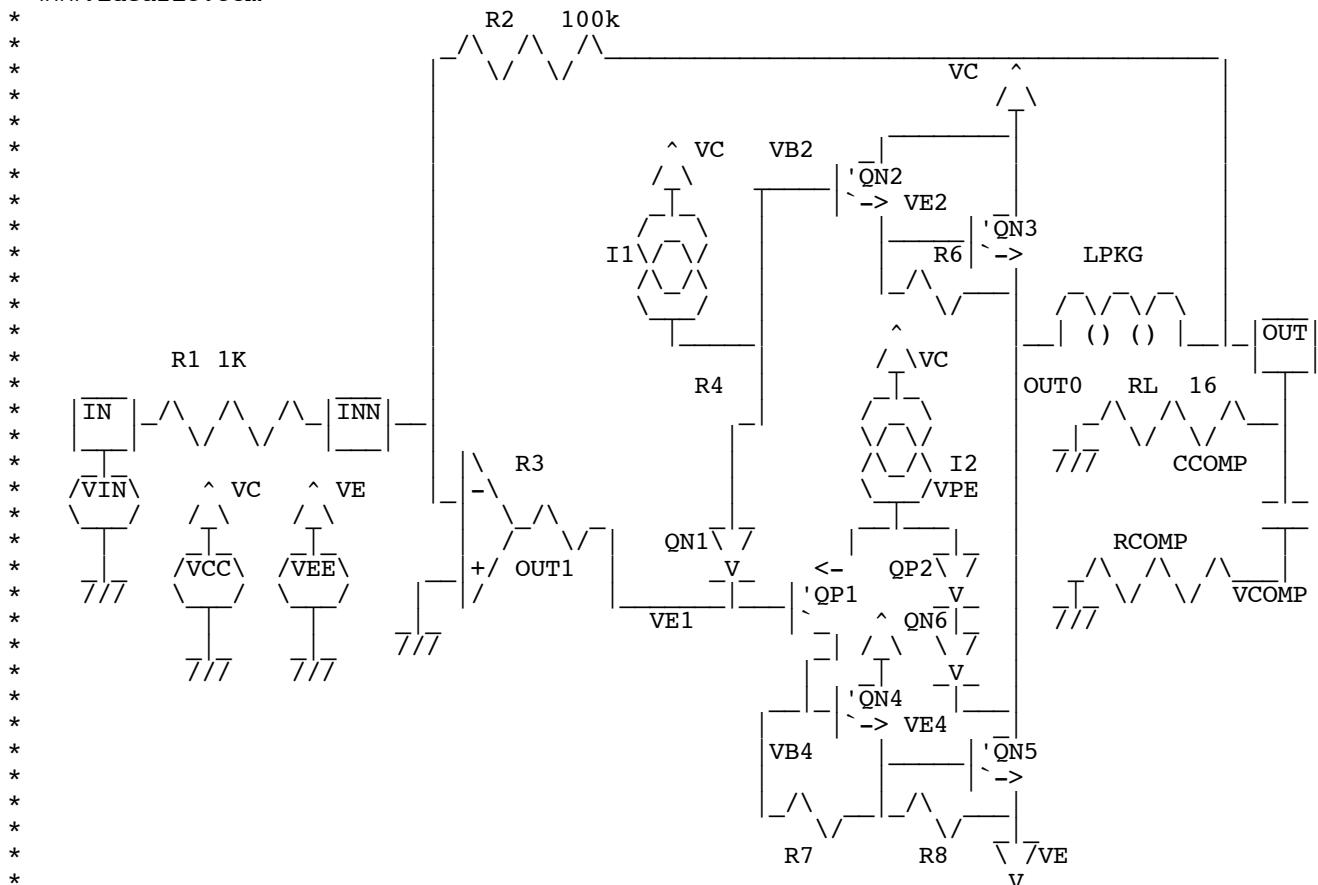

.OPTIONS GMIN=1e-15 METHOD=gear ABSTOL=1e-15 temp=27

VCC	VC	0	DC	8
VEE	VE	0	DC	-7
VIN	IN	0	DC	0 SIN(0 50m 10k 1n)
R1	IN	INN	1k	
R2	INN	OUT	100k	
X_OPA	INN	0	OUT1	OP_AMP
R3	OUT1	VE1	10	
QN1	VB2	VB2	VE1	NPNP 90
I1	VC	VB2	200u	
QN2	VC	VB2	VE2	NPNP 5
QN3	VC	VE2	OUT0	NPNP 100
R6	VE2	OUT	20k	
I2	VC	VPE	1m	

```

QP1      VB4      VE1      VPE      PNPP  1
QP2      VPB2     VPB2     VPE      PNPP  10
QN6      VPB2     VPB2     OUT0    NPNP  10
QN4      VC       VB4      VE4      NPNP  10
QN5      OUT0    VE4      VE      NPNP  200
R7       VB4      VE4      100k
R8       VE4      VE      20k
LPKG     OUT0    OUT      10n
RL       OUT      0       16
CCOMP    OUT      VCOMP .1u
RCOMP    VCOMP   0       1
.tran   10n    .2m    0       10n

.control
run
set      pensize = 1
plot    out out1 vb4 ve  title With_Comp

alter  CCOMP capacitance = 1p
run
set      pensize = 1
plot    out out1 vb4 ve  title WithOut_Comp


```

```
.endc
```

```

.SUBCKT OP_AMP INN   INP   OUT
EGBUF   VDIFF  0     INN   INP   1
RGM1    VDIFF  VDIFF2 1k
RGM2    VDIFF  VGND2 1k
CBW     OUT    VGND2 4p
CSP    VDIFF2 0     4f
EGOUT   OUT    0      VGND2 0     -100000000
.ENDS  OP_AMP

```

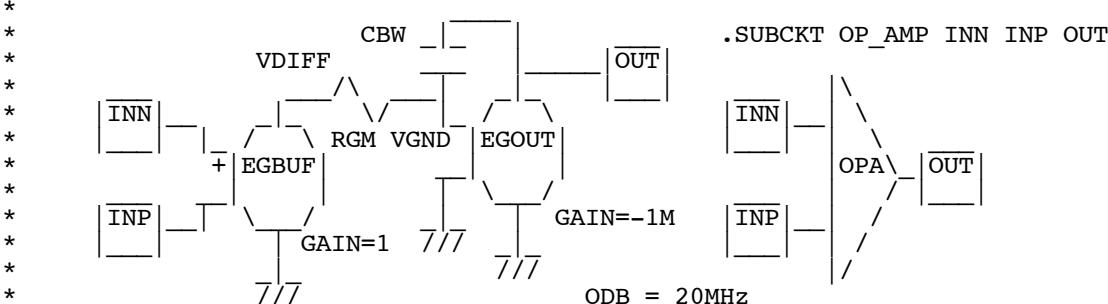

```

.model      NPNP   NPN( BF=210 IS=1e-17 )
.model      PNPP   PNP(   BF=10   IS=1e-17 IKF=7.6e-06 ITF=1.70E-6
+ CJE= 4e-12  CJC=1.826E-12   CJS=1.826E-12
+ TF=.03e-6   PTF=205      )

.end

```