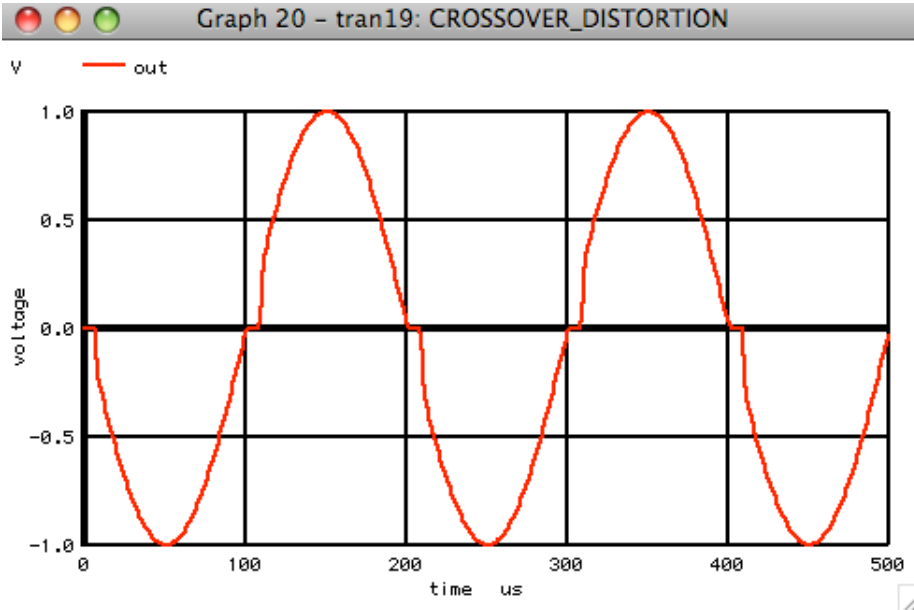





**.end**

**====CrossOver\_Distortion=====**

**One common job in designing a power amplifier is choosing a level of AB bias for the output transistors.**



 **The output transistors tend to be very large. The goal is to keep them on all the time while not wasting supply current.**




**The above simulation is a really a "B" biased output stage. Both output transistors are never**

on at the same time. Hence there is a period to time where both transistors are off and the power amplifier goes open loop at this time. The result usually shows up as glitch in the output waveform.

\*#1=====WinSpiceVersion=====

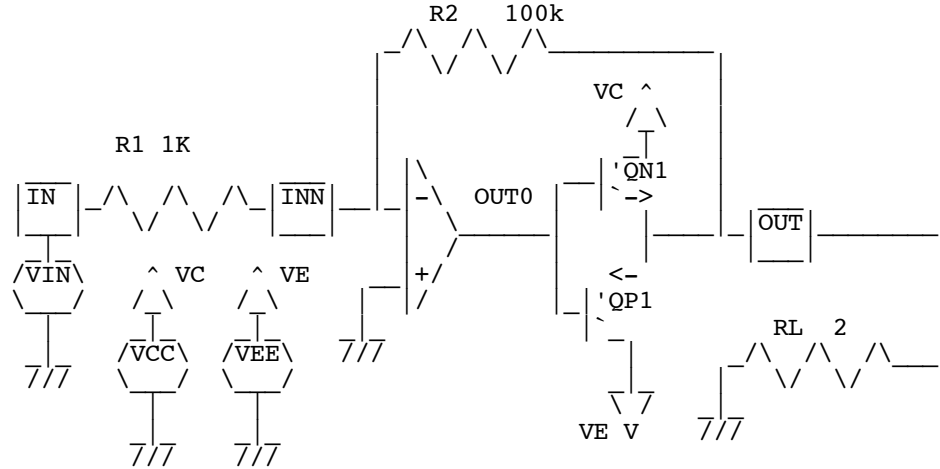CROSSOVER\_DISTORTION  
 \* dsauersanjose@aol.com 8/15/08  
 \* www.idea2ic.com



```
VCC      VC      0      DC      6
VEE      VE      0      DC     -6
VIN      IN      0      DC      0      SIN( 0 10m 5k 1n )
R1      IN      INN    1k
R2      INN     OUT   100k
RL      OUT     0      8
X_OPA   INN     0      OUT0    OP_AMP
QN1     VC      OUT0   OUT      NPNP
QP1     VE      OUT0   OUT      PNPP
```

```
.tran    1u    .5m    0      1u
```

```
.control
run
set      pensize = 2
plot    out
plot    out out0
.endc
```

```
.SUBCKT OP_AMP INN INP OUT
EGBUF  VDIFFF 0 INN INP 1
RGM    VDIFFF VGND2 1k
CBW    OUT    VGND2 8p
EGOUT  OUT    0    VGND2 0    -100000000
.ENDS OP_AMP
```

