


Top_Side_Invention

* dsauersanjose@aol.com 8/15/08

* www.idea2ic.com

* US PATENT # 4122401

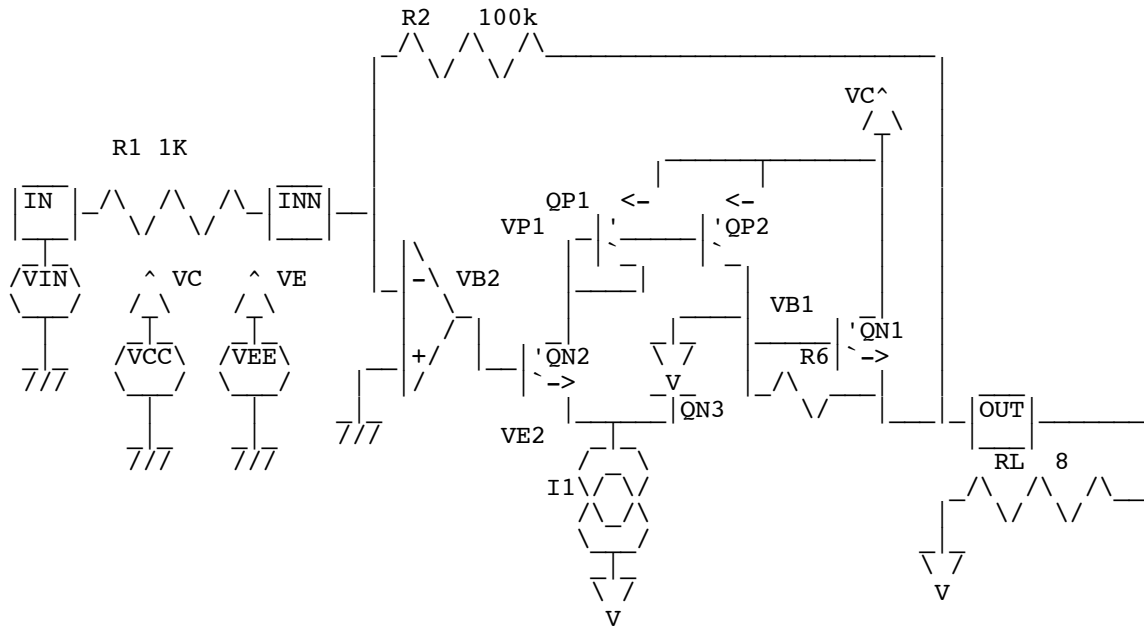*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*
*



.OPTIONS GMIN=1e-15 METHOD=gear ABSTOL=1e-15 temp=27 set srcsteps = 1

```

VCC VC 0 DC 6
VEE VE 0 DC -7
VIN IN 0 DC 0 SIN( 0 55m 10k 1n )
R1 IN INN 1k
R2 INN OUT 100k
X_OPA INN 0 OUT1 OP_AMP
R3 OUT1 VB2 1k
QN2 VP1 VB2 VE2 NPNP 5
QP1 VP1 VP1 VC PNPP 1
QP2 VB1 VP1 VC PNPP 30
QN3 VB1 VB1 VE2 NPNP 5
I1 VE2 VE 8m
QN1 VC VB1 OUT NPNP 400
R6 VB1 OUT 20k
RL OUT VE 4

```

.tran 10n .2m 0 10n

.control

```

run
set pensize = 1
plot out vb1 vc
plot out
.endc

```


.SUBCKT

```


OP_AMP INN INP OUT
EGBUF VDIFF 0 INN INP 1
RGM1 VDIFF VDIFF2 1k
RGM2 VDIFF2 VGND2 1k
CBW OUT VGND2 4p
CSP VDIFF2 0 4f
EGOUT OUT 0 VGND2 0 -100000000
.ENDS OP_AMP

```


* US PATENT # 4122401

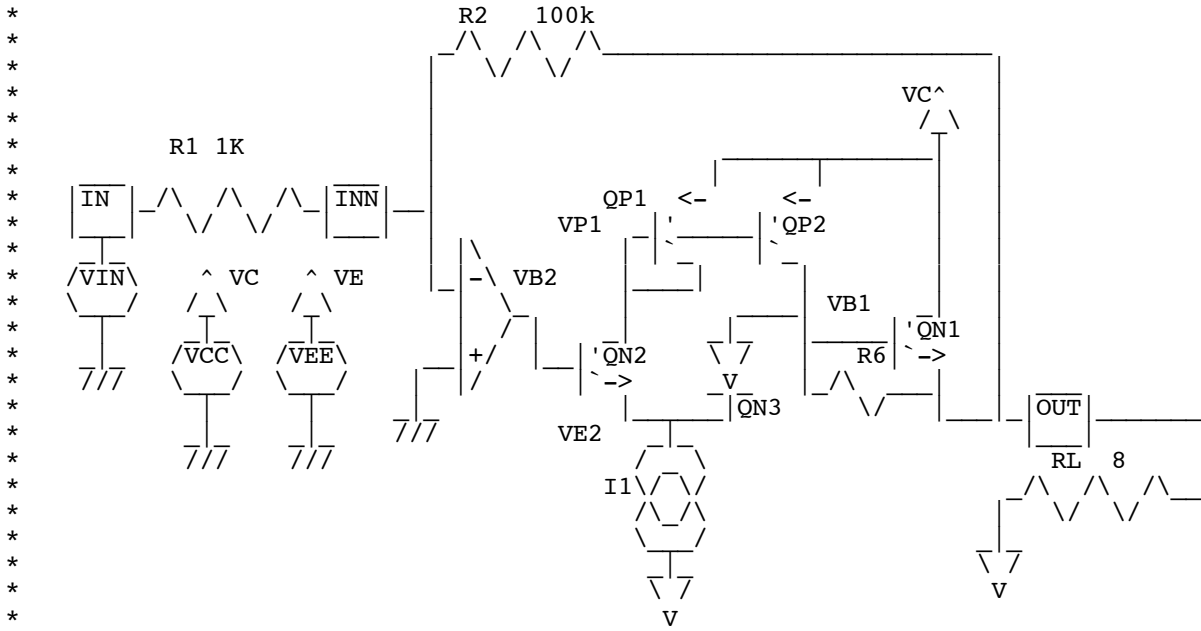

The invention shown above uses a diode and current source to make a smaller current loop. Transistor QN1 still needs to put out 5Amps. That means QP2 will still have to have as much current gain as possible. QP1 is only added to sort of stabilize AB bias. The 5Amps output requirement still needs current gain from both the PNP and NPN. But both current gains don't have to be put together in the same loop.

 

With the top side composite much more stable, the stability situation for the bottom side composite remains about the same.


***#1=====WinSpiceVersion=====**

Top_Side_Invention

* dsauersanjose@aol.com 8/15/08

* www.idea2ic.com

* US PATENT # 4122401

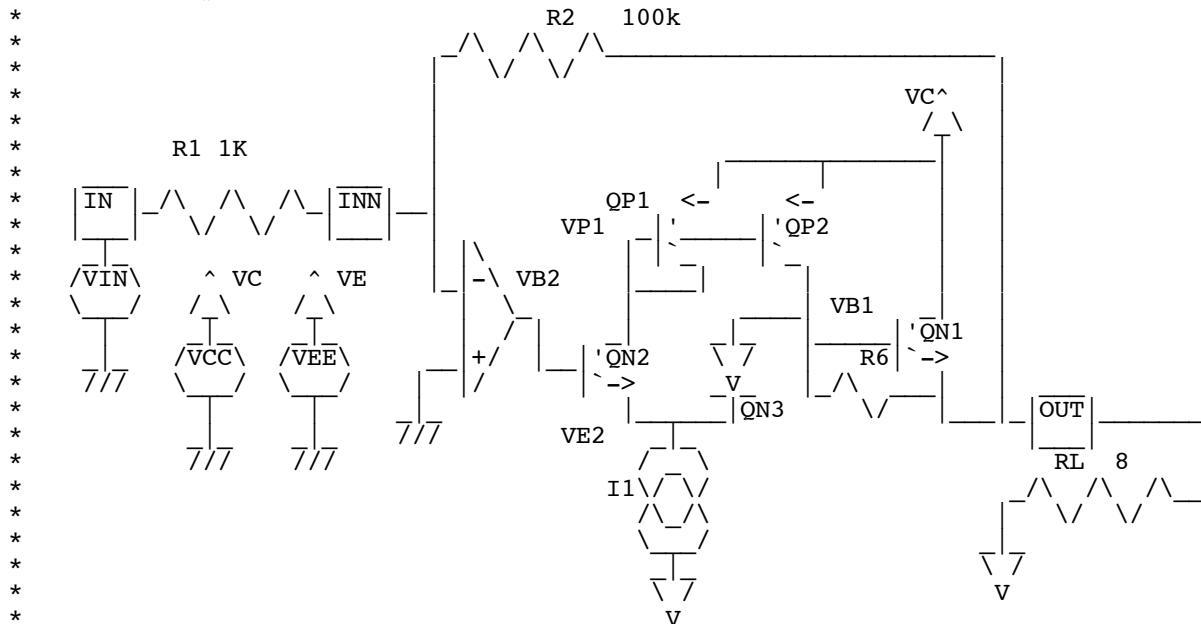

.OPTIONS GMIN=1e-15 METHOD=gear ABSTOL=1e-15 temp=27 set srcsteps = 1

```
VCC      VC      0      DC      6
VEE      VE      0      DC     -7
VIN      IN      0      DC      0      SIN( 0 55m 10k 1n )
R1       IN      INN    1k
R2       INN     OUT    100k
X_OPA    INN     0      OUT1    OP_AMP
R3       OUT1    VB2    1k
QN2      VP1     VB2    VE2     NPNP  5
QP1      VP1     VP1    VC      PNPP  1
QP2      VB1     VP1    VC      PNPP  30
QN3      VB1     VB1    VE2     NPNP  5
I1       VE2    VE      8m
QN1      VC      VB1    OUT     NPNP  400
R6       VB1     OUT    20k
RL       OUT     VE      4
.tran    10n    .2m    0      10n
```

```
.control
run
set pensize = 1
plot out vb1 vc
plot out
```

.endc

```
.SUBCKT OP_AMP INN INP OUT
EGBUF VDIFF 0 INN INP 1
RGM1 VDIFF VDIFF2 1k
RGM2 VDIFF2 VGND2 1k
CBW OUT VGND2 4p
CSP VDIFF2 0 4f
EGOUT OUT 0 VGND2 0 -100000000
.ENDS OP_AMP
```

```
*
* CBW _|_ _ _ _ .SUBCKT OP_AMP INN INP OUT
```

