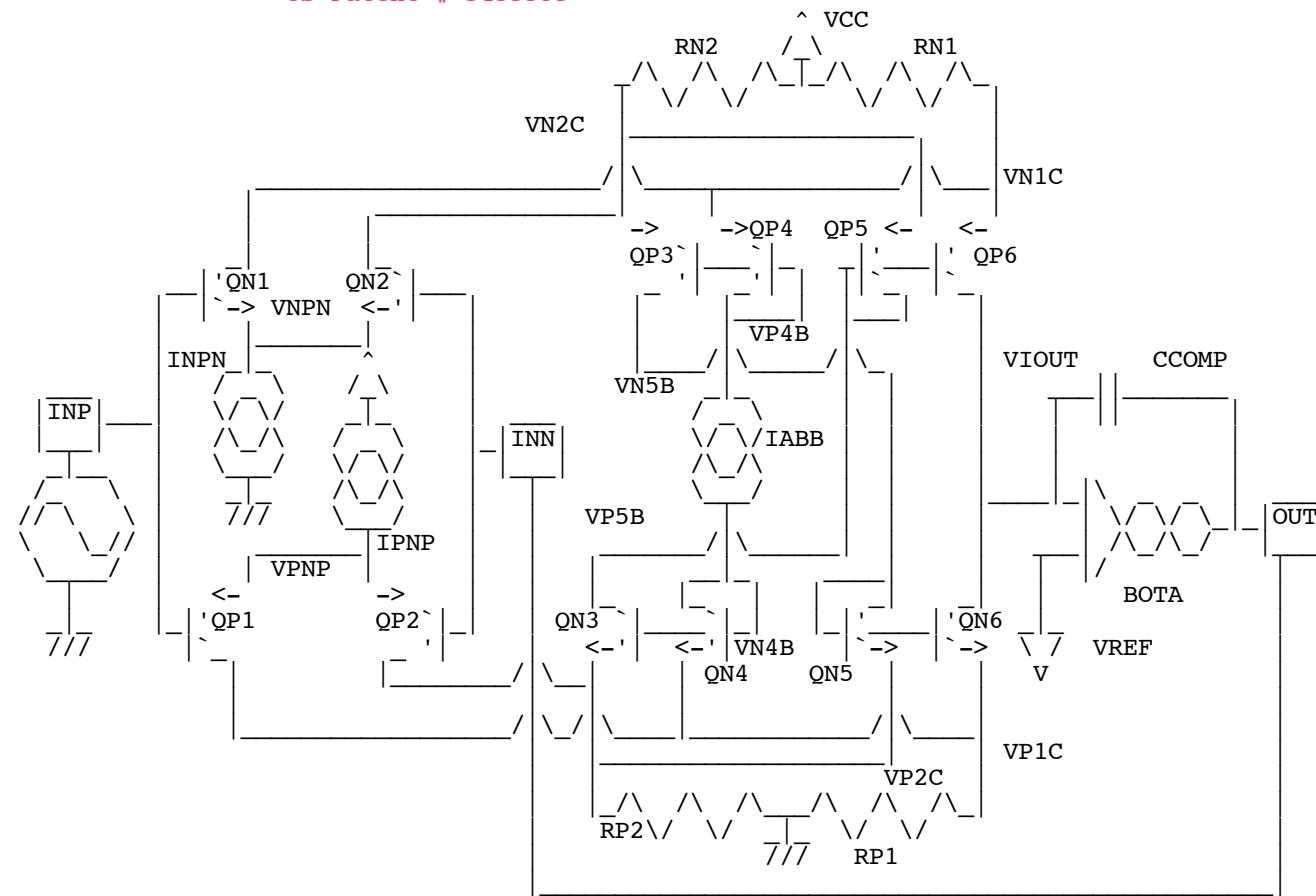


AB_BIAS_TURNAROUND

* dsauersanjose@aol.com 12/17/08

* www.idea2ic.com

* US Patent # 5455535



.OPTIONS method=trap

VIN	INP	0	PULSE(1 9 1n 1n 1n 10u 20u) dc 6
QP1	VP1C	INP	VPNP PPNPV 1
QP2	VP2C	OUT	VPNP PPNPV 1
RP1	VP1C	0	5K
RP2	VP2C	0	5K
QN1	VN1C	INP	VNPN NPNV 1
QN2	VN2C	OUT	VNPN NPNV 1
RN1	VCC	VN1C	5K
RN2	VCC	VN2C	5K

```

VCC      VCC      0      12
VREF     VREF      0      6
IPNP     VCC      VPNP    20u
INPN     VNPN     0      20n

QP3      VN5B     VP4B    VN2C    PNPV    1
QP4      VP4B     VP4B    VN1C    PNPV    1
QP5      VP5B     VP5B    VN2C    PNPV    1
QP6      VIOUT   VP5B    VN1C    PNPV    1

QN3      VP5B     VN4B    VP2C    NPNV    1
QN4      VN4B     VN4B    VP1C    NPNV    1
QN5      VN5B     VN5B    VP2C    NPNV    1
QN6      VIOUT   VN5B    VP1C    NPNV    1

IABB     VP4B     VN4B    2u
BOTA     OUT      0      I = -1*( V(VIOUT) - V(VREF) )/50
CCOMP    OUT      VIOUT   20p

.tran    100n    50u    0      100n
.model   NPNV    npn     BF=150
.model   PNPV    pnp     BF=150

.control
run
set      pensize = 2
*plot    v(out) v(inp)
echo    "4% Area Sensitivity vs Transistor \n"
echo    "MissMatch Device      Input_Offset_mV"
op
let      voffset = (v(out)- v(inp))*1000
echo    "0%          QP1      $&voffset"
alter   QP1      area =1.04
op
let      voffset = (v(out)- v(inp))*1000
echo    "4%          QP1      $&voffset"
alter   QP1      area =1
alter   QP2      area =1.04
op
let      voffset = (v(out)- v(inp))*1000
echo    "4%          QP2      $&voffset"
alter   QP2      area =1
alter   QP3      area =1.04
op
let      voffset = (v(out)- v(inp))*1000
echo    "4%          QP3      $&voffset"
alter   QP3      area =1
alter   QP4      area =1.04
op
let      voffset = (v(out)- v(inp))*1000
echo    "4%          QP4      $&voffset"

```

```

alter      QP4      area =1
alter      QN1      area =1.04
op
let        voffset = (v(out)- v(inp))*1000
echo      "4%          QN1           $&voffset"
alter      QN1      area =1
alter      QN2      area =1.04
op
let        voffset = (v(out)- v(inp))*1000
echo      "4%          QN2           $&voffset"
alter      QN2      area =1
alter      QN3      area =1.04
op
let        voffset = (v(out)- v(inp))*1000
echo      "4%          QN3           $&voffset"
alter      QN3      area =1
alter      QN4      area =1.04
op
let        voffset = (v(out)- v(inp))*1000
echo      "4%          QN4           $&voffset"
alter      QN4      area =1
alter      RN1      resistance =5050
op
let        voffset = (v(out)- v(inp))*1000
echo      "1%          RN1           $&voffset"
alter      RN1      resistance =5000
alter      RN2      resistance =5050
op
let        voffset = (v(out)- v(inp))*1000
echo      "1%          RN2           $&voffset"
alter      RN2      resistance =5000
alter      RP1      resistance =5050
op
let        voffset = (v(out)- v(inp))*1000
echo      "1%          RP1           $&voffset"
alter      RP1      resistance =5000
alter      RP2      resistance =5050
op
let        voffset = (v(out)- v(inp))*1000
echo      "1%          RP2           $&voffset"

.endc
.end

* ======END=====

```


To Convert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

The goal of any Op Amp design is to minimize input offset voltage and input referred to noise. This implies that both offset and noise should be dominated by only the input stage and that all following stage should be insignificant.


Both noise and offset add with power such that in input stage which contributes a 1mV standard deviation of input offset which is followed by second stage which contributes 1/5mV of offset will have a combined offset of..

$$1.02 = \sqrt{1^2 + (.2)^2}$$


For the LM6142, the two input stages needed to be combined together such that either input stage could work as well. Plus there was the added requirement that the inputs should be able to exceed both rails by 200mV. There was another requirement for the LM6142. The cell phone application at the time was needing an Op Amp with greatly that 10MegHz GainBandWidth Product which of course had to be unity gain stable with a 200pF load capacitor. And add to this the noise and offset should always be dominated by the input.

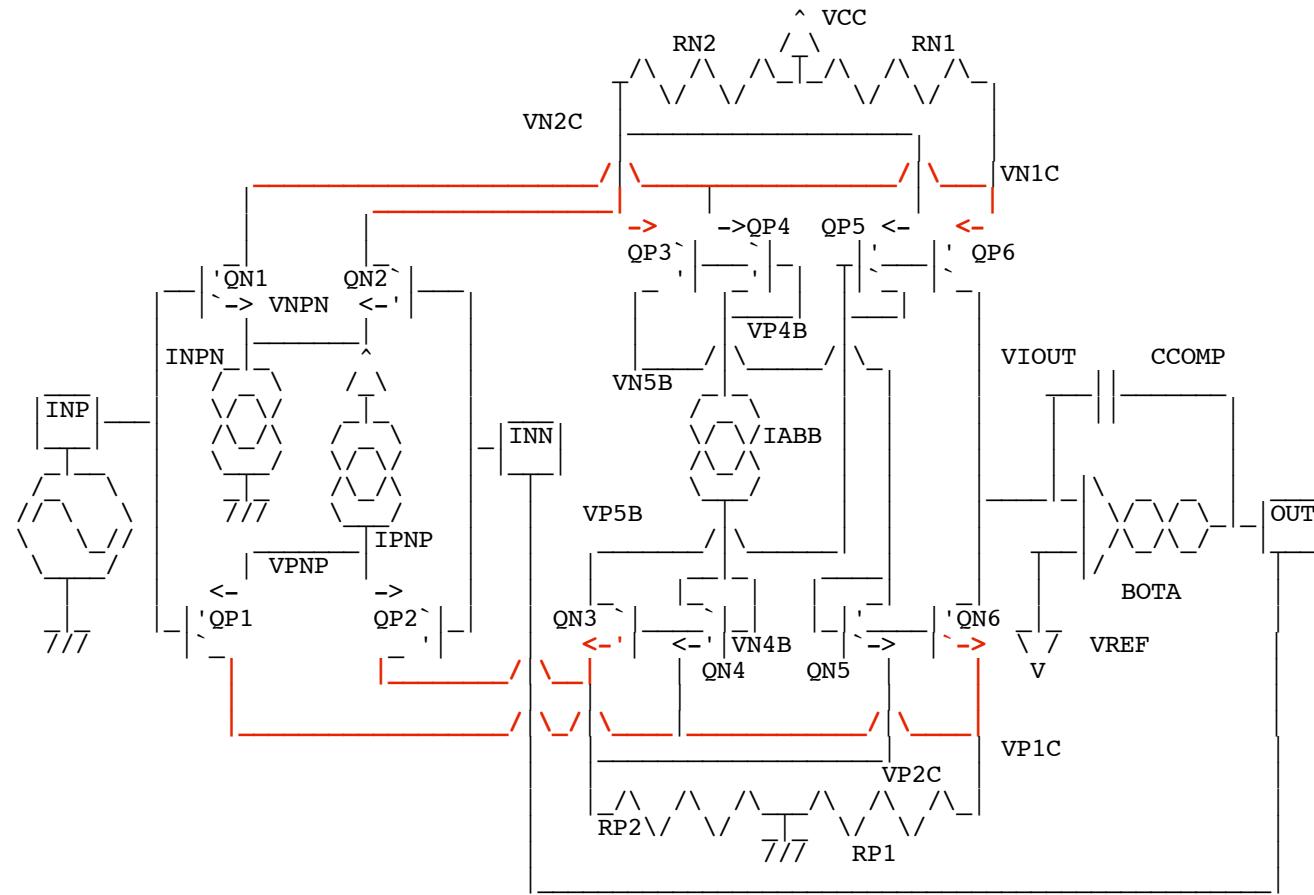

Several things were discovered using the circuit above. Driving signal into an emitter of a transistors as actually the first way transistors were used. This "common base" drive has the advantage in that it is one of the fastest ways to drive a bipolar transistor. Given that the input stages wanted to have their collectors go to resistor anyway was convenient. Resistors have low offset and noise. Having an input stage take gain in some resistors was a common practice.

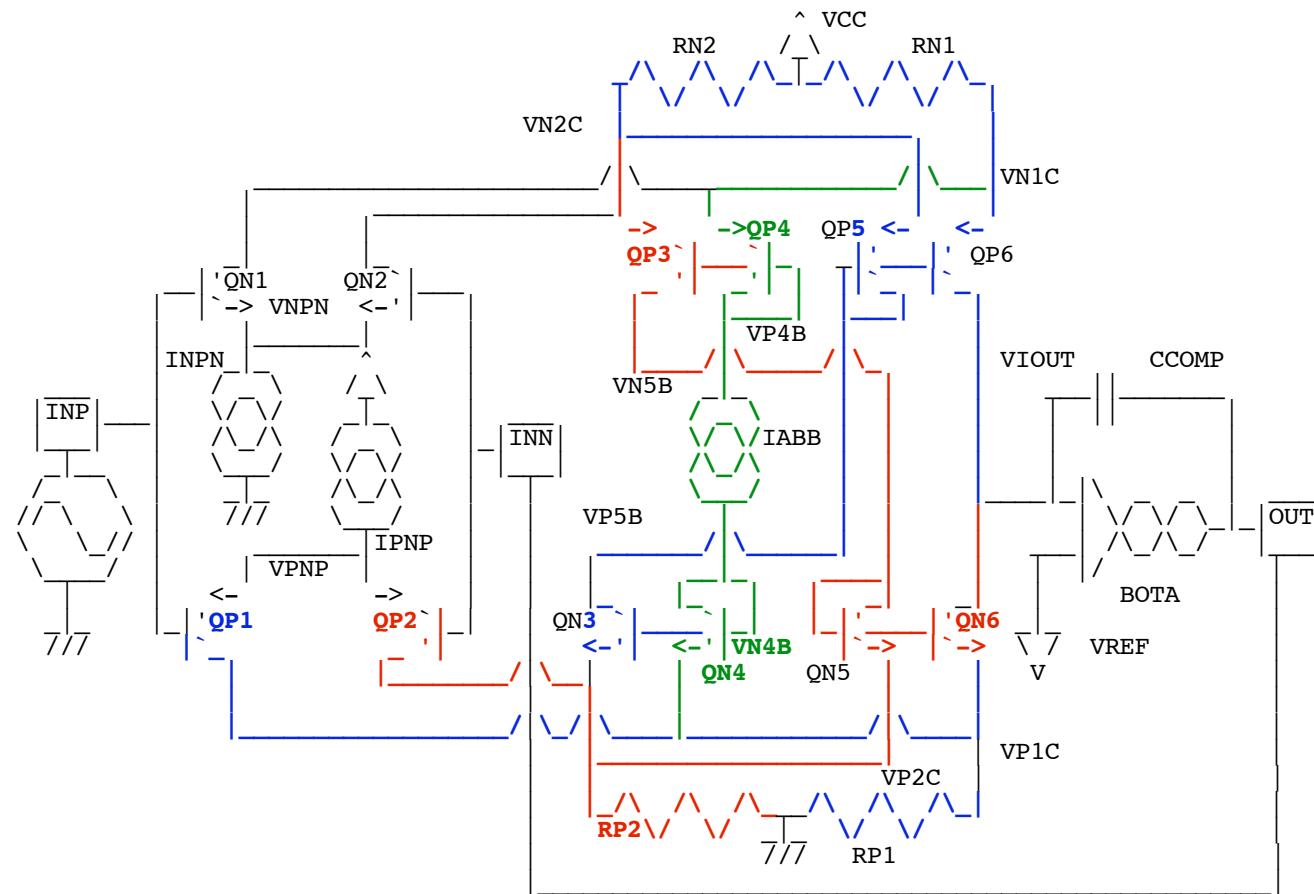

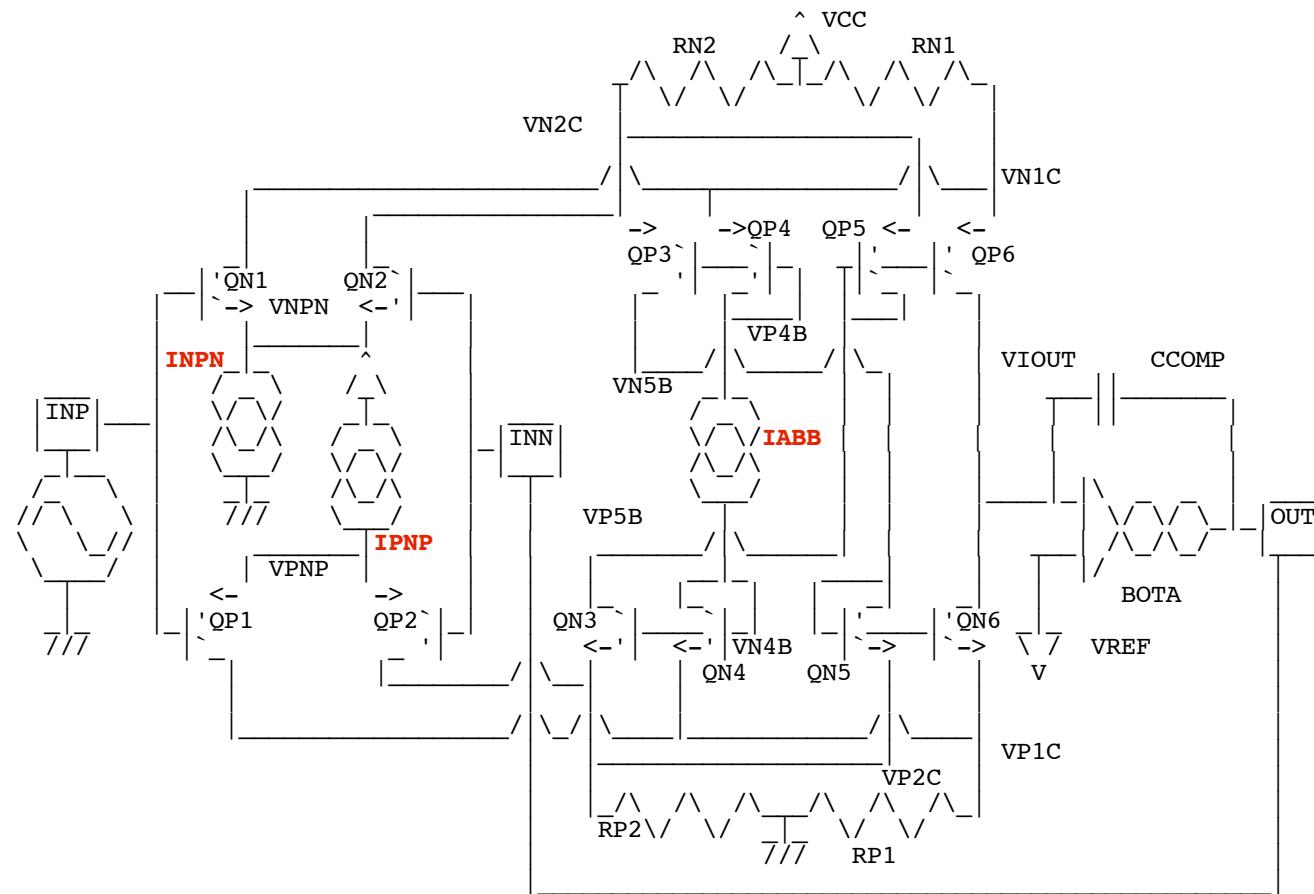This dual input turn around stage is using diode and cross coupling to communicate a differential signal from one end to the other. In the circuit above, assume QP1 is turning off (getting cold) while QP2 is turning on (getting warm). A differential signal is involving all the transistors and resistors. The resistor a driving base voltage through diodes and directly driving emitters.



There is another important feature in that this stage operates in an AB bias mode. Current source IABB is chosen to be much less than what INPN or IPNP. A 1mV offset in the input stage represents a 4% area mismatch. If all the transistors in the turn around stage are running at a much lower current, then their 4% contribution of mismatch is at a smaller current level.

MissMatch	Device	Input_Offset_mV
0%	QP1	-7.71252E-07
4%	QP1	-1.0134
4%	QP2	1.0134
4%	QP3	0.262465
4%	QP4	-0.26256

4%	QN1	0.00101179
4%	QN2	-0.00101337
4%	QN3	-0.2625
4%	QN4	0.262525
1%	RN1	0.102932
1%	RN2	-0.102494
1%	RP1	-0.359263
1%	RP2	0.35926

The simulation is performing a transistor by transistor mismatch on all transistors and measuring the resulting input offset. A 1mV or 4% mismatch for transistor and a 1% mismatch for resistor may be a little high. But their close enough to be convenient.

From the table that the simulation prints out, the input transistors QP1 and QP2 dominate. The input is configured in the LM324 mode which is just pnp inputs. As desired, the process parameters of the vertical input pnps define most of the performance specs.