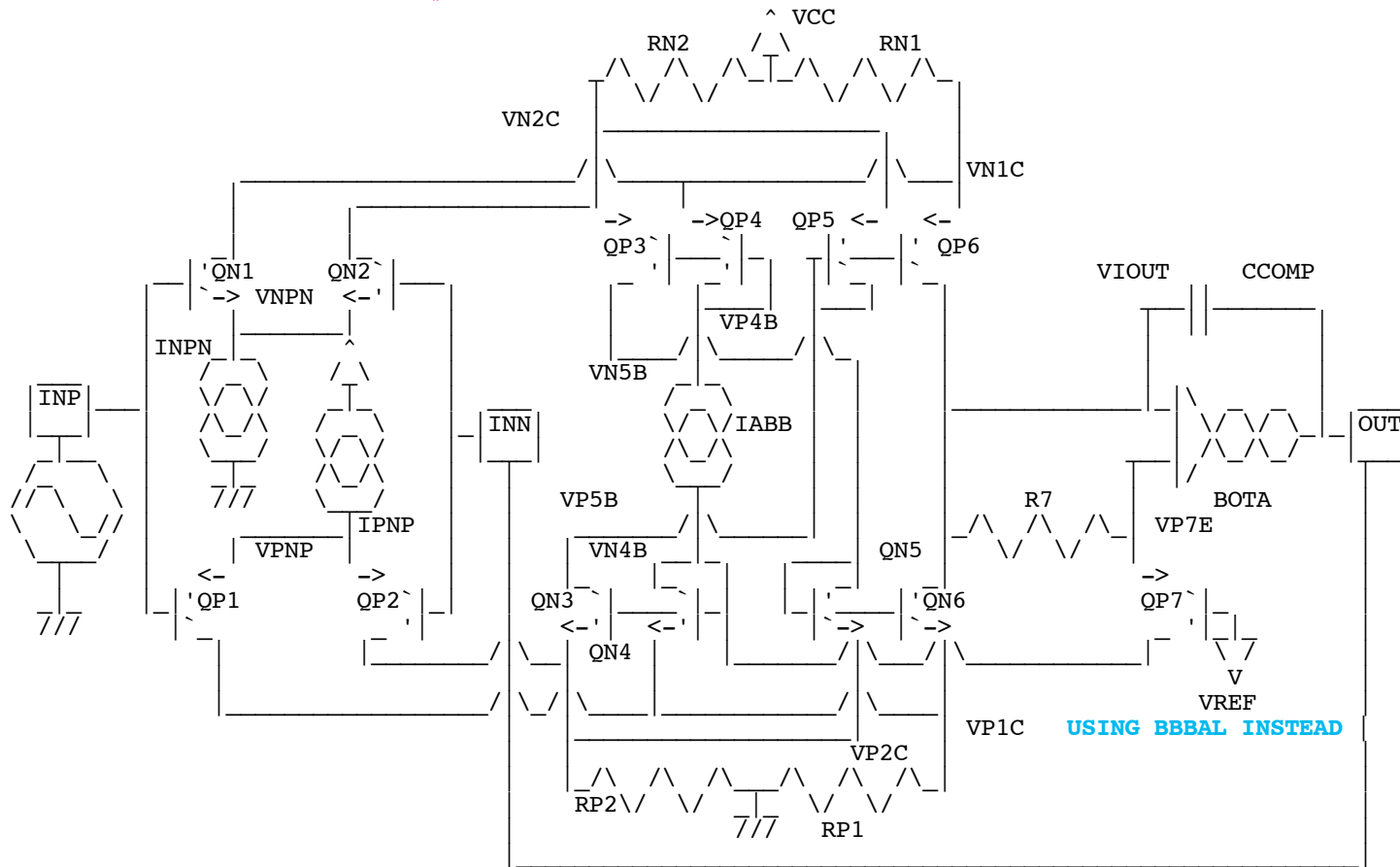


BETA_BALANCE

* dsauersanjose@aol.com 12/17/08

* www.idea2ic.com

US Patent # 545535



.OPTIONS method=trap

VIN	INP	0	DC 6	AC 1m	
QP1	VP1C	INP	VPNP	PNPV	1
QP2	VP2C	OUT	VPNP	PNPV	1
RP1	VP1C	0	5K		
RP2	VP2C	0	5K		
QN1	VN1C	INP	VNPN	NPNV	1
QN2	VN2C	OUT	VNPN	NPNV	1
RN1	VCC	VN1C	5K		
RN2	VCC	VN2C	5K		

```

VCC      VCC      0      12
VREF     VREF     0      6
IPNP     VCC      VPNP    20u
INPN     VNPN     0      20n

QP3      VN5B     VP4B     VN2C     PNPV    1
QP4      VP4B     VP4B     VN1C     PNPV    1
QP5      VP5B     VP5B     VN2C     PNPV    1
QP6      VIOUT    VP5B     VN1C     PNPV    1

QN3      VP5B     VN4B     VP2C     NPNV    1
QN4      VN4B     VN4B     VP1C     NPNV    1
QN5      VN5B     VN5B     VP2C     NPNV    1
QN6      VIOUT    VN5B     VP1C     NPNV    1

IABB     VP4B     VN4B     5u
BOTA     OUT      0      I = -1*( V(VIOUT) - V(VREF) ) * 1
CCOMP    OUT      VIOUT    1p
R7       VIOUT    VREF     20K
RL       OUT      VREF     1Meg

VBBAL    VBBAL    0      DC 2.07E14
BBBAL    VN4B     0      I = -1*( V(VIOUT) - V(VREF) ) / V(VBBAL)

.model   NPNV    npn      BF=150  CJE=.3p  VAF=200
.model   PNPV    pnp      BF=60   CJE=.3p  VAF=60

.control
run
set      pensize = 2

ac       dec 10 1 100000K
let      gain = v(out) / ( v(out) - v(inp) )
plot     dB(gain) phase(gain) title No_Load

alter    RL resistance = 10k
ac       dec 10 1 100000K
let      gain = v(out) / ( v(out) - v(inp) )
plot     dB(gain) phase(gain) title 10K_Load

alter    RL resistance = 1k
ac       dec 10 1 100000K
let      gain = v(out) / ( v(out) - v(inp) )
plot     dB(gain) phase(gain) title 1K_Load

alter    VBBAL dc = 2.06E4
ac       dec 10 1 100000K
let      gain = v(out) / ( v(out) - v(inp) )
plot     dB(gain) phase(gain) title 1K_Load_with_Beta_Bal


.endc
.end

```


* =====END=====

To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

 
The output stage of a RRIO is effectively a transconductance stage in that it produces output current out of pnp collector off the top rail and a npn collector off the bottom rail.



 
This type of output stage demonstrates a requirement of current gain. When the output stage is not loaded with any resistance or current, the open loop gain of the Op Amp is usually defined by the early voltage of the transistors which is usually high.



 But in bipolar there is always a finite amount of input to output current gain in a transconductance amplifier. This current gain causes an output load to load the open loop gain response.



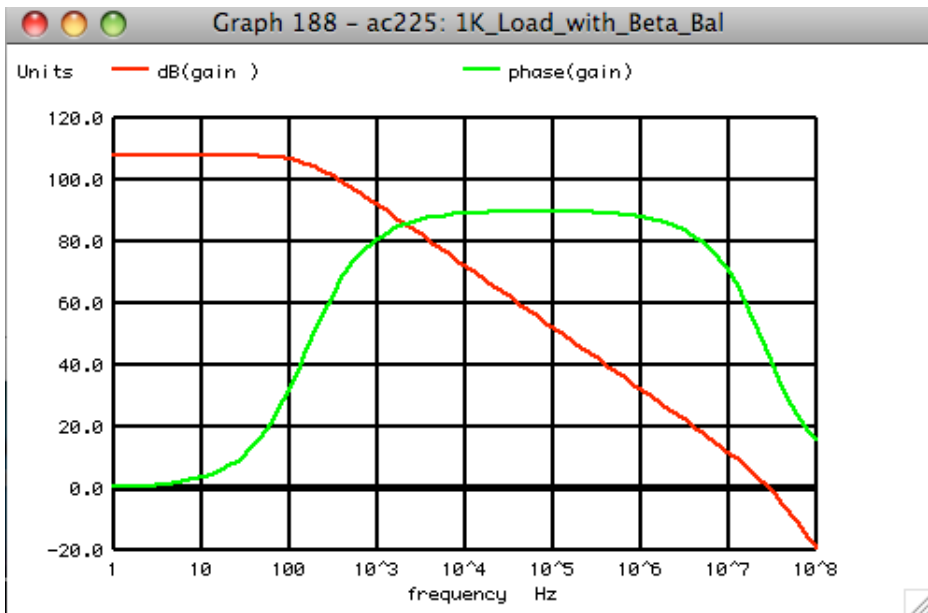The spec calls for a 600 ohm load test, and while the LM6142's output stage has the beta gain of two npns in series with a pnp, open loop gain at 600 Ohms is a little lacking.



The effect can be thought of as balancing out the errors of beta. While the exact magnitude of a beta error can not be known, any equal and opposite error coming from the same source can be recruited to cancel out both errors.