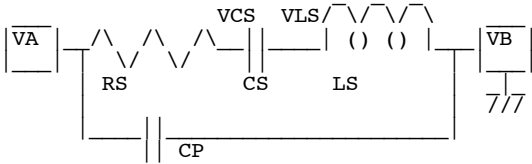


=====CRYSTAL_Serial_Network=====


What does an AC simulation predict as the oscillation frequency for a crystal model sub-circuit being used in the serial mode? Being able to mathematically process the output of an AC analysis can provide some needed precision.

=====CRYSTAL SubCircuit=====

```
.SUBCKT XCRYST VA VB
RS VA VCS 340
CS VCS VLS 7f
LS VLS VB 3.5
CP VA VB 3pf
.ENDS XCRYST
```



CS LS = 29.97meg @ 885Gohms

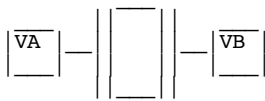


* Freq	Mode	L1	C1	R1	C0	Q
* 1 MHz	fund	3.5H	0.007pf	340	3pf	64679

The point where the crystal is more like a zero phase short circuit is being sought.

=====Test Circuit=====


OneMegCrystal_serial_network

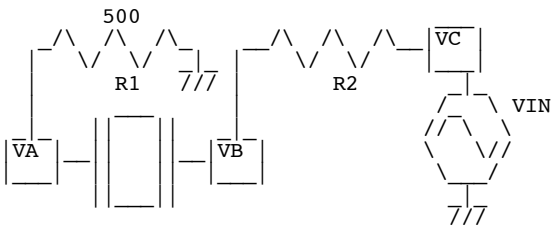

=====Run AC=====

```
.OPTIONS GMIN=1e-18 METHOD=trap ABSTOL=1e-18 TEMP=27 srcsteps = 1 gminsteps = 1
VIN VC 0 DC AC 1
XCRY1 VA VB XCRYST
R1 VA 0 500
R2 VC VB 1m
.control
*AC DECLin NUMDEC FSTART FSTOP
ac dec 600000 1.0165meg 1.0184meg
set pensize = 2
plot mag(va) mag(vb) ylog
```

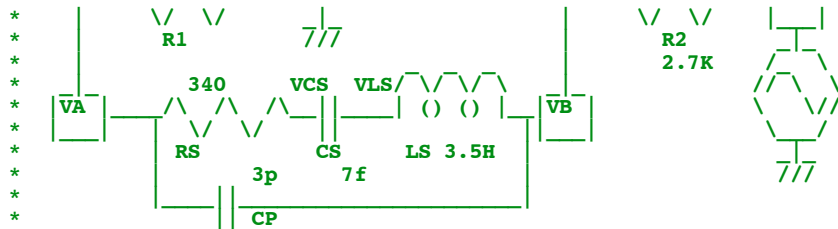At one frequency, the impedance of the crystal will try to look like a short circuit. At another frequency it will try to look like an open circuit.



```

* 1.017e+6
* Freq          Mode L1    C1      R1      C0      Q
* 1 MHz         fund  3.5H   0.007pf 340     3pf     64679
*
.OPTIONS GMIN=1e-18  METHOD=trap  ABSTOL=1e-18  TEMP=27  srcsteps = 1  gminsteps = 1
VIN      VC          0          DC        AC        1
XCRY1    VA         VB          XCRYST
R1       VA          0          500
R2       VC         VB          1m

```

```

.control
*AC      DECLin NUMDEC FSTART   FSTOP
ac      dec   600000 1.0165meg 1.0184meg
set     pensize = 2
plot    mag(va) mag(vb)      ylog

```

```

=====Process_Output_Arrays=====
let     lenV= length(va)
compose phva_deg start = 1 stop = $&lenV step = 1
compose f_Hz      start = 1 stop = $&lenV step = 1
settype frequency      f_Hz

```

```

=====Remove_Phase_Wrap_around_If_Needed=====

```

```

let     i = 0
let     phasMin=180
let     FrqPHZero = 0
repeat $&lenV
let     phva_deg[i] = ph(va[i])

```

```

if      (phva_deg[i] > 0)
let     phva_deg[i] = phva_deg[i]
endif

```

```

if      (abs(phva_deg[i]) < phasMin)
let     phasMin = abs(phva_deg[i])
let     FrqPHZero = frequency[i]
endif

```

```

let     f_Hz[i] = frequency[i]
let     i = i + 1
end

```

```

=====Find_Where_Phase_zero=====

```

```

plot    phva_deg  db(va) vs f_Hz
plot    phva_deg  db(va) vs f_Hz xlimit 1.01678Meg 1.01682meg ylimit -10 0
print   FrqPHZero

```

```

.endc

```

```


=====CRYSTAL_SubCircuit=====

```

```

.SUBCKT XCRYST VA VB
RS      VA      VCS    340
CS      VCS     VLS    7f
LS      VLS     VB     3.5
CP      VA      VB     3pf
.ENDS XCRYST

```

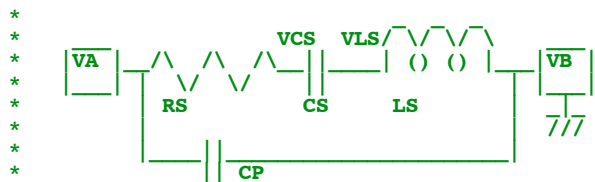

CS LS = 29.97meg @ 885Gohms



```

* Freq          Mode L1    C1      R1      C0      Q
* 1 MHz         fund  3.5H   0.007pf 340     3pf     64679

```

*

*=====

.end

4.11.10_4.54PM
dsauersanjose@aol.com
Don Sauer
<http://www.idea2ic.com/>