 



**Sample\_Hold\_Two\_Stage**

When two sample and hold circuits are connected using a two phase clock, the result is an analog delay element.



The idea is to input an analog voltage say on a rising edge and output that voltage on a falling edge. It can save a lot of trouble when inputs only read output when outputs are stationary. When outputs do move in voltages, inputs should all be open.

Sample\_Hold\_two\_Stage

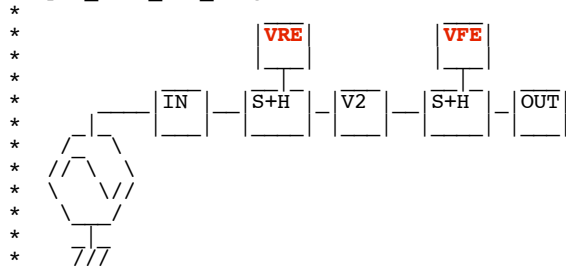


```

*V SIN#   NODE_P NODE_N DC   VALUE SIN(  V_DC  AC_MAG FREQ  DELAY  FDamp)
VIN#     IN      0      DC   0      SIN(    0    1    1k
)V PULSE# NODE_P NODE_N DC   VALUE PULSE( VINIT VPULSE TDELAY TRISE  TFALL  PWIDTH PERIOD )
VCLK     VCLK   0      DC   0      PULSE( 0    5    1n    1n    1n    25u    50u )
XRE      VCLK   VRE     RISE_E
XFE      VCLK   VFE     FALL_E
XS_H     IN     V2      VRE   S_HOLD
XS_H2    V2     OUT     VFE   S_HOLD
.MODEL   SWP    SW(    VT=2.6 VH=.2 RON=1 ROFF=10MEG)
.control
*TRAN    TSTEP  TSTOP  TSTART TMAX
tran     1u    3m    0        1u
set      pensize = 2
plot    s_h:v1 s_h:v2
plot    in out
.endc

```

**Full\_Netlist\_For\_Copy\_Paste**

 

```

*
* 777
*
*V_SIN#  NODE_P NODE_N DC    VALUE SIN(  V_DC  AC_MAG FREQ  DELAY  FDamp)
VIN      IN      0      DC    0      SIN(  0    1    1k
*V_PULSE# NODE_P NODE_N DC    VALUE PULSE( VINIT VPULSE TDELAY TRISE  TFALL  PWIDTH PERIOD )
VCLK     VCLK   0      DC    0      PULSE( 0    5    1n    1n    1n    25u    50u )
XRE      VCLK   VRE     RISE  E
XFE      VCLK   VFE     FALL  E
XS_H     IN      V2     VRE   S_HOLD
XS_H2    V2     OUT    VFE   S_HOLD
.MODEL   SWP    SW(    VT=2.6 VH=.2  RON=1  ROFF=10MEG)

```

```


.control
*TRAN    TSTEP  TSTOP  TSTART TMAX
tran     1u     3m     0       1u
set      pensize = 2
plot     s_h:v1 s_h:v2
plot     in out
.endc

```

```

=====Sample_And_Hold=====
.SUBCKT  S_HOLD IN      OUT    CNT
*SXXXXXX N+      N-      NC+    NC-    MODEL      <ON><OFF>
S1       V1      V2      CNT    0      SWP
BIN      V1      0       V =   V(IN)
C1       V2      0       30n
BOUT     OUT    0       V =   V(V2)
.ENDS    S_HOLD


```

 

```

=====Rising Edge=====
.SUBCKT  RISE_E VIN      OUT
R1       VIN      VTD    100k
C1       VTD     0       1p
BRE      OUT     0       V = 5*u(V(VIN)-V(VTD)-.1)
.ENDS    RISE_E


```

 

```

=====Falling Edge=====
.SUBCKT  FALL_E VIN      OUT
R1       VIN      VTD    100k
C1       VTD     0       1p
BRE      OUT     0       V = 5*u(V(VTD) -V(VIN)-.1)
.ENDS    FALL_E

```

 

.end

4.11.10 4.54PM  
dsauersanjose@aol.com  
Don Sauer  
http://www.idea2ic.com/