
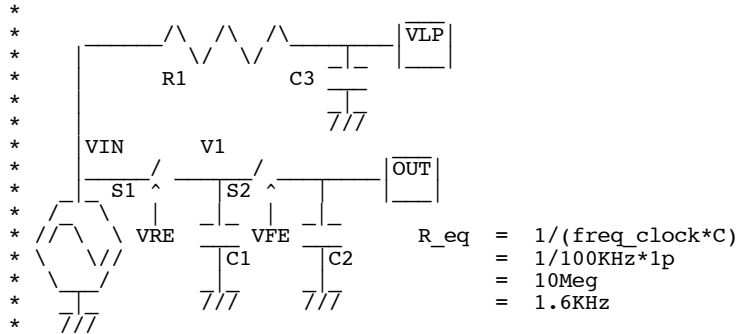


 **\*=====Switch\_Cap=====\***

A switch capacitor circuit shows why discreet time analog signal processing circuits need a two phase clock.



Capacitor C1 in the circuit above is switching charge from VIN to C2. Switch S1 is closed only a short period during a rising edge of the clock. And switch S2 is on only during the falling edge.





Capacitor C1 is in effect acting just like a resistor. In this case it resembles a 10Meg resistor. Notice it has the same wave form as R1 and C3.

```
.Options gmin = 1e-15
*v_PULSE# NODE_P NODE_N DC VALUE PULSE( VINIT VPULSE TDELAY TRISE TFALL PWIDTH PERIOD )
VCLK VCLK 0 DC 0 PULSE( 0 5 1n 1n 1n 5u 10u )
XRE VCLK VRE RISE_E
XFE VCLK VFE FALL_E
*v_SIN# NODE_P NODE_N DC VALUE SIN( V_DC AC_MAG FREQ DELAY FDamp )
VIN VIN 0 DC 0 SIN( 0 1 1.6k )
*sxxxxx N+ N- NC+ NC- MODEL <ON><OFF>
S1 VIN V1 VRE 0 SWP
S2 V1 OUT VFE 0 SWP
C1 V1 0 1p
C2 OUT 0 10p
R1 VIN VLP 10Meg
C3 VLP 0 10p
.MODEL SWP SW( VT=2.6 VH=.2 RON=1m ROFF=100MEG)
.control
*TRAN TSTEP TSTOP TSTART TMAX
tran 1u 1m 0 1u
set pensize = 2
plot vlp out vin
.endc
```

=====**Full\_Netlist\_For\_Copy\_Paste**=====

Switch\_Cap

  

$$R_{eq} = 1/(freq\_clock * C)$$

$$= 1/100KHz * 1p$$

$$= 10Meg$$

$$= 1.6KHz$$

```
.Options gmin = 1e-15
*V_PULSE# NODE_P NODE_N DC VALUE PULSE( VINIT VPULSE TDELAY TRISE TFALL PWIDTH PERIOD )
VCLK VCLK 0 DC 0 PULSE( 0 5 1n 1n 1n 5u 10u )
XRE VCLK VRE RISE E
XFE VCLK VFE FALL E
*V_SIN# NODE_P NODE_N DC VALUE SIN( V_DC AC_MAG FREQ DELAY FDamp )
VIN VIN 0 DC 0 SIN( 0 1 1.6k )
*SXXXXXX N+ N- NC+ NC- MODEL <ON><OFF>
S1 VIN V1 VRE 0 SWP
S2 V1 OUT VFE 0 SWP
C1 V1 0 1p
C2 OUT 0 10p
R1 VIN VLP 10Meg
C3 VLP 0 10p
.MODEL SWP SW( VT=2.6 VH=.2 RON=1m ROFF=10MEG)
.control
*TRAN TSTEP TSTOP TSTART TMAX
tran 1u 1m 0 1u
set pensize = 2
plot vlp out vin
.endc
*=====Rising_Edge=====
.SUBCKT RISE_E VIN OUT
R1 VIN VTD 200k
C1 VTD 0 1p
BRE OUT 0 V = 5*u(V(VIN)-V(VTD)-.1)
.ENDS RISE_E
*
* 
*=====Falling_Edge=====
.SUBCKT FALL_E VIN OUT
R1 VIN VTD 200k
C1 VTD 0 1p
BRE OUT 0 V = 5*u(V(VTD) -V(VIN)-.1)
.ENDS FALL_E
*
* 
*=====end=====
.end
```