
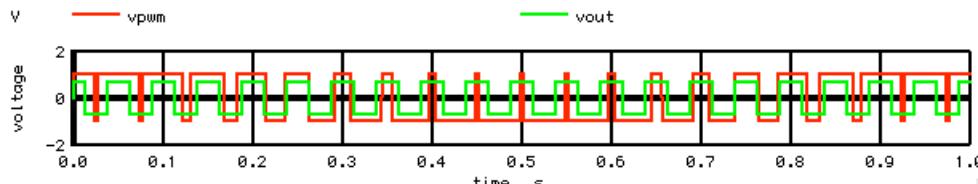


=====PWM_WithOut_PM_Sanity=====

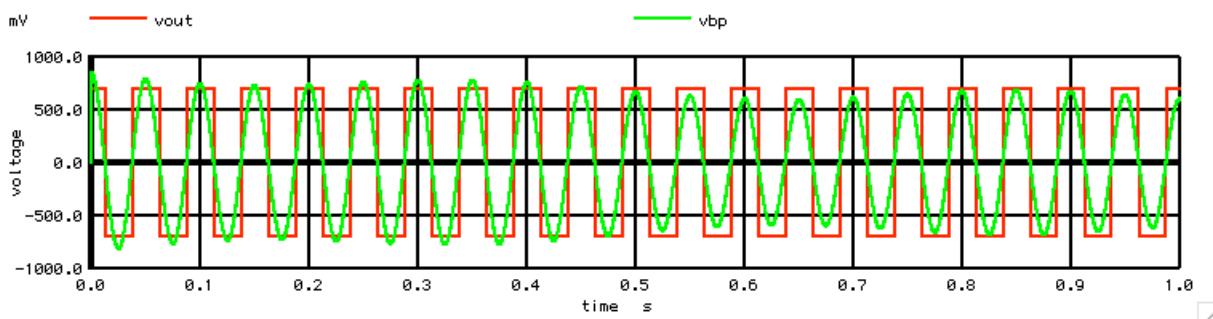A good sanity test as to whether a balanced PWM produces no phase modulation, is to linearly bandpass filter the PWM signal, and then clip it.



The Q of the bandpass filter does need to be set high enough to remove the modulating second harmonic. The output of the bandpass should still show some amplitude modulation.




Clipping the signal after the bandpass should only remove AM. PM should mainly be unaffected.

```

PWM_Without_PM_BP
*****
*          VTRI      VPWM      VBP      OUT
*          VT        VPWM     R1       L1       C1
*          VT        VPWM     B1       B2       7/7
*          VIN       VPWM     V =       V =       7/7
*          B1        VTRI    VPWM   acos(cos(2*v(VP)*20*v(VT)))/v(VP)
*          B2        VPWM    VPWM   2.0*u(1-v(VTRI)*2 + .9*cos(1*v(VP)*2*v(VT)))-1
*          B3        VREF    VPWM   1.8*u(1-v(VTRI)*2 )-.9
*          B4        VOUT    VPWM   1.4*u( v(VBP)*2 ) -.7
*          R1        VPWM    VBP   34000
*          L1        VBP     VBP   6.333 IC= 0
*          C1        VBP     VBP   10u  IC= .849
*****Run_Simulation=====
.tran  .1m  1  0  .1m  UIC
.control
run
set  pensize = 2
plot  vpwm vout
plot  vref vpwm vout xlimit 0 .05
plot  vref vpwm vout xlimit .5 .55
plot  vref vpwm vout xlimit .95 1
.endc
.end
*****
```

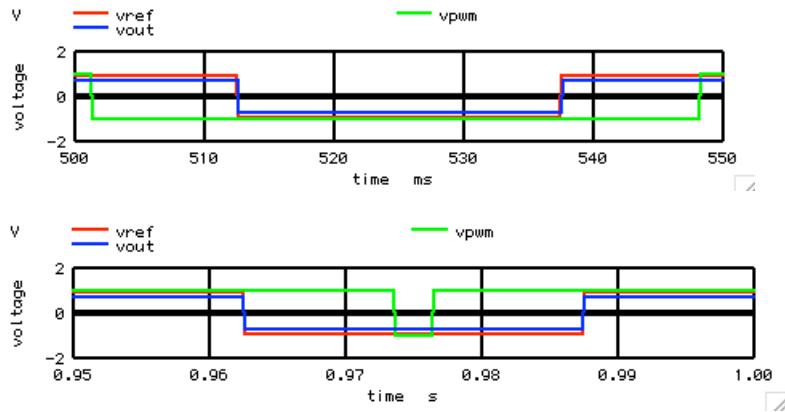The amplitude of the reference square wave and the output square wave are made slightly different on the plots below to display the fact that they are pretty much the same curve.



The PWM signal is also included for comparison.

Looks like the unmodulated square wave can be recovered from this type of pulse width modulation by just using a bandpass filter and an inverter.

=====Full_Netlist_For_Copy_Paste=====

```
PWM_Without_PM_BP
*
*          VTRI           VPWM           VBP
*          VT              VT              VT
*          *               *               *
*          *               *               *
*          *               *               *
*          *               *               *
*          *               *               *
*          *               *               *
*          *               *               *
*          *               *               *
*          VT              VT              VT
*          B1              B2              R1
*          7/7              7/7              7/7
*          7/7              7/7              c1
*          7/7              7/7              L1
*          7/7              7/7              7/7
*          7/7              7/7              OUT
*
VP      VP      0      DC      3.141592653589793
VT      VT      0      PWL     ( 0 0 1 1 )
VIN    VIN    0      DC      1 AC 1
B1      VTRI   0      V =      acos(cos(2*v(VP)*20*v(VT)))/v(VP)
B2      VPWM   0      V =      2*u(1-v(VTRI)*2 + .9*cos(1*v(VP)*2*v(VT)) )-1
B3      VREF   0      V =      1.8*u(1-v(VTRI)*2 )-.9
B4      VOUT   0      V =      1.4*u( v(VBP)*2 )-.7
R1      VBP    VBP   34000
L1      VBP    0      6.333  IC= 0
C1      VBP    0      10u    IC= .849
.tran  .1m    1  0    .1m    UIC
.control
run
set    pensize = 2
plot  vpwm vout
plot  vout vbp
plot  vref vpwm vout xlimit 0 .05
plot  vref vpwm vout xlimit .5 .55
plot  vref vpwm vout xlimit .95 1
.endc
.end

2.12.10_3.08PM
dsauersanjose@aol.com
Don Sauer
http://www.idea2ic.com/
```