 



A simple Asynchronous ADC

(Auto-Folding Multi-Bit Comparator)
(US Pat. 7839317)




A Simple 4Bit 1GHz Level-Crossing A to D

This invention could have been invented in the late 60's. Would a high speed comparator which provides a multi-bit output been useful back then? And the architecture is simple and all NPN. The circuit shown above is **actually the full schematic for a 4 bit 1GHz asynchronous level crossing A to D**. The **digital elements shown in blue** are not drawn at transistor level since **differential logic needs to be used**. All the **DC reference currents shown in green** match each other in current value. All NPNs are minimum 1X geometries, and the reference currents are chosen to run all NPNs at their maximum ftau. The **analog input shown in red** is an input current having a full scale range from **zero to the reference current level**. When the NPNs are modeled as having a ftau at 4GHz, the digital output response to a full scale 16ns ramp input current is shown below.

 


Each cell is doing a current comparison to the reference current, but it is also outputting a folded version of the analog signal current as well. Some simple first order speed up techniques have been applied to allow **4GHz NPNs** to track a moving input with **no missing codes at a 1GHz rate**. Some much better modeling, and some more advanced speed up techniques might allow the LSB tracking output code rate to come even closer to the τ of the transistors.

 The XOR logic circuit is reformatting the digital output into the normal binary format. Notice how when the MSB reverses state, all the other bits need to reverse state at the same time.




 The pre-processed digital output has an interesting format. **Only one cell is able to switch state at a given time.** When any of the cells switch state, all the other cells are stationary. So a single output state change could trigger all the bits to be cleanly sampled. The XOR function can then be applied later at any time.




The comparator cell was actually invented as a way to perform an absolute value function on two input current sources (4,069,460). It has since then found other uses, such as for a precise AM decoder for use in an AM stereo decoder (4,359,693).


The circuit is essentially a dual input current mirror in which the larger of two input currents take over the current mirror. Some voltage clamping transistors prevent saturation while provide an output current equal to the absolute difference between the two input currents. If I_{in} is 0.2mA larger than I_{ref} , 1.2mA will flow in Q_{n1} and Q_{n2} . Transistors Q_{n4} and Q_{n6} will be off. And transistor Q_{n5} will make up the 0.2mA difference in input current.

 


Now if the I_{in} current is ramping up, it becomes obvious that the input current is both being compared and folded at the output at the same time. The comparator's differential input voltage will toggle around the reference current, and can be used as a differential digital output port. The absolute value output current happens to be the input current folded around the reference current. This folded output current can be sent to another stage, and the analog signal gets compared and folded a again.

 

 The current processing of the signal is mathematical. Each stage compares the current between an analog input current and a reference current. The analog input current further gets folded to an absolute value of the difference between the two input currents. This folded output current can then be passed on to a series of following stages.




But the folding of the analog signal is being done just like it would be done on a piece of paper. Every fold means a half reduction in magnitude. This means that the reference currents will have to be reduced by a factor of two at each stage. A need for speed makes it desirable to use minimum geometries for all transistors in the signal path. And all the transistors need to operate at an optimum current level to have a maximum f_{tau} .

 

High Speed Simulation Bit Block

Some simple first order techniques to address speed issues are shown in the circuit above. Transistors **Qn6** and **Qn5** make up for the gain reduction happening at each current fold. A NPN transistor which has a 4GHz f_{tau} is being used as a model. This NPN has an optimum f_{tau} around 1mA. Transistors **Qn1** to **Qn4** all want to be biased up to run as fast as possible. Diode **D6** and resistor **R6b** are biasing **Qn3** and **Qn4**. Degeneration resistors at **Qn1** and **Qn2** may be desirable to enhance matching.


The biggest problem is when a transistor turns off, it often takes a while to turn back on. So transistors **Qn7** and **Qn8** have pick up the additional job of being clamping diodes. The voltages between the bases of **Qn3** and **Qn4** is the actual digital output. These nodes are going to want to go to some differential logic stage. Raising the **Vbias** voltage applied to **Qn7** and **Qn8** will begin to limit the voltage swing of the differential digital output. So **Vbias** can control the degree to which transistors like **Qn3**, **Qn4**, **Qn7** and **Qn8** can turn off. So how little of a input voltage does internal differential logic need? A swing around $\pm 50mV$ between the bases of **Qn3** and **Qn4** might be a good place to start.

 

Output current for a 160ns Input Ramp


Whenever something turns off, it will have a little delay at turning back on. In amplifier applications, this is often called cross over distortion. It will create a glitch for a short amount of time. Biasing transistors to stay on will reduce this effect.

All reference currents at 1mA

 


$0 < I_{in} < 1\text{mA}$ A 4bit ADC with a 160ns/1mA Input Ramp

 Using the higher speed cells, the connection of the cells has become easier. Everything gets biased to the same reference current of 1mA. This tends to bias all NPNs at a maximum τ .




a 160ns Ramp

 The crossover glitches have a convenient format. They appear to want to distort all the folded analog waveforms at their endpoints. This is convenient in that the critical current comparison is always happening at the center of the folded waveforms.



But folding every stage means that currents get toggled twice as fast for every bit stage. When toggling speeds approach the f_{tau} of the transistors, the crossover glitches may no longer be at just the endpoints. At high enough speeds, they begin to migrate away from the endpoints, and start interfering with the current comparison process.

 This is an interesting type of failure. It means that missing lsb codes starts to appear at higher input slew rates. So there is a bit resolution versus input slew rate tradeoff. Put in a faster moving analog signal, and get a lower bit resolution digital output.



Simulation suggests that 4 cells can track a 16nsec full scale ramp and produce all 16 individual LSB codes at a rate of 1GHz per LSB. The f_{tau} for the NPNs is only 4GHz. Only some simple speed up techniques were used to do this. Just how close the conversion rate can come to matching f_{tau} is going to require an exception ability to match silicon to spice models.

 


FIG 11 ADC_{4bits}(10MHz) Input/Output

Apply a Full scale 10Mhz sine wave to the input, and then mathematically reconstruct the digital output back into a analog waveform. This shows that the output transitions are not happening at a periodic rate. In some applications, this has the benefit in that the digital output is only changing state when something is actually happening.

This kind of digitizing of analog signal has been referred to as level crossing sampling, or as a threshold crossing detector, or as an Asynchronous Analog-to-Digital Converters, or even as a Level-Crossing Flash Asynchronous Analog-to-Digital Converter.

Where as a normal A to D stores its resolution in terms of a precise voltage level, this type of converter stores its resolution in terms of a precise time when something has happened. There has been some interest in using this type of a converter lately. The following are some recent examples of Asynchronous ADC activity off the web.

- [6 bit Asynchronous December 2006](#)
- [Asynchronous ADC In CAD Mentor Graphics](#)
- [Asynchronous Data Processing System](#)
- [ASYNCHRONOUS PARALLEL RESISTORLESS ADC](#)
- [Flash Asynchronous Analog-to-Digital Converter](#)
- [Novel Asynchronous ADC Architecture](#)
- [LEVEL BASED SAMPLING FOR ENERGY CONSERVATION IN LARGE NETWORKS](#)
- [A Level-Crossing Flash Asynchronous Analog-to-Digital Converter](#)
- [Weight functions for signal reconstruction based on level crossings](#)
- [Adaptive Rate Filtering Technique Based on the Level Crossing Sampling](#)
- [Adaptive Level-Crossing Sampling Based DSP Systems](#)
- [A 0.8 V Asynchronous ADC for Energy Constrained Sensing Applications](#)
- [Spline-based signal reconstruction algorithm from multiple level crossing samples](#)
- [A New Class of Asynchronous Analog-to-Digital Converters](#)
- [Effects of time quantization and noise in level crossing sampling stabilization](#)

Here is some more background information on Analog to Digital converters.

- [A 1-GS/s 6-bit 6.7-mW ADC](#)
- [A Study of Folding and Interpolating ADC](#)
- [Folding ADCs Tutorials](#)
- [high speed ADC design](#)
- [Investigation of a Parallel Resistorless ADC](#)

Here are some patents on the subject.

[4,291,299 Analog to digital converter using timed](#)
[4,352,999 Zero crossing comparators with threshold](#)
[4,544,914 Asynchronously controllable successive approximation](#)
[4,558,348 Digital video signal processing system using](#)
[5,001,364 Threshold crossing detector](#)
[5,315,284 Asynchronous digital threshold detector](#)
[5,945,934 Tracking analog to digital converter](#)
[6,020,840 Method and apparatus for representing waveform](#)
[6,492,929 Analogue to digital converter and method](#)
[6,501,412 Analog to digital converter including a quantizers](#)
[6,667,707 Analog to digital converter with asynchronous ability](#)
[6,720,901 Interpolation circuit having a conversio2](#)
[6,850,180 SelfTimed ADC](#)
[6,965,338 Cascade A D converter](#)
[7,133,791 Two mean level crossing time interval](#)

11.19.10_1.20PM
dsauersanjose@aol.com
Don Sauer