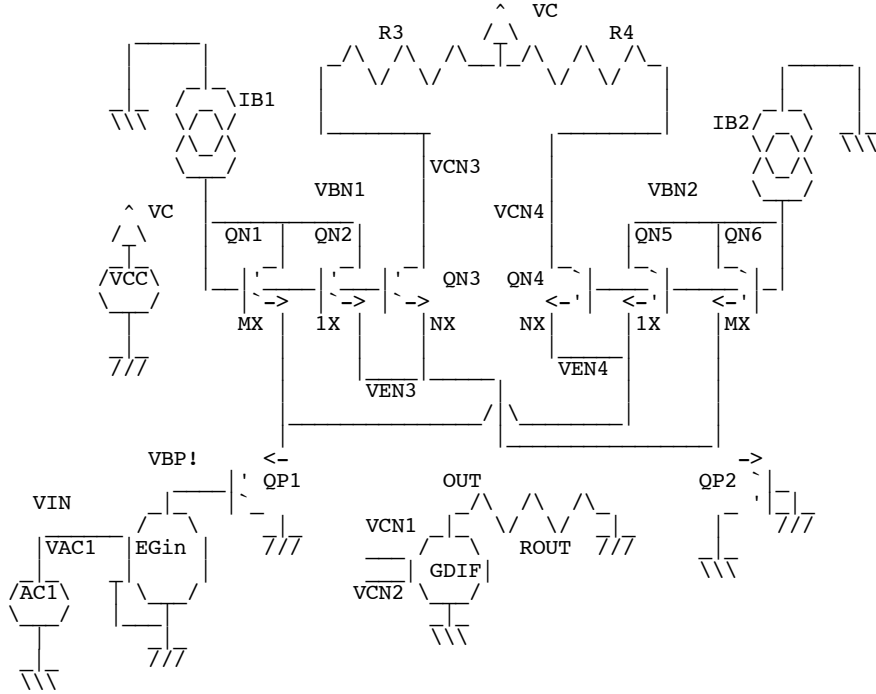


AB_BIAS_DIFF_Thd_MX

* www.idea2ic.com
 * dsauersanjose@aol.com 4/23/08



```
.OPTIONS GMIN=1e-18 METHOD=trap srcsteps = 1 gminsteps = 1
*****
VCC      VC      0          DC      10
VAC1     VIN     0          DC      0      SIN( 0      1  1000 )
IB1      0      VBN1      1u
IB2      0      VBN2      1u
QN1      VBN1   VBN1     VE4     NPN1   4.70
QN2      VBN1   VBN1     VE3     NPN1   1.00
QN3      VCN3   VBN1     VE3     NPN1   15.00

QN4      VCN4   VBN2     VE4     NPN1   15.00
QN5      VBN2   VBN2     VE4     NPN1   1.00
QN6      VBN2   VBN2     VE3     NPN1   4.70

QP1      0      VBP1     VE3     PNP1   1.00
QP2      0      0         VE4     PNP1   1.00
R3       VCN3   VC        1K
R4       VCN4   VC        1K
E_DIF    OUT    0         VCN3   VCN4   1
ROUF     OUT    0         1K
E_GAININ VBP1   0         VIN     0      1m
```

```
.control
tran      25u          5m          0      1u
plot      out
echo      "THD% versus VIN_vpk "
setplot   new
set       NameList = ( Mx4 Mx4pt25 Mx4pt5 Mx5 )
compose  NxVals    values  4  4.25  4.5  5
compose  VinVals   values  10m 30m 35m 40m 60m 70m 80m 100m 110m 120m 140m 150m 170m 185m 200m
250m
settype   voltage    VinVals
let       NoOfNx = length(NxVals)
let       NoOfVin = length(VinVals)

begin
unset
interrupt
* =====Loop_Nx=====
let      j      = 1
while   (j      <= NoOfNx )
let     Nx      = NxVals[j-1]
alter   QN1    area = $&Nx
alter   QN6    area = $&Nx
set     thisName = $NameList[$&j]
let     $thisName = 0*vector(NoOfVin)
```

```

* =====Loop_Vin=====
let      k          = 1
while   (k          <= NoOfVin )
let     Vin         = VinVals[k-1]
alter   e_gainin gain = $&Vin
tran    25u        5m          0      1u
linearize
set     specwindow= "blackman"
spec    200      8k      200      v(out)
let     thdsq       =mag(out[9])^2 +mag(out[14])^2 +mag(out[19])^2 +mag(out[24])^2
let     thd_percent= 100*sqrt(thdsq)/mag(out[4])
echo    "$&unknown.Vin      $&thd_percent"
let     unknown.{ $thisName}[unknown.k-1] = thd_percent
repeat  3
destroy
end
if      ($?interrupt)
goto   bail
endif
let     k           =      k + 1
endwhile
setscale VinVals
plot   $NameList loglog title "AB_BIAS THD_% vs Vin_pK and Mx"
let     j           =      j + 1
endwhile
label  bail
echo   "Done."
end
.endc

*=====
.model  NPN1  NPN(  BF=2100  VAF=216 )
.model  PNP1  PNP(  BF=2100  VAF=21 )
.end


```

=====END_OF_SPICE=====

To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>


**This simulation only works on MacSpice for now.
Data in spice apparently gets stored in vectors which
are ready to be plotted.**

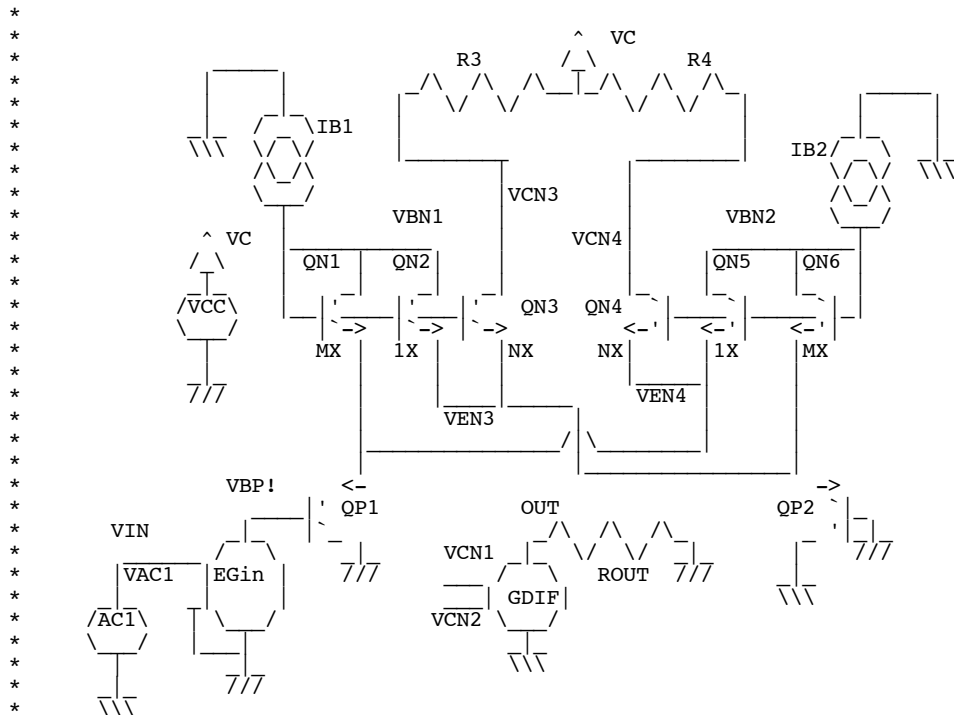**The real goal to a OTA differential input is to actually be
able to lower the overall offset and noise while at the
same time improving the distortion performance.**



A normal input stage actually has its noise defined by the number of electrons that flow through it. To be able to break this barrier, the input stage needs to be AB biased. That means that the differential input stage needs to be able to put out more differential output current than it is drawing DC wise.

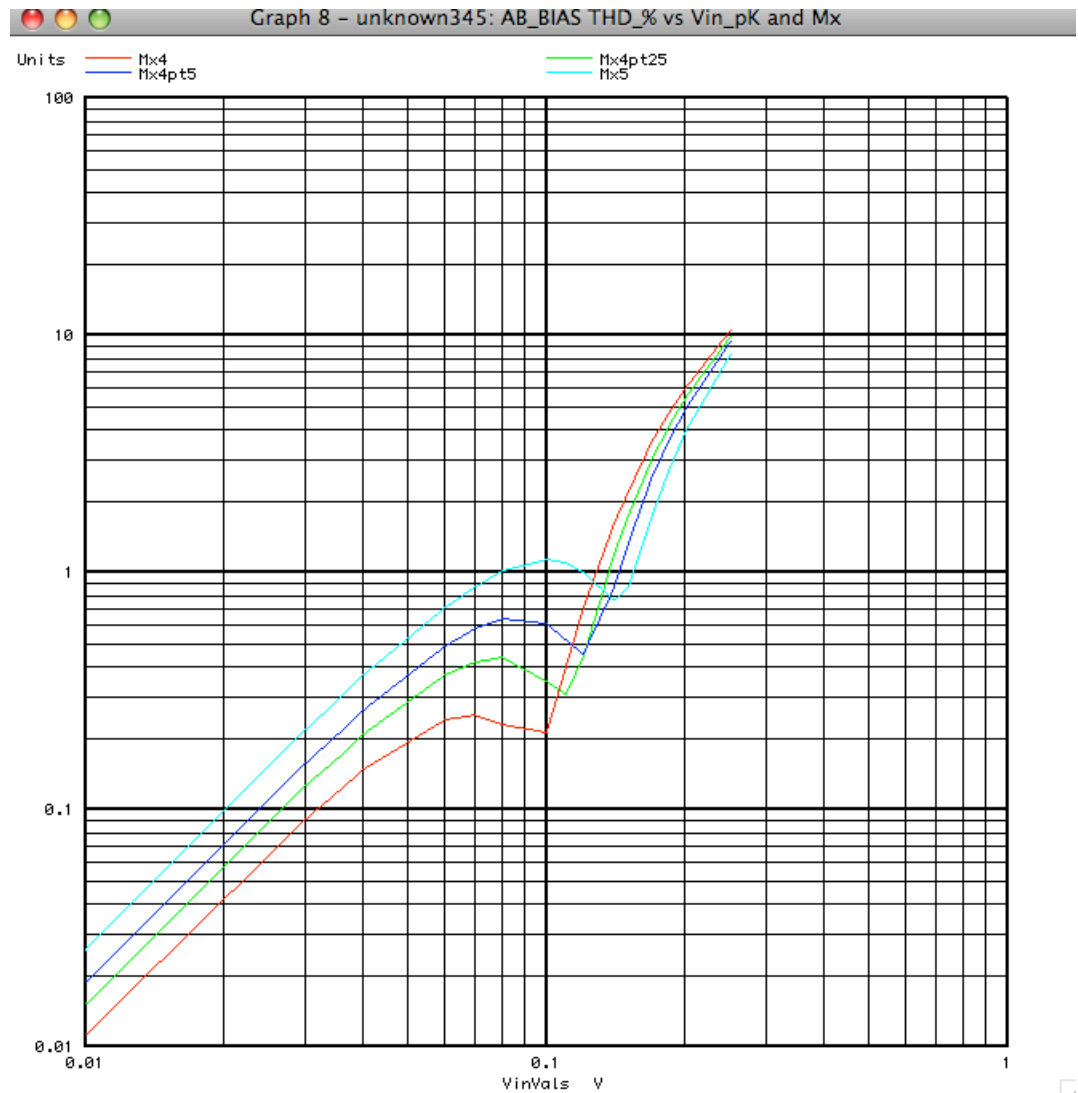A invention above is doing this with two area ratios. The NX ratio term defines a current gain which is possible to take place in output transistors QN3 and QN4. The MX term defines what DC current is present with no input signal.




This simulation tests various sizes of the M area ratio. The larger the value of M, the more the AB_Biased input stage is B biased. Less current will flow with no signal. This will lower the overall effects of both offset and noise. However the input distortion will also be higher because it will introduce a type of crossover distortion.

A smaller value of M is a more A biased input stage. The distortion at low signals is better. But the performance of noise, offset, and maximum input signal are all reduced.

For a M value around 4.5, the 1% distort is about at the 150mV level compared to the 18mV level for a normal differential input stage. The distortion levels for the dual differential input stage are shown below.

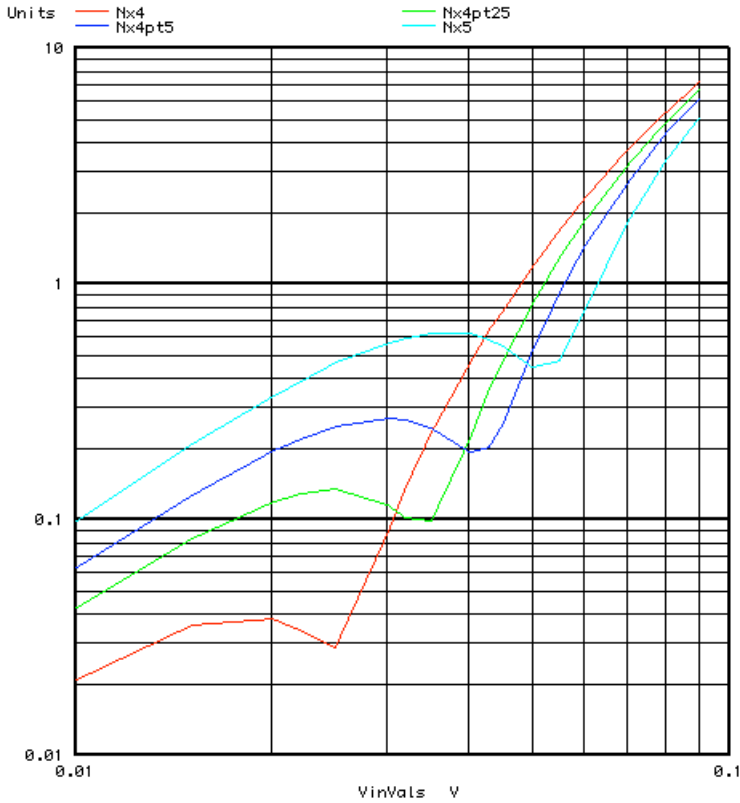Graph 133 - unknown1452: DUAL_DIFF THD_% vs Vin_pK and Nx



There appears to be least a factor of two increase in the magnitude of input voltage signal. But really the dual differential input stage should be thought of as having 1% distortion at 62% of its maximum differential output current. The AB_Bias input is at about 75% of the maximum available output current at the same level of distortion.